

---

# **EE434**

## **ASIC & Digital Systems**

Partha Pande  
School of EECS  
Washington State University  
pande@eecs.wsu.edu

Spring 2015  
Dae Hyun Kim  
daehyun@eecs.wsu.edu

---

## Lecture 2

# Introduction to CMOS Gates


*Ref: Textbook chapter 2*

*Some of the slides are adopted from Digital  
Integrated Circuits by Jan M Rabaey*
 
# Signals

---


- $0 = V_{SS} = \text{Ground} = \text{GND} = \text{Low} = 0\text{V}$
- $1 = V_{DD} = \text{Power} = \text{PWR} = \text{High} = 5\text{V}, 3.3\text{V}, 1.5\text{V}, 1.2\text{V}, 1.0\text{V}$




# Switches

---


- What is a switch?

 


Electrically open

 

Electrically short

 

Electrically open

 


Electrically short

# Switches

- Function


$$F = \bar{A} \text{ (inverter)}$$

 

|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| 1 | 0 | 1 | 0 |
|   | 1 | 0 | 1 |

- Two issues

1.

 


|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| 1 | 0 | 1 | 0 |
|   | 1 | 0 | 1 |

2. Electrical modeling of the operation
 
# Static CMOS Circuit

---

- At every point in time (except during the switching transients), each gate output is connected to either  $V_{DD}$  or  $V_{SS}$  via a low-resistive path.
- The outputs of the gates assume at all times the value of the Boolean function implemented by the circuit (ignoring the transient effects during switching periods).





# Switches



---

- Two types of switches

Normally open


 
 


Normally closed

  

# Switches

- Function  
 $F = \bar{A}$  (inverter)

   




# Switches

- Function

$$F = \overline{A \cdot B}$$

$V_{DD}$

 

$V_{SS}$


F

|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 1 | 1 |
|   | 1 | 1 | 0 |

# Switches

- Function

$$F = \overline{A \cdot B}$$

 

|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 1 | 1 |
|   | 1 | 1 | 0 |


# Example

---


- $F = \overline{A + B}$  (NOR2)
- $F = \overline{A + B + C}$  (NOR3)

# Transistors as Switches





- NMOS and PMOS

 

NMOS Transistor

 


PMOS Transistor

    


# Transistors as Switches

- NMOS and PMOS

Normally open  
(NMOS)

 


Normally closed  
(PMOS)

 

# CMOS Gates

- Function

$$F = \bar{A}$$

 


|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| A | 0 | 1 | 0 |
| A | 1 | 0 | 1 |

# CMOS Gates

- Function

$$F = \overline{A \cdot B}$$

 


|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 1 | 1 |
|   | 1 | 1 | 0 |

# CMOS Gates

- Function

$$F = A \cdot B$$

$V_{DD}$

 

$V_{SS}$


F

|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 0 | 0 |
|   | 1 | 0 | 1 |



# CMOS Gates

- Function  
 $F = A \cdot B$

 


|   | A |   |
|---|---|---|
|   | 0 | 1 |
| B | 0 | 0 |
|   | 1 | 1 |




# Electrical Modeling

- Ideal switch



 


- Real switch


 


# Electrical Modeling

- Ideal switch

   







- Real switch

  

Charge



# Transistors as Switches

- NMOS and PMOS

     
 


# Threshold Drops

Pull-up network

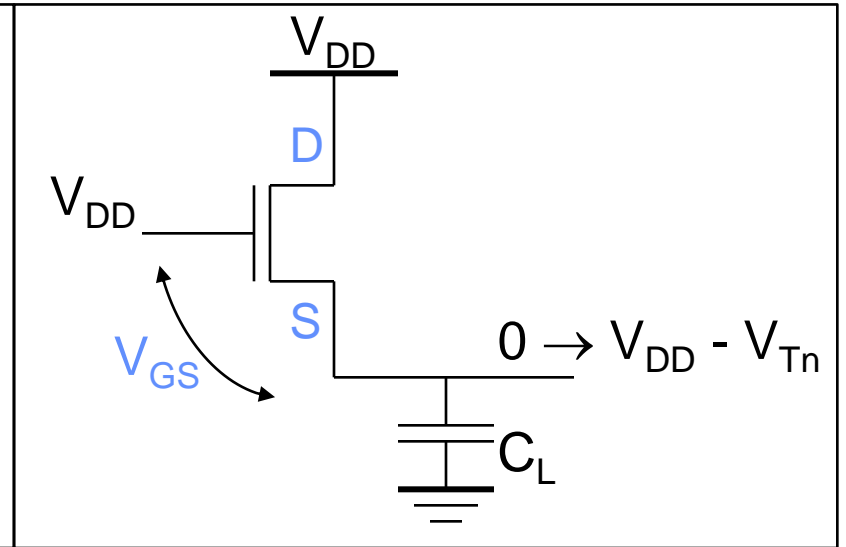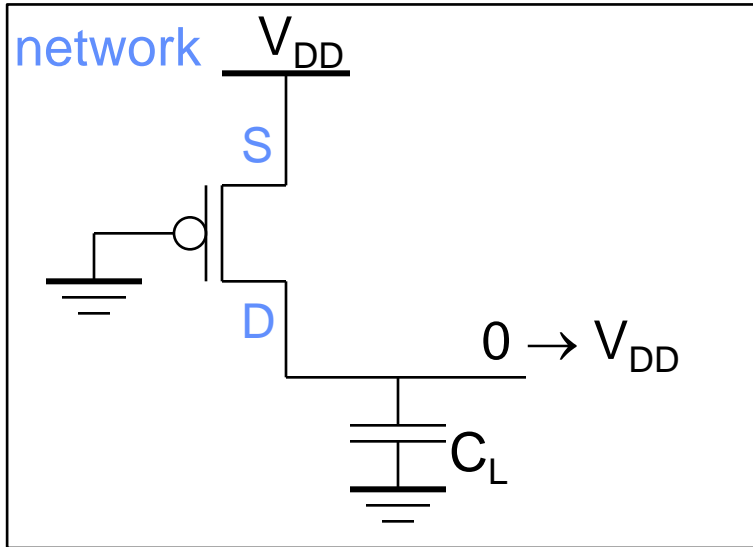


Pull-down network

 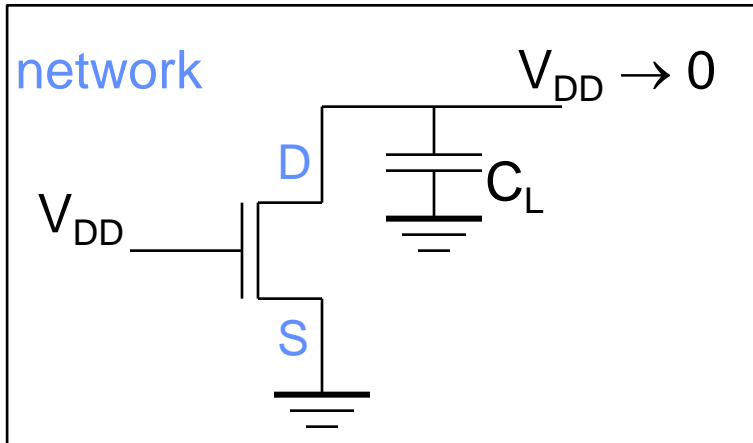

# CMOS Gates

- Function

$$F = \overline{A \cdot B}$$

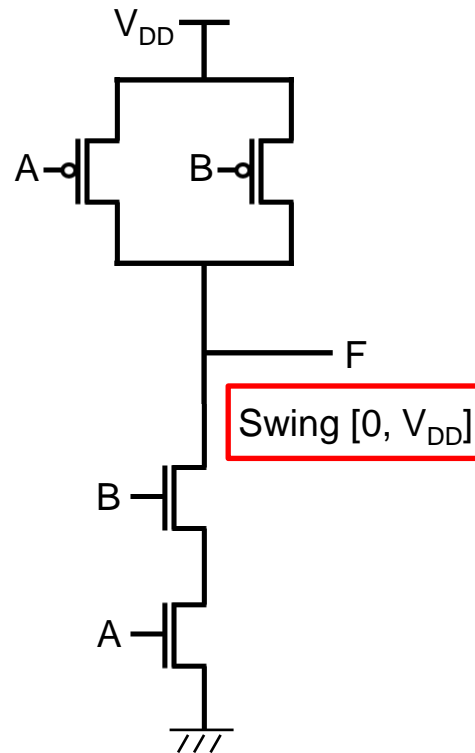


|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 1 | 1 |
|   | 1 | 1 | 0 |

# CMOS Gates

- Function

$$F = A \cdot B$$

 


**Threshold drop!**

1. Why does this happen?
2. Why is this a problem?

|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 0 | 0 |
|   | 1 | 0 | 1 |

# The MOS Transistor

 



 
# Structural Details

---

- Channel length  $L$ 
  - Typical values of  $L$  today vary from 130nm to 22 nm
  - The dimension will continue to scale according to Moore's law
- Perpendicular to the plane of the figure is the channel width  $W$ 
  - Much larger than the minimum length
- Gate oxide thickness  $t_{ox}$ 
  - Around 25 Å




# Operational Mechanism


---

- NMOS
  - N+ source and N+ drain regions separated by p-type material
  - The body or substrate, is a single-crystal silicon wafer
  - Suppose, source, drain and body are all tied to ground and a positive voltage applied to the gate
    - A positive gate voltage will tend to draw electrons from the substrate into the channel region
    - A conducting path is created between drain and source
    - Current will flow from drain to source in presence of a voltage difference between the source and the drain
    - The gate voltage needed to initiate formation of a conducting channel is termed as the threshold voltage  $V_t$

# Threshold Voltage: Concept

 


# Transistor in Linear

 


MOS transistor and its bias conditions

# Transistor in Saturation

 
 
# Drain Current (NMOS)

- Cut-off ( $V_{gsn} - V_{tn} < 0$ )
  - $I_{dsn} = 0$
- Linear region ( $V_{gsn} - V_{tn} > 0$  and  $V_{dsn} < V_{gsn} - V_{tn}$ )
  - $I_{dsn} = \beta_n \left[ (V_{gsn} - V_{tn})V_{dsn} - \frac{1}{2}V_{dsn}^2 \right]$
- Saturation region ( $V_{gsn} - V_{tn} > 0$  and  $V_{dsn} \geq V_{gsn} - V_{tn}$ )
  - $I_{dsn} = \frac{1}{2}\beta_n(V_{gsn} - V_{tn})^2$




$$\beta_n = \mu_n c_{OX} \frac{W_n}{L_n} = \mu_n \frac{\epsilon_{OX}}{t_{OX}} \cdot \frac{W_n}{L_n}$$

# Drain Current (PMOS)

- Cut-off ( $|V_{gsp}| - |V_{tp}| < 0$ )

- $I_{sdp} = 0$

 

- Linear region ( $|V_{gsp}| - |V_{tp}| > 0$  and  $|V_{dsp}| < |V_{gsp}| - |V_{tp}|$ )

- $I_{sdp} = \beta_p \left[ (|V_{gsp}| - |V_{tp}|) |V_{dsp}| - \frac{1}{2} |V_{dsp}|^2 \right]$

- Saturation region ( $|V_{gsp}| - |V_{tp}| > 0$  and  $|V_{dsp}| > |V_{gsp}| - |V_{tp}|$ )


- $I_{sdp} = \frac{1}{2} \beta_p (|V_{gsp}| - |V_{tp}|)^2$

$$\beta_p = \mu_p c_{OX} \frac{W_p}{L_p} = \mu_p \frac{\epsilon_{OX}}{t_{OX}} \cdot \frac{W_p}{L_p}$$

# CMOS Gates

- Function

$$F = \overline{A \cdot B}$$

 


|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 1 | 1 |
|   | 1 | 1 | 0 |



# CMOS Gates

- Function

$$F = A \cdot B$$

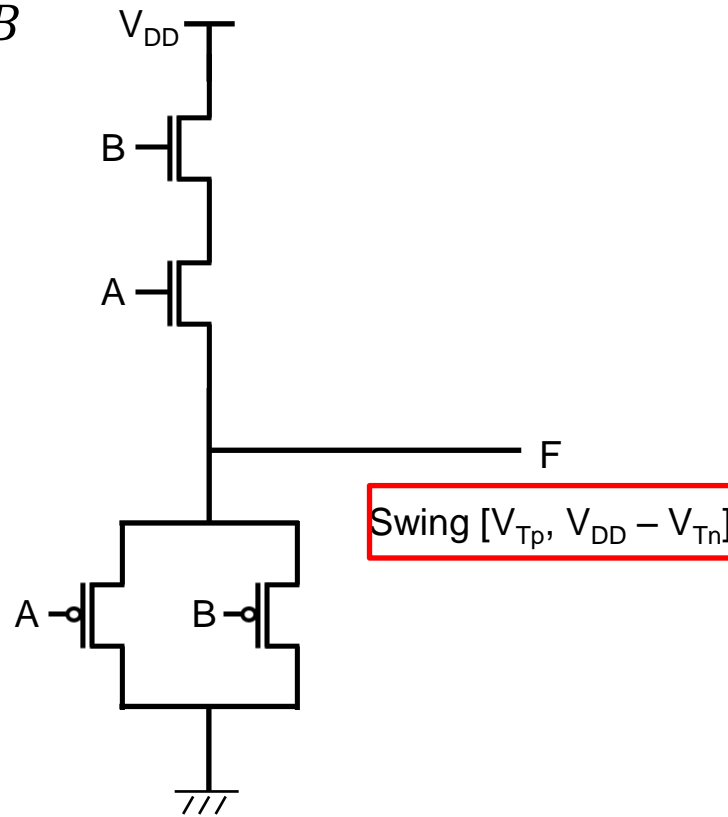


|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 0 | 0 |
|   | 1 | 0 | 1 |
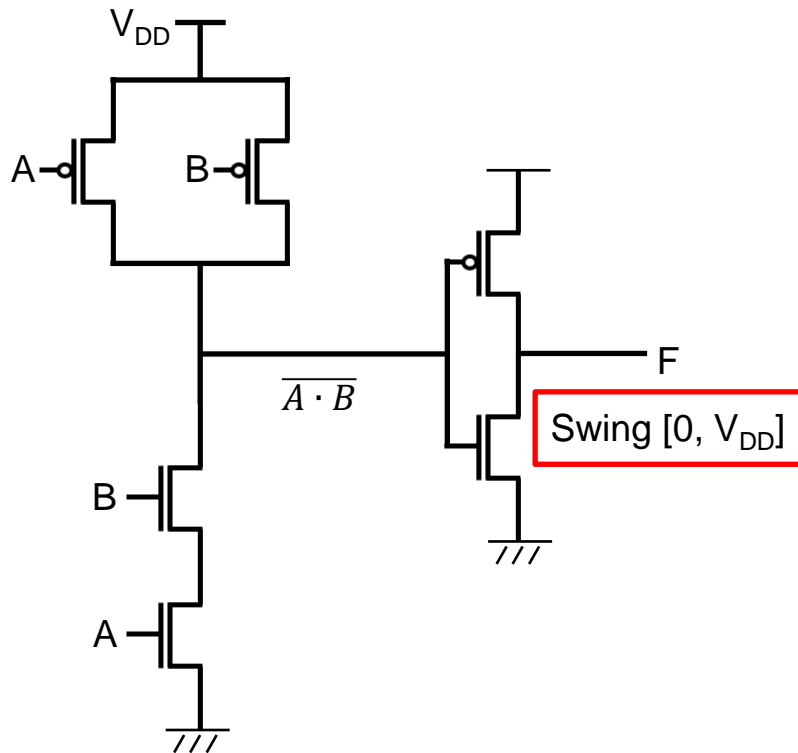
# CMOS Gates

- Function


$$F = A \cdot B = \overline{\overline{A \cdot B}}$$



|   |   | A |   |
|---|---|---|---|
|   |   | 0 | 1 |
| B | 0 | 0 | 0 |
|   | 1 | 0 | 1 |
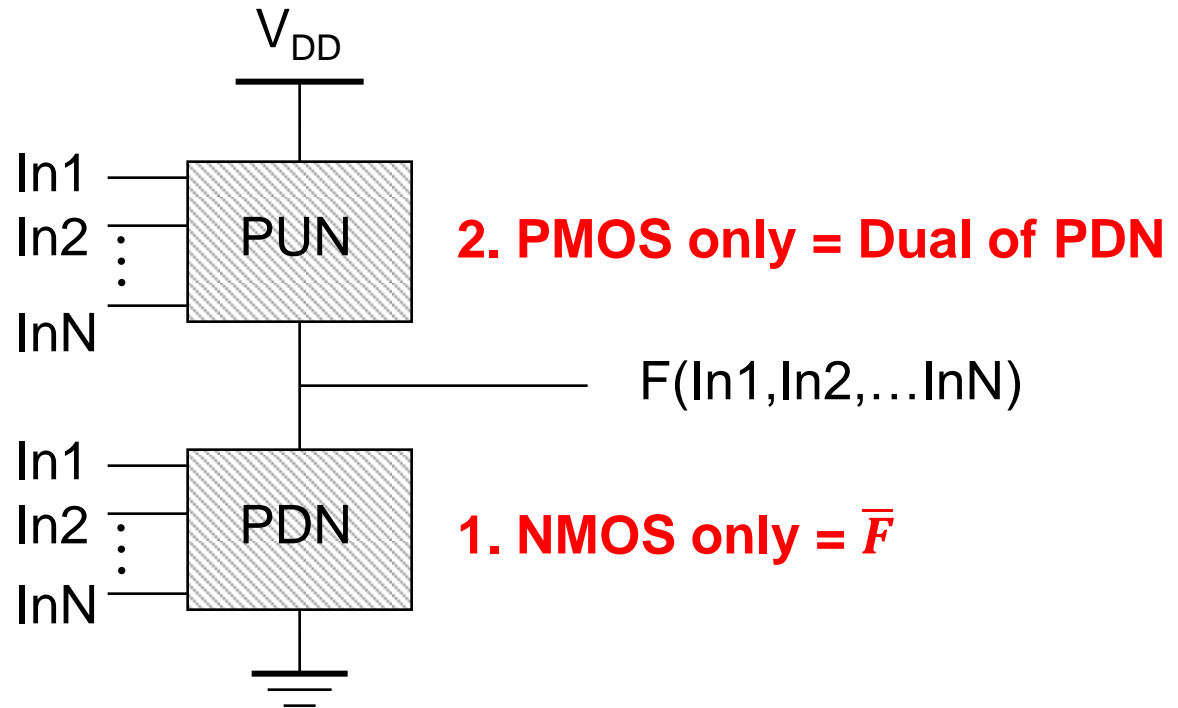
# How to Design CMOS Gates

- The function of the PUN is to provide a connection between the output and  $V_{DD}$  anytime the output of the logic gate is meant to be 1
- Similarly the role of the PDN is to connect the output to GND when the output is meant to be 0



Pull-up network (PUN) and Pull-down network (PDN) are **dual** logic networks.

# Dual Logic


---

- Dual of  $f(X_1, X_2, \dots, X_n, 0, 1, \text{AND}, \text{OR})$   
 $= f(X_1, X_2, \dots, X_n, \mathbf{1}, \mathbf{0}, \mathbf{OR}, \mathbf{AND})$
- $(A \cdot B)^D = A + B$
- $(A + B)^D = A \cdot B$
- $(1 \cdot A)^D = 0 + A = A$
- $(1 + A)^D = 0 \cdot A = 0$
- $(0 \cdot A)^D = 1 + A = 1$
- $(0 + A)^D = 1 \cdot A = A$

# Example Gate: NAND

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 0   |

Truth Table of a 2 input NAND gate

 

PDN:  $G = A B \Rightarrow$  Conduction to GND


PUN:  $F = \overline{A + B} = \overline{AB} \Rightarrow$  Conduction to  $V_{DD}$

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


# Example Gate: NOR

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 0   |


Truth Table of a 2 input NOR gate

 


# Complex CMOS Gate

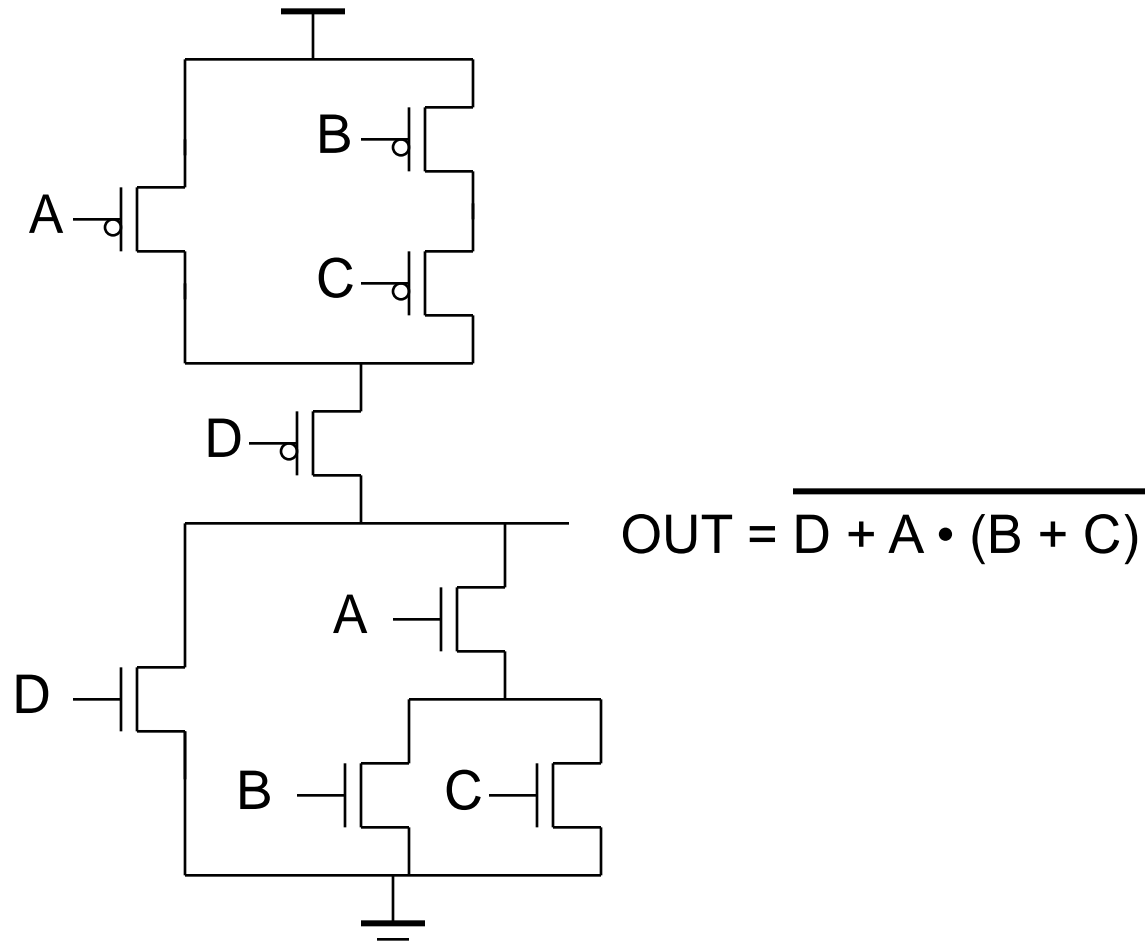


# Constructing a Complex Gate

 

(a) pull-down network

 

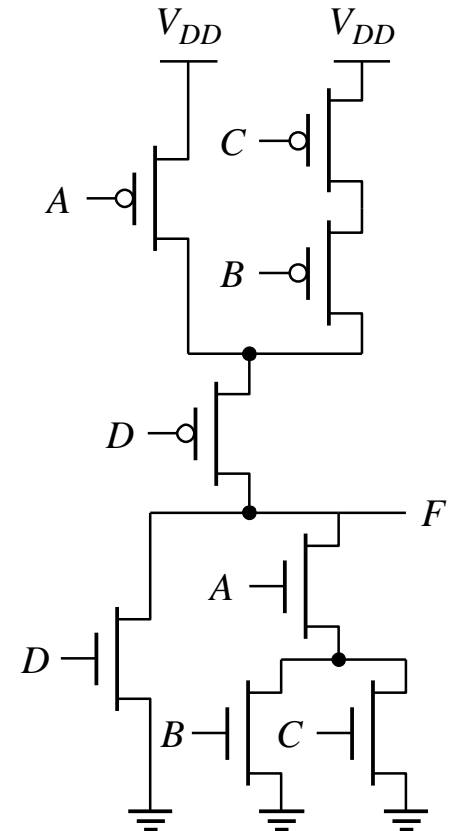(b) Deriving the pull-up network hierarchically by identifying sub-nets



(c) complete gate



# Conversion From a Boolean Equation to a Schematic

---

- For given F

1.  $F$

2.  $F = \bar{\bar{F}} = \boxed{\bar{F}} \rightarrow \text{NOT} \rightarrow F$

- $F = \overline{A \cdot B}$

- $F = A \cdot B$

- $F = A \cdot \bar{B}$

# Example

---


- $F = \overline{A \cdot B \cdot C}$  (NAND3)
- $F = A + B + C$  (OR3)
- $F = \overline{A \cdot B + C}$  (AOI21)
- $F = A \oplus B$  (XOR2)
- $F = \overline{A \oplus B}$  (XNOR2)
- $S = A \oplus B \oplus C$  (Sum)
- $CO = (A \oplus B) \cdot C + (A \cdot B)$  (Carry-out)

# DC Characteristics of CMOS Gates


---

- Need to consider
  - ON resistance
  - Parasitic capacitance


# Dynamic Behavior of MOS Transistor

 

# The Gate Capacitance

 

Top view

 


Cross section

$$C_{gate} = \frac{\epsilon_{ox}}{t_{ox}} WL$$


 
# MOS Capacitance

- The source and drain regions and the substrate form pn junctions that give rise to two additional capacitances
- The capacitances  $C_{sb}$  and  $C_{db}$  are n+p source/drain junction capacitance for NMOS devices



# MOS Capacitance

$$C_g = C_{gb} + C_{gs} + C_{gd}$$

  

Cut-off

$$C_{gs} = C_{gd} = 0$$

$$C_{gb} = \frac{C_o C_{dep}}{C_o + C_{dep}}$$

$$C_o = \frac{\epsilon_{SiO2} \epsilon_o}{t_{ox}} WL$$

$$C_{dep} = \frac{\epsilon_{Si} \epsilon_o}{d} WL$$

Linear

$$C_{gb} = 0$$

$$C_{gs} = C_{gd} = \frac{1}{2} \cdot \frac{\epsilon_{SiO2} \epsilon_o}{t_{ox}} WL$$

Saturation

$$C_{gb} = 0$$

$$C_{gd} = 0$$

$$C_{gs} = \frac{2}{3} \cdot \frac{\epsilon_{SiO2} \epsilon_o}{t_{ox}} WL$$

# MOS Resistance

---


- Average  $V/I$  at two voltages:
  - maximum output voltage
  - middle of linear region
- Voltage is  $V_{ds}$ , current is given  $I_d$  at that drain voltage. Step input means that  $V_{gs} = V_{DD}$  always.

Saturation: conductance =  $g_m = \beta(V_{gs} - V_t)$

Linear: conductance =  $g_m = \beta V_{ds}$



# MOS Resistance Approximation

 

# Example

---

- $F = \overline{A1 \cdot A2 \cdot A3 \cdot A4 \cdot A5 \cdot A6 \cdot A7 \cdot A8}$  (NAND8)