

Homework Assignment 3

(Due Nov. 29th at the beginning of the class)

Read the second project reference paper (Project reference 2 in the class website) and answer the following questions.

- (1) [**20 points**] Explain how the circuit in Fig. 1 (Basic HLFF circuit) works. Show all the details.
- (2) [**20 points**] Explain how the circuit in Fig. 4 (HLFF with ENABLE) works. Show all the details.