 


EE 466/586
VLSI Design



Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 6
MOS Inverter Circuits

The CMOS Inverter: A First Glance





CMOS Inverter

  

Two Inverters

Share power and ground


Abut cells

  


Principle of Operation

- ❖ *When the input is at V_{DD} , the NMOS device is conducting while the PMOS device (which has $V_{GS}=0$ V) is cut off*
- ❖ *V_{out} is approximately 0 V*
- ❖ *When the input is at ground, the NMOS device is cut off while the PMOS device is conducting. Only the small leakage current of the NMOS can flow, so V_{out} is very close to V_{DD}*
 - ❖ *$V_{OH} = V_{DD}$ and $V_{OL}=0$ v*
 - ❖ *Large noise margin*



CMOS Inverter Load Characteristics

 

CMOS Inverter VTC

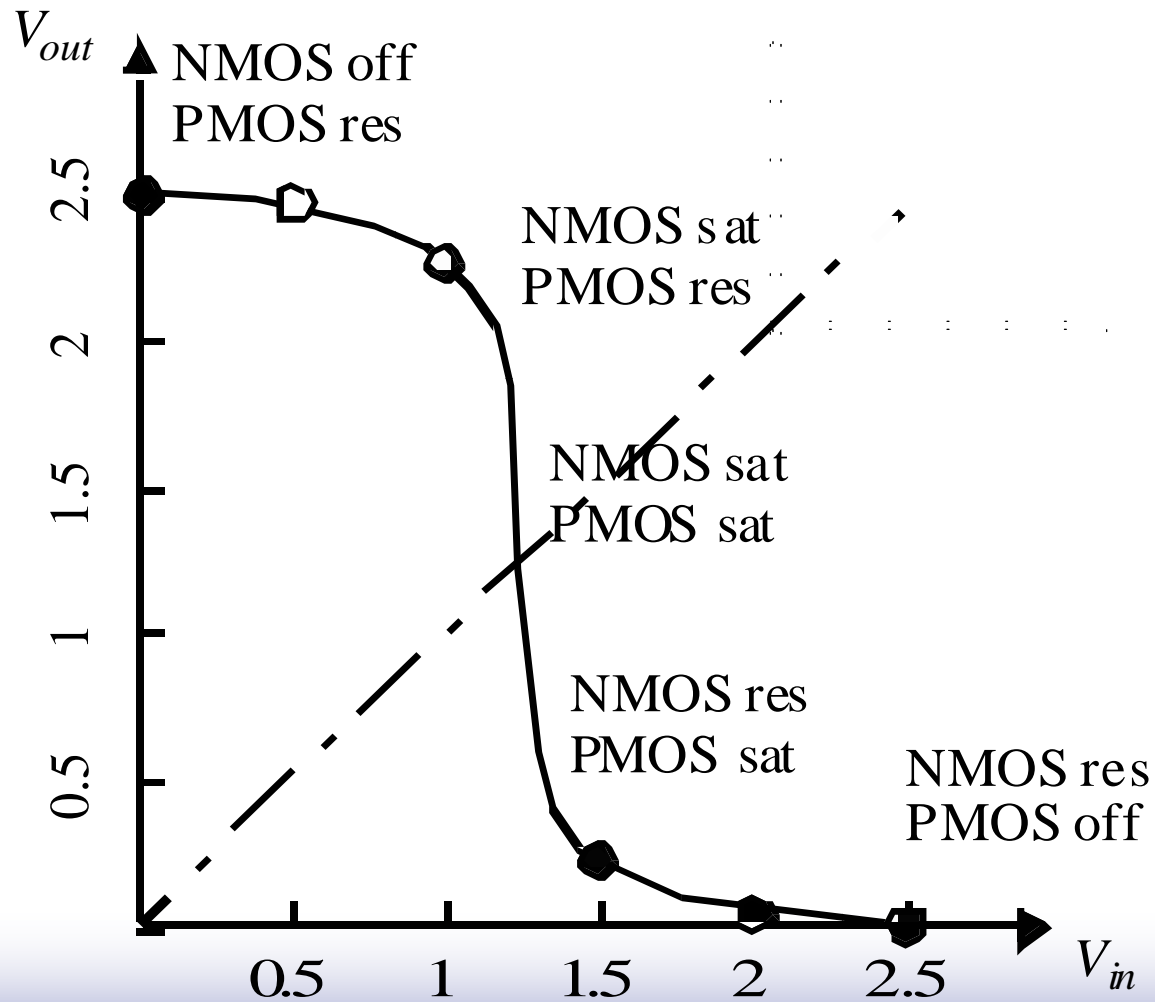

CMOS Inverter Characteristics

  

Region I: n-off, p-lin

- The NMOS device is off while the PMOS device is linear.
- The output remains at $V_{OH} = V_{DD}$ up to the point when $V_{in} = V_{TN}$

Region II: n-sat, p-lin

- ❑ The NMOS device is on and in saturation, while the PMOS device is still in the linear region since its V_{DS} is relatively small.
- ❑ $I_{DN}(sat) = I_{DP}(lin)$
- ❑ Obtain V_{IL} from here
- ❑ Follow board notes

Region III: n-sat, p-sat

- ❑ This involves the nearly vertical segment of the VTC where both transistors are saturated.
- ❑ Follow board notes
- ❑ Skewed Inverter

Region IV: n-lin, p-sat

- ❑ The NMOS device is on and in the linear region since V_{DS} is small
- ❑ PMOS device is still in saturation
- ❑ Determine V_{IH}
- ❑ Follow board notes



Region V: n-lin, p-off

- The applied input voltage is above $V_{DD} - |V_{TP}|$, so the output is now 0 V and will remain that way up to and beyond $V_{in} = V_{DD}$.

Pseudo-NMOS Inverter

- ❑ The saturated-enhancement NMOS load inverter suffers from a lower V_{OH} than the other configurations.
- ❑ The “linear”-enhancement NMOS load inverter requires two voltage supplies to produce $V_{OH}=V_{DD}$.
- ❑ One Advantage
 - when designing multi-input gates, we only require one load regardless of the number of inputs.
 - Because of the *push-pull arrangement in standard CMOS*, it needs roughly twice as many transistors to implement multi-input gates.

Pseudo-NMOS Inverter (Cont'd)

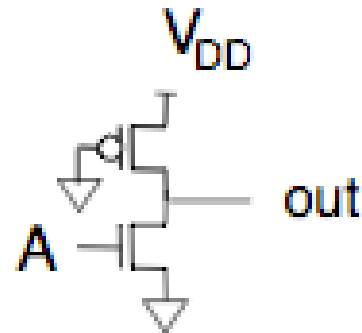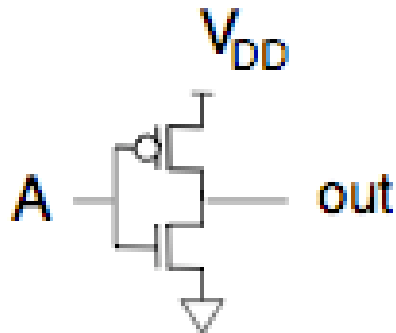

- ❑ The gate of the PMOS device is connected to ground so that the transistor is always on.
- ❑ This device is able to pull the output to V_{DD} when the NMOS device is off without the need for additional supplies.
- ❑ However, it will fight the NMOS transistor when it is on.
- ❑ it must be sized along with the NMOS device to deliver the desired V_{OL}
- ❑ Ratioed Structure
- ❑ When the output is low, power is dissipated in the pseudo-NMOS inverter

VTC of Pseudo-NMOS

- $V_{OH} = V_{DD}$
- For V_{OL}
 - $I_P(\text{Sat}) = I_N(\text{Lin})$
 - *Follow board notes*

Sizing of Inverters

- ❑ Selecting W/L ratio of the pull-up and pull-down devices
- ❑ Follow board notes