


EE 466/586
VLSI Design

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 12


Logical Effort (Cont'd)

Path Optimization using LE

 


- Introduce the concept of **stage effort**

Practical Interpretation

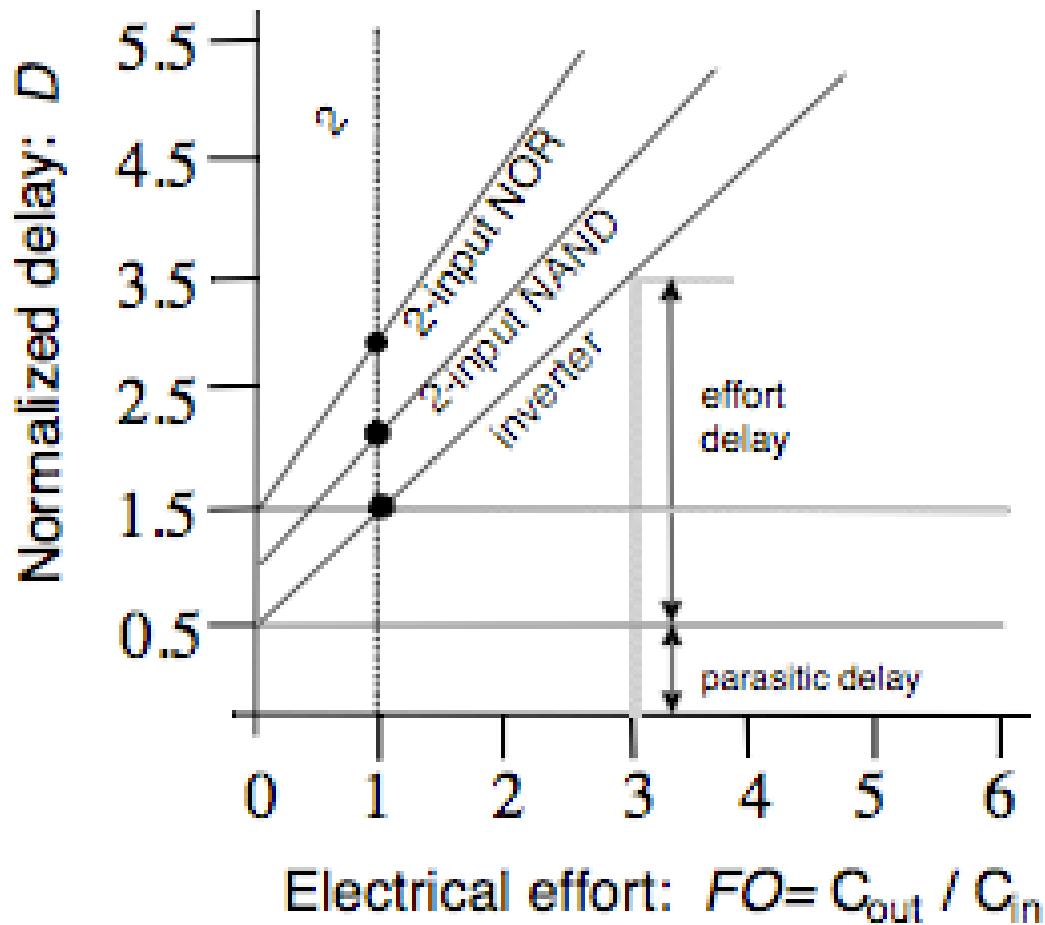


LE for a skewed inverter

 



- Follow board notes*
- LE will be different for rising and falling cases*

Path Optimization using LE

 

Follow board notes


LE of Pseudo-NMOS gates

  


$$LE = \frac{(C_{in} \times delay)_{gate}}{(C_{in} \times delay)_{inv}} = \frac{(C_{in} \times \Delta t)_{gate}}{(C_{in} \times \Delta t)_{inv}} = \frac{(C_{in} \times C_{out} \Delta V / I)_{gate}}{(C_{in} \times C_{out} \Delta V / I)_{inv}}$$

High fan-in gates

 - An 8-input AND gate is to be designed to drive a load of 200 fF, with an input capacitance of 20 fF



Pseudo-NMOS Implementation

 


□ *Which one is faster?*

Note: The LE of the gates in a logic path, by themselves, do not tell us which configuration is faster. A delay calculation must be performed to make the determination.


Branching Effort

 - Suppose there are one or more branches from a given node



$$total_path_effort = \prod LE \times BE \times FO = (\prod LE \times BE) \times \frac{C_{load}}{C_{in}}$$

Side loads

 

- ❑ *First solve without the side loads*
- ❑ *Add side load. Remove gates beyond side load but including their loading effects. Solve sub problem.*
- ❑ *Combine two solutions.*

Side loads

