

# Adder

Dae Hyun Kim

EECS  
Washington State University

---

# References

---

- Israel Koren, “Computer Arithmetic Algorithms,” 2001.
  - Chapter 5


# Table of Contents

---

- Full Adder
- Ripple-Carry Adder
- Conditional Sum Adder
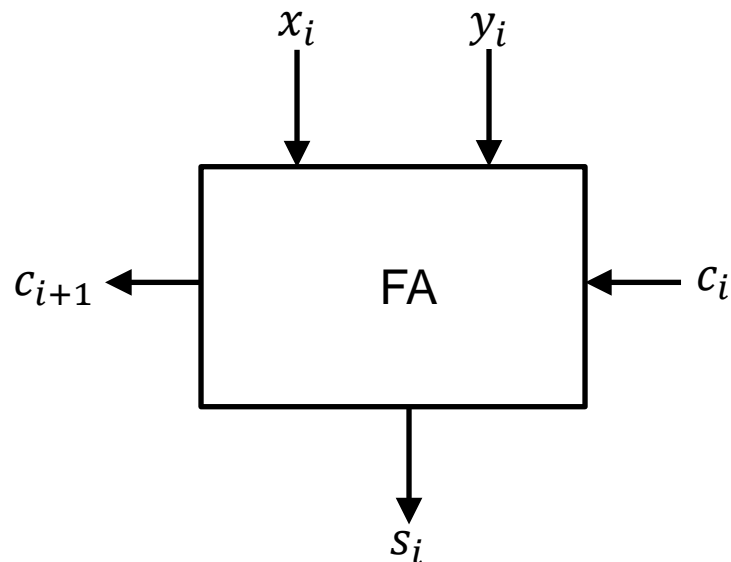
# Full Adder

- Sum
  - $s_i = x_i \oplus y_i \oplus c_i$
- Carry-out
  - $c_{i+1} = x_i \cdot y_i + c_i(x_i + y_i)$



$x_i$	$y_i$	$c_i$	$s_i$	$c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full Adder

- Delay computation

- Assume two-level logic minimization

- $s_i = x_i \oplus (y_i \oplus c_i) = x_i \oplus (y_i \cdot \bar{c}_i + \bar{y}_i \cdot c_i) = x_i \cdot \overline{(y_i \cdot \bar{c}_i + \bar{y}_i \cdot c_i)} + \bar{x}_i \cdot (y_i \cdot \bar{c}_i + \bar{y}_i \cdot c_i) = x_i \cdot y_i \cdot c_i + x_i \cdot \bar{y}_i \cdot \bar{c}_i + \bar{x}_i \cdot y_i \cdot \bar{c}_i + \bar{x}_i \cdot \bar{y}_i \cdot c_i$

- $c_{i+1} = x_i \cdot y_i + x_i \cdot c_i + y_i \cdot c_i$

- Delay for  $s_i$ :  $2 \cdot \Delta_G$

- Delay for  $c_{i+1}$ :  $2 \cdot \Delta_G$

# Ripple-Carry Adder (RCA)

- n-bit ripple-carry adder

- Delay of a FA:  $\Delta_{FA}$

$x_i, y_i, c_0: 0$


$c_1, s_0: \Delta_{FA}$

$c_2, s_1: 2\Delta_{FA}$

...

$c_{n-1}, s_{n-2}: (n - 1) \cdot \Delta_{FA}$

$c_n, s_{n-1}: n \cdot \Delta_{FA}$

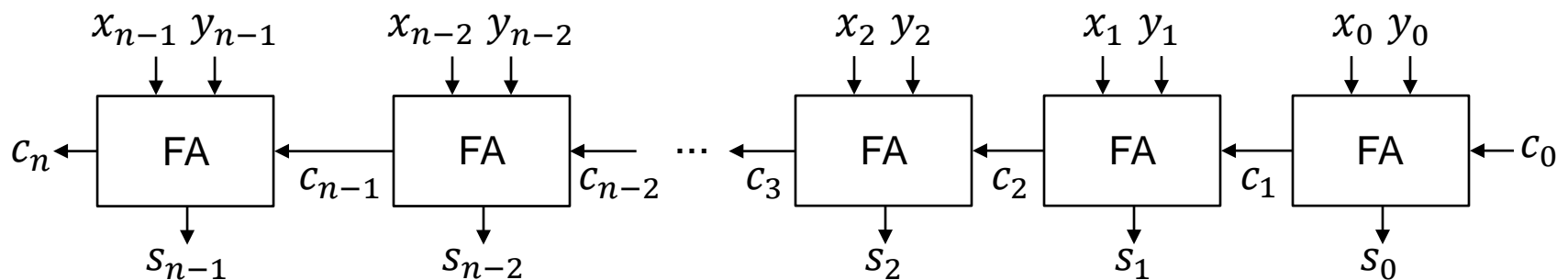


# Carry-Lookahead Adder (CLA)

- 1-level CLA

$$c_{i+1} = x_i \cdot y_i + c_i \cdot (x_i + y_i) = G_i + c_i \cdot P_i$$

$G_i = x_i \cdot y_i$ : Generated carry (the carry is always generated)

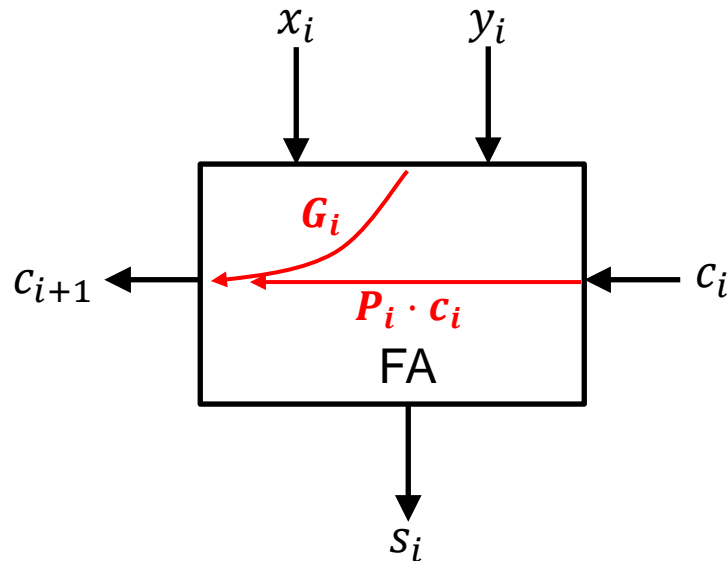$P_i = x_i + y_i$ : Propagated carry (the incoming carry  $c_i$  is propagated)



# Carry-Lookahead Adder (CLA)

- 1-level CLA

$$c_{i+1} = x_i \cdot y_i + c_i \cdot (x_i + y_i) = G_i + c_i \cdot P_i$$

$G_i = x_i \cdot y_i$ : Generated carry (the carry is always generated)

$P_i = x_i + y_i$ : Propagated carry (the incoming carry  $c_i$  is propagated)

$$c_1 = G_0 + P_0 \cdot c_0$$

$$c_2 = G_1 + P_1 \cdot c_1 = G_1 + P_1 \cdot (G_0 + P_0 \cdot c_0) = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot c_0$$

$$c_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot c_0$$

$$c_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot c_0$$

## Delay

$$G_i, P_i: \Delta_G$$

$$c_1, c_2, c_3, c_4: \Delta_G + 2\Delta_G \text{ (assuming two-level logic minimization)}$$

$$s_0: 2\Delta_G$$

$$s_1, s_2, s_3: \Delta_G + 2\Delta_G + 2\Delta_G$$



# Carry-Lookahead Adder (CLA)

- 1-level CLA

$$c_1 = G_0 + P_0 \cdot c_0$$

$$c_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot c_0$$

$$c_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot c_0$$

$$c_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot c_0$$

$$c_5 = G_4 + P_4 \cdot c_4$$

$$c_6 = G_5 + P_5 \cdot G_4 + P_5 \cdot P_4 \cdot c_4$$


$$c_7 = G_6 + P_6 \cdot G_5 + P_6 \cdot P_5 \cdot G_4 + P_6 \cdot P_5 \cdot P_4 \cdot c_4$$

$$c_8 = G_7 + P_7 \cdot G_6 + P_7 \cdot P_6 \cdot G_5 + P_7 \cdot P_6 \cdot P_5 \cdot G_4 + P_7 \cdot P_6 \cdot P_5 \cdot P_4 \cdot c_4$$

...

# Carry-Lookahead Adder (CLA)

- $n$ -bit 1-level CLA

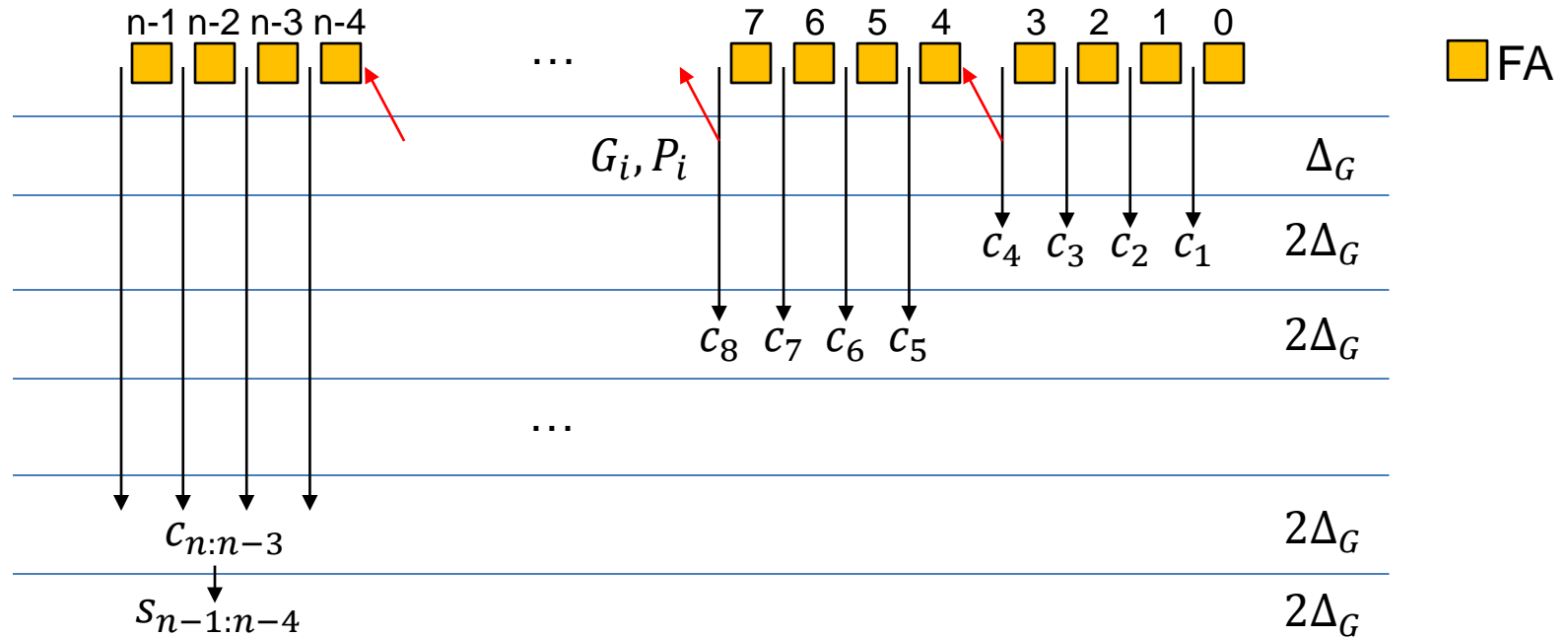

Delay

$$\Delta_G + 2\Delta_G \cdot \binom{n}{4} + 2\Delta_G = \left(\frac{n}{2} + 3\right) \Delta_G$$

# Carry-Lookahead Adder (CLA)

- 2-level CLA

$$c_1 = G_0 + P_0 \cdot c_0$$

$$c_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot c_0$$

$$c_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot c_0$$

$$c_4 = \boxed{G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0} + \boxed{P_3 \cdot P_2 \cdot P_1 \cdot P_0} \cdot c_0$$

$G_{3:0}$   $P_{3:0}$

$$c_5 = G_4 + P_4 \cdot c_4$$

$$c_6 = G_5 + P_5 \cdot G_4 + P_5 \cdot P_4 \cdot c_4$$

$$c_7 = G_6 + P_6 \cdot G_5 + P_6 \cdot P_5 \cdot G_4 + P_6 \cdot P_5 \cdot P_4 \cdot c_4$$

$$c_8 = \boxed{G_7 + P_7 \cdot G_6 + P_7 \cdot P_6 \cdot G_5 + P_7 \cdot P_6 \cdot P_5 \cdot G_4} + \boxed{P_7 \cdot P_6 \cdot P_5 \cdot P_4} \cdot c_4$$

$G_{7:4}$   $P_{7:4}$

$$c_9 = G_8 + P_8 \cdot c_8$$

$$c_{10} = G_9 + P_9 \cdot G_8 + P_9 \cdot P_8 \cdot c_8$$

$$c_{11} = G_{10} + P_{10} \cdot G_9 + P_{10} \cdot P_9 \cdot G_8 + P_{10} \cdot P_9 \cdot P_8 \cdot c_8$$

$$c_{12} = \boxed{G_{11} + P_{11} \cdot G_{10} + P_{11} \cdot P_{10} \cdot G_9 + P_{11} \cdot P_{10} \cdot P_9 \cdot G_8} + \boxed{P_{11} \cdot P_{10} \cdot P_9 \cdot P_8} \cdot c_8$$

$G_{11:8}$   $P_{11:8}$

$$c_{16} = G_{15:12} + P_{15:12} \cdot G_{11:8} + P_{15:12} \cdot P_{11:8} \cdot G_{7:4} + P_{15:12} \cdot P_{11:8} \cdot P_{7:4} \cdot G_{3:0} + P_{15:12} \cdot P_{11:8} \cdot P_{7:4} \cdot P_{3:0} \cdot c_0$$

# Carry-Lookahead Adder (CLA)

- 2-level CLA

$$c_4 = G_{3:0} + P_{3:0} \cdot c_0$$


$$c_8 = G_{7:4} + P_{7:4} \cdot G_{3:0} + P_{7:4} \cdot P_{3:0} \cdot c_0$$

$$c_{12} = G_{11:8} + P_{11:8} \cdot G_{7:4} + P_{11:8} \cdot P_{7:4} \cdot G_{3:0} + P_{11:8} \cdot P_{7:4} \cdot P_{3:0} \cdot c_0$$

$$c_{16} = G_{15:12} + P_{15:12} \cdot G_{11:8} + P_{15:12} \cdot P_{11:8} \cdot G_{7:4} + P_{15:12} \cdot P_{11:8} \cdot P_{7:4} \cdot G_{3:0} \\ + P_{15:12} \cdot P_{11:8} \cdot P_{7:4} \cdot P_{3:0} \cdot c_0$$

# Carry-Lookahead Adder (CLA)

- 16-bit 2-level CLA

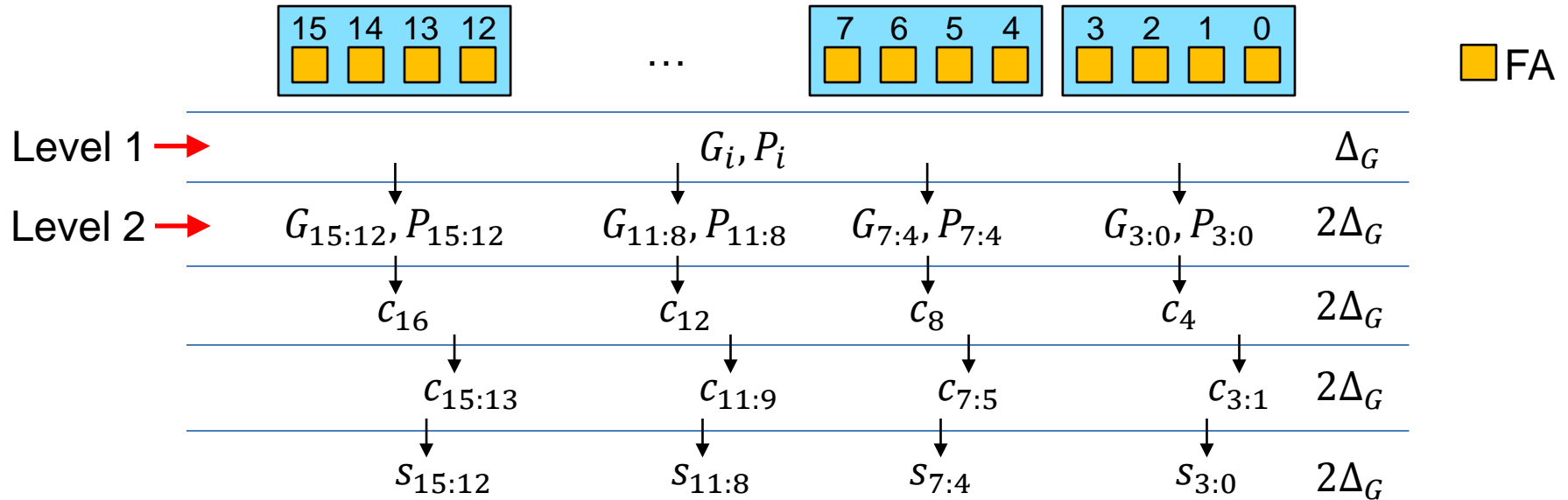

Delay:  $9\Delta_G$

# Carry-Lookahead Adder (CLA)

- $k$ -level CLA

$$c_4 = G_{3:0} + P_{3:0} \cdot c_0$$

$$c_8 = G_{7:4} + P_{7:4} \cdot G_{3:0} + P_{7:4} \cdot P_{3:0} \cdot c_0$$

$$c_{12} = G_{11:8} + P_{11:8} \cdot G_{7:4} + P_{11:8} \cdot P_{7:4} \cdot G_{3:0} + P_{11:8} \cdot P_{7:4} \cdot P_{3:0} \cdot c_0$$

$$c_{16} = G_{15:12} + P_{15:12} \cdot G_{11:8} + P_{15:12} \cdot P_{11:8} \cdot G_{7:4} + P_{15:12} \cdot P_{11:8} \cdot P_{7:4} \cdot G_{3:0} \\ + P_{15:12} \cdot P_{11:8} \cdot P_{7:4} \cdot P_{3:0} \cdot c_0$$

$$c_{20} = f_{20}(G_{19:16}, P_{19:16}, c_{16})$$

$$c_{24} = f_{24}(G_{23:20}, G_{19:16}, P_{23:20}, P_{19:16}, c_{16})$$


$$c_{28} = f_{28}(G_{27:24}, G_{23:20}, G_{19:16}, P_{27:24}, P_{23:20}, P_{19:16}, c_{16})$$

$$c_{32} = f_{32}(G_{31:28}, G_{27:24}, G_{23:20}, G_{19:16}, P_{31:28}, P_{27:24}, P_{23:20}, P_{19:16}, c_{16})$$

...

# Carry-Lookahead Adder (CLA)

- $n$ -bit  $k$ -level CLA

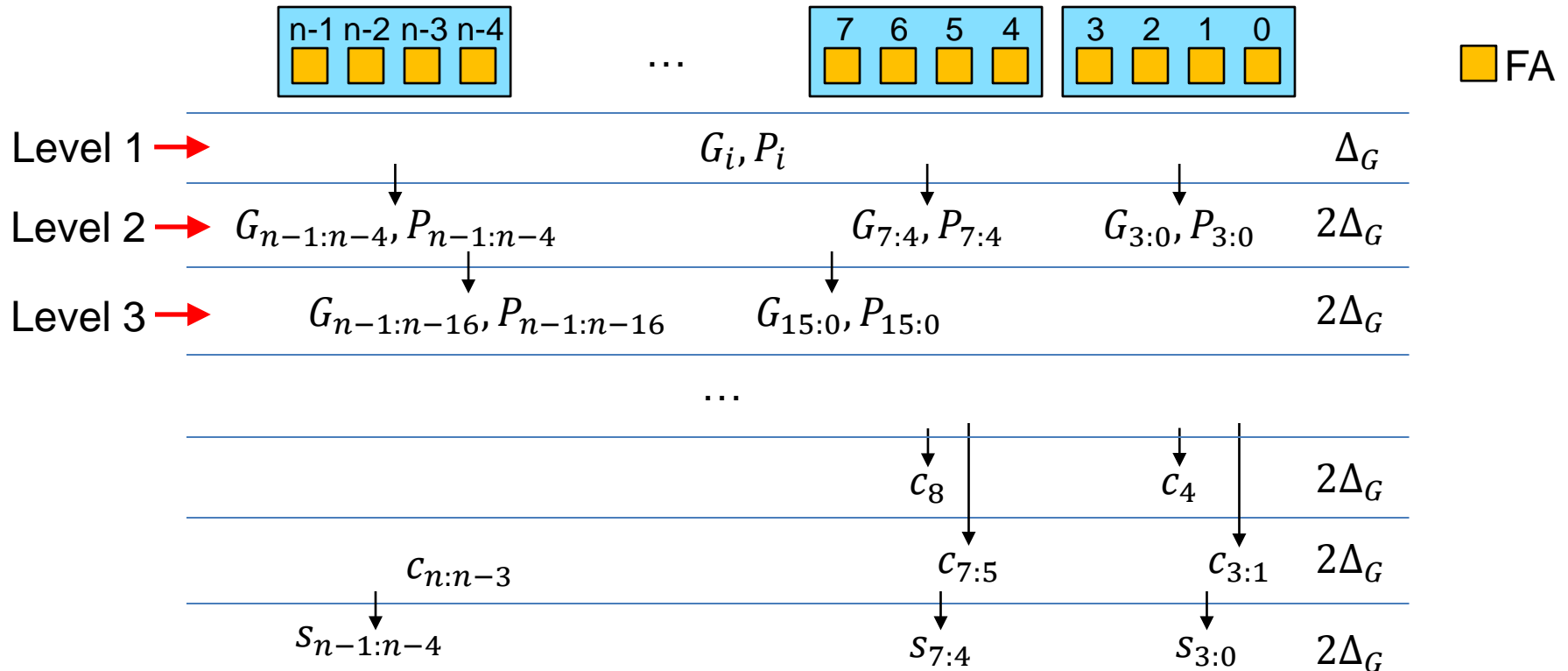


Delay

$$\Delta_G + 2\Delta_G \cdot (\log_4 n - 1) + 2\Delta_G + 2\Delta_G + 2\Delta_G = (2 \log_4 n + 5)\Delta_G$$

# Carry-Lookahead Adder (CLA)

- 64-bit CLA


■ FA

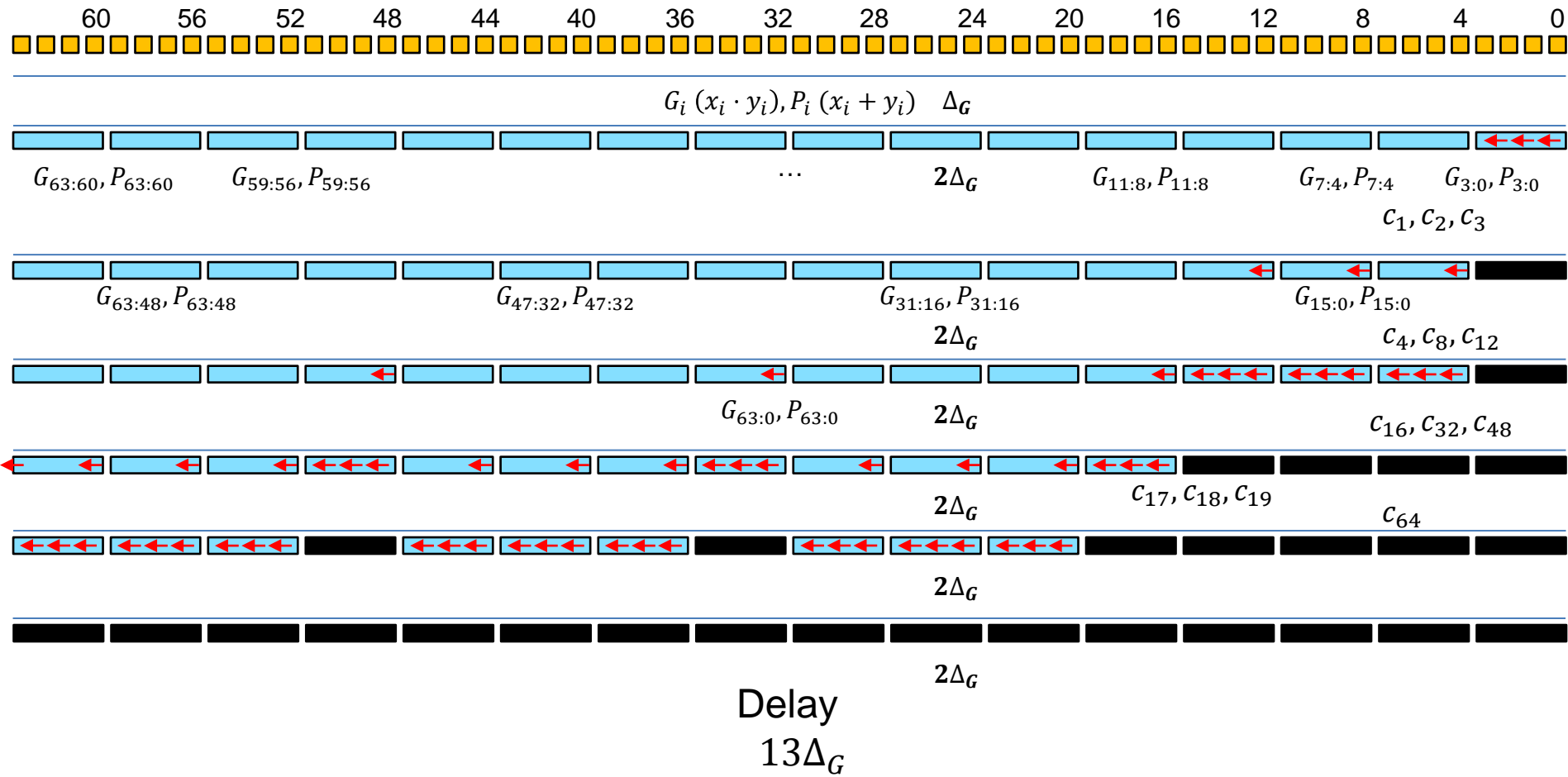


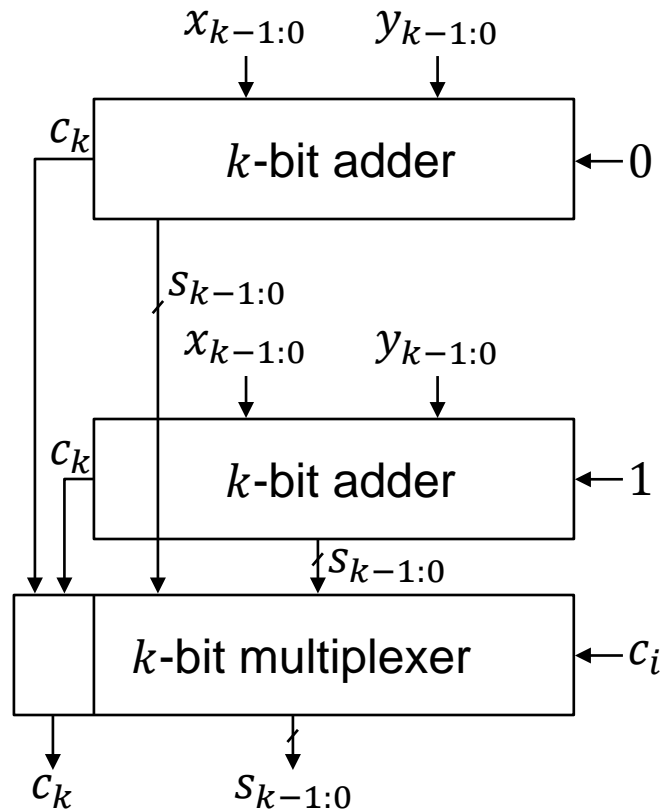
# Conditional Sum Adder

- n-bit conditional sum adder
  - Delay:  $\log(n)$



# Conditional Sum Adder

---