
Advanced Techniques in CMOS Logic Circuits

Dae Hyun Kim

EECS
Washington State University

References

- John P. Uyemura, “Introduction to VLSI Circuits and Systems,” 2002.
 - Chapter 9

Goal


- Understand various advanced logic design techniques
 - Mirror circuits
 - Pseudo-nMOS
 - Tri-state circuits
 - Clocked CMOS
 - Dynamic CMOS
 - Dual-rail logic

Mirror Circuits

- Uses the same transistor topology for the nFET and pFET networks.
- When there are equal numbers of input combinations producing 0s and 1s.
 - XOR
 - XNOR
 - ...
- Advantages
 - More symmetric layouts
 - Shorter rise and fall times


Mirror Circuits

- XOR

 

Traditional static CMOS
 
$$\tau_n = 2R_n C_{out} + R_n C_x$$
$$\tau_p = 2R_p C_{out} + R_p (2C_x)$$




Mirror circuit

$$\tau_n = 2R_n C_{out} + R_n C_x$$
$$\tau_p = 2R_p C_{out} + R_p C_x$$


Mirror Circuits

- XNOR

 

Traditional static CMOS
 
$$\tau_n = 2R_n C_{out} + R_n C_x$$
$$\tau_p = 2R_p C_{out} + R_p (2C_x)$$




Mirror circuit

$$\tau_n = 2R_n C_{out} + R_n C_x$$
$$\tau_p = 2R_p C_{out} + R_p C_x$$


Pseudo-NMOS

 - Ratioed logic
- If the nFET logic is turned off, $F = 1$.
- If the nFET logic is turned on, $F = 0$ (ideally).
- V_{OL} is determined by the resistance ratio between the pFET and the nFETs.
- Smaller, but $V_{OL} > 0$.
- Static power consumption.



Pseudo-NMOS

- Pseudo-NMOS inverter

 

- If $A = 0$: $F = V_{DD}$.

- If $A = 1$

- nFET: $V_{GS} - V_{Tn} = V_{DD} - V_{Tn} > V_{DS} = V_{out}$

- pFET: $V_{SG} - |V_{Tp}| = V_{DD} - |V_{Tp}| < V_{SD} = V_{DD} - V_{out}$


- Linear region.

- $I_{DSn} = \beta_n \left[(V_{DD} - V_{Tn})V_{out} - \frac{1}{2}V_{out}^2 \right] = I_{SDp} = \frac{1}{2}\beta_p (V_{DD} - |V_{Tp}|)^2$

- $V_{OL} = (V_{DD} - V_{Tn}) - \sqrt{(V_{DD} - V_{Tn})^2 - \frac{\beta_p}{\beta_n} (V_{DD} - |V_{Tp}|)^2}$

Tri-State Circuits

 - Tri-state inverter
 - $EN = 1: F = \bar{A}$
 - $EN = 0: F = Z$



Clocked CMOS

- C²MOS