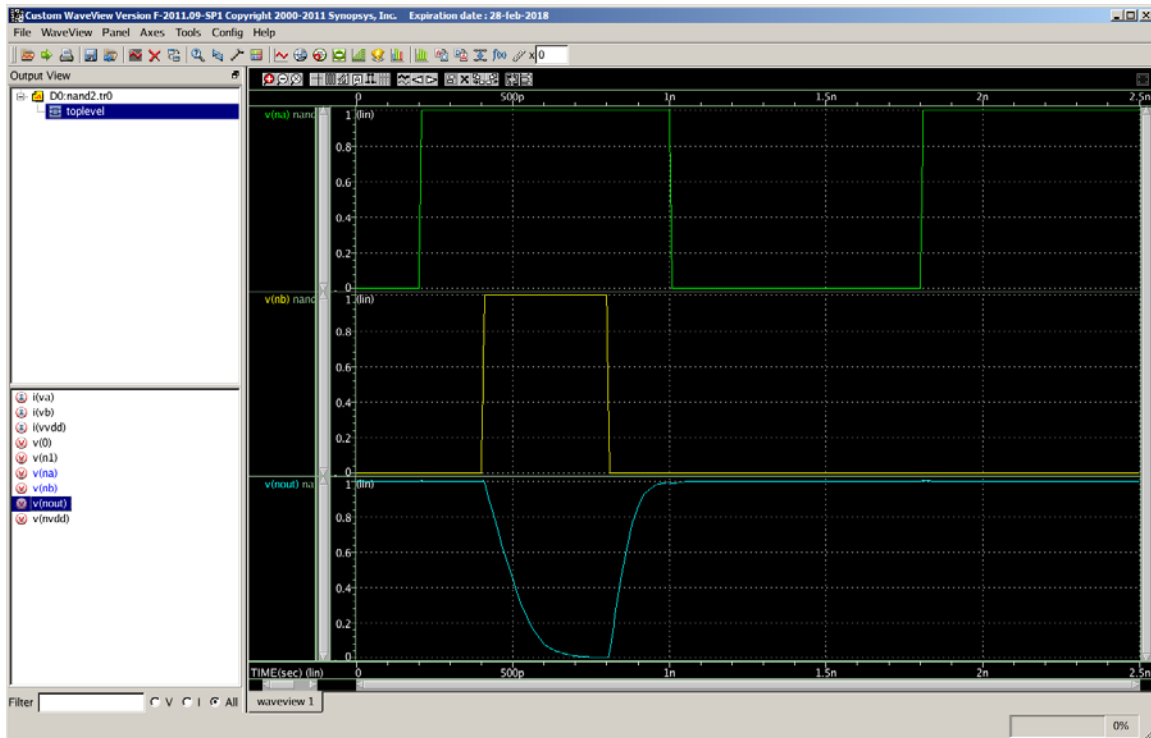



Homework Assignment 3

(Due 5pm, Jan. 26, email to daehyun@eecs.wsu.edu)


- (1) [SPICE, 10 points] Download hw03.zip and unzip it. You will see nand2.sp. Open it in a text editor and see the netlist. It implements a two-input NAND gate. Simulate it using HSpice and see the waveform.
- [Submit] Screen-capture the waveforms of the two inputs (nA and nB) and the output (nOut).



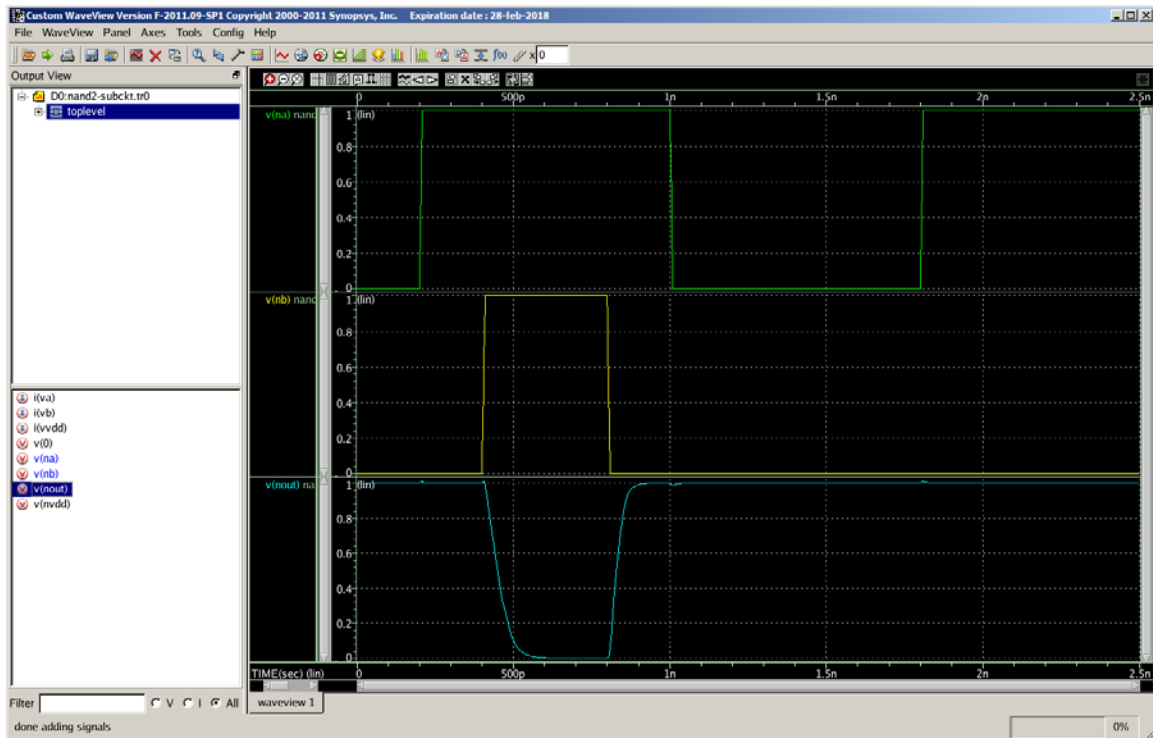- (2) [SPICE, 10 points] Open subckt-nand2.sp in a text editor and see the subckt definition. It defines a subckt for a two-input NAND gate. Now, open nand2-subckt.sp and see how a two-input NAND gate is instantiated. Simulate it using HSpice and see the waveform.
- [Submit] Screen-capture the waveforms of the two inputs (nA and nB) and the output (nOut).



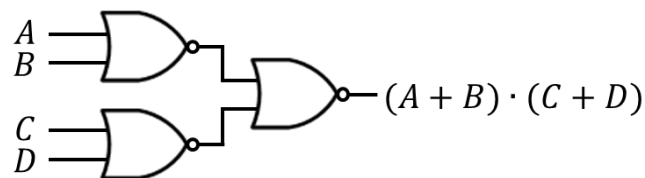- (3) [SPICE, 20 points] Create a subckt for a two-input NOR gate. Use $L=45\text{nm}$ and $W=50\text{nm}$ for the NFETs. Use $L=45\text{nm}$ and $W=300\text{nm}$ for the PFETs. Then, instantiate three two-input NOR gates as follows:



The load capacitance at the output node is 10fF . Generate input signals and simulate all the 16 input combinations (from 0000 to 1111). Make sure the output signal swings between 0 and 1 (if your implementation is not correct, the output might not reach 0V or 1V).

- [Submit] Screen-capture the waveforms of the four inputs (A, B, C, D) and the output. You also need to submit your HSpice netlist files.

```
.subckt myNor2 npA npB npOut npVdd npGnd
mn1 npOut npA npGnd npGnd NMOS_HP L=45n W=50n
mn2 npOut npB npGnd npGnd NMOS_HP L=45n W=50n
mp1 npOut npA n1 npVdd PMOS_HP L=45n W=300n
mp2 n1 npB npVdd npVdd PMOS_HP L=45n W=300n
```

.ends myNor2


* Subckt instantiation (see the port mapping. The order should match the order of the

* port definition of the subckt.


X1 nA nB n1 nVdd 0 myNor2

X2 nC nD n2 nVdd 0 myNor2

X3 n1 n2 nOut nVdd 0 myNor2

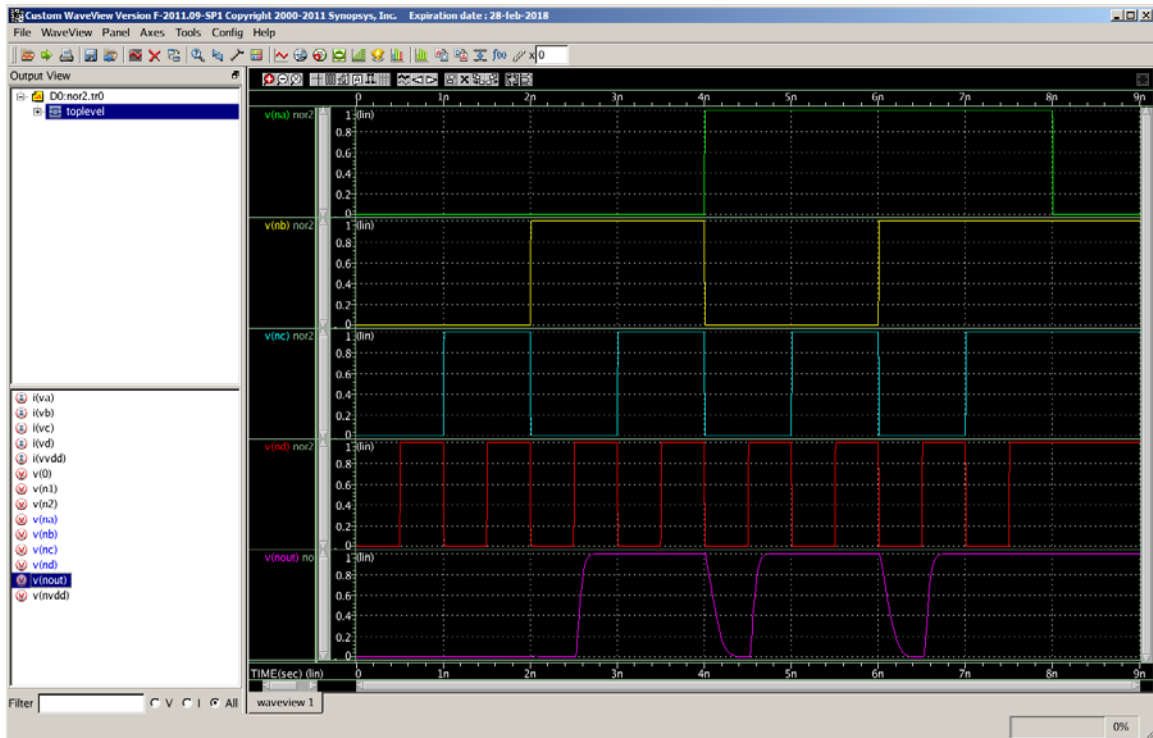

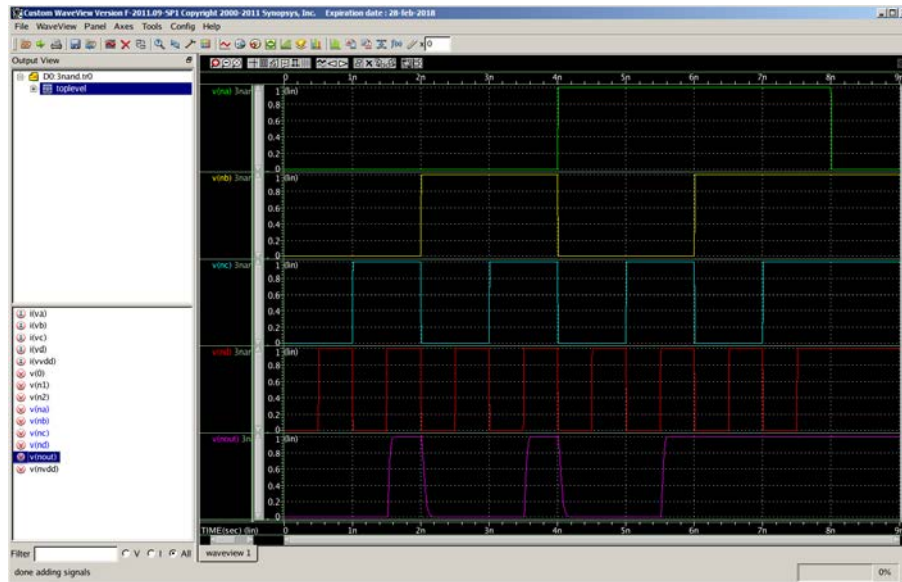- The following shows a sample waveform for $Y = A \cdot B + C \cdot D$.



[Submit] Zip the HSpice netlist for Problem 3 and all the waveforms into “hw03_your_id#.zip” (e.g., hw03_012345678.zip) and submit it by email.