

Homework Assignment 3
(Due 5pm, Jan. 26, email to daehyun@eecs.wsu.edu)


(1) [SPICE, 10 points] Download hw03.zip and unzip it. You will see nand2.sp. Open it in a text editor and see the netlist. It implements a two-input NAND gate. Simulate it using HSpice and see the waveform.

- [Submit] Screen-capture the waveforms of the two inputs (nA and nB) and the output (nOut).

(2) [SPICE, 10 points] Open subckt-nand2.sp in a text editor and see the subckt definition. It defines a subckt for a two-input NAND gate. Now, open nand2-subckt.sp and see how a two-input NAND gate is instantiated. Simulate it using HSpice and see the waveform.


- [Submit] Screen-capture the waveforms of the two inputs (nA and nB) and the output (nOut).

 (3) [SPICE, 20 points] Create a subckt for a two-input NOR gate. Use $L=45\text{nm}$ and $W=50\text{nm}$ for the NFETs. Use $L=45\text{nm}$ and $W=300\text{nm}$ for the PFETs. Then, instantiate three two-input NOR gates as follows:



The load capacitance at the output node is 10fF. Generate input signals and simulate all the 16 input combinations (from 0000 to 1111). Make sure the output signal swings between 0 and 1 (if your implementation is not correct, the output might not reach 0V or 1V).

 - [Submit] Screen-capture the waveforms of the four inputs (A, B, C, D) and the output. You also need to submit your HSpice netlist files.
- The following shows a sample waveform for $Y = A \cdot B + C \cdot D$.



[Submit] Zip the HSpice netlist for Problem 3 and all the waveforms into “hw03_your_id#.zip” (e.g., hw03_012345678.zip) and submit it by email.