

Homework Assignment 5
(Due 5pm, Feb. 2, email to daehyun@eecs.wsu.edu)

- (1) **[Proof, 20 points]** A Boolean function can be expressed as a function of non-inverted and inverted inputs, AND operations, and OR operations as follows:

$$f(x_1, \bar{x}_1, x_2, \bar{x}_2, \dots, x_n, \bar{x}_n, \text{AND}, \text{OR}).$$

For instance, $Y = \overline{x_1 + x_2 \cdot x_3 + \bar{x}_1 \cdot x_2 \cdot \bar{x}_4}$ is a Boolean function. Suppose $F = f(x_1, \bar{x}_1, x_2, \bar{x}_2, \dots, x_n, \bar{x}_n, \text{AND}, \text{OR})$ is expressed in inversion-of-sum-of-product form, i.e.,

$$F = \overline{\sum_{i=1}^s \left(\prod_{j=1}^{p_i} k_{i,j} \right)} \quad (1)$$

where Σ is a sum (OR operations), Π is a product (AND operations), s is the number of product terms, p_i is the number of literals (a literal is a logic variable or its complement) in the i -th product term, and $k_{i,j}$ is the j -th literal in the i -th product term ($k_{i,j} \in \{x_1, \bar{x}_1, x_2, \bar{x}_2, \dots, x_n, \bar{x}_n\}$).

For $Y = \overline{x_1 + x_2 \cdot x_3 + \bar{x}_1 \cdot x_2 \cdot \bar{x}_4}$, for example, s is 3 (there are three product terms $(x_1, x_2 \cdot x_3, \bar{x}_1 \cdot x_2 \cdot \bar{x}_4)$), $p_1 = 1, p_2 = 2, p_3 = 3$, $k_{1,1} = x_1, k_{2,1} = x_2, k_{2,2} = x_3, k_{3,1} = \bar{x}_1, k_{3,2} = x_2, k_{3,3} = \bar{x}_4$.

[Submit] Prove that implementing F in Equation (1) using the static CMOS design style requires maximum K NFETs and K PFETs where K is

$$K = \sum_{i=1}^s p_i.$$

Assume that all the non-inverted and inverted inputs are available for F .

- (2) **[Analysis, 30 points]** The following figures shows the NFET network of a static CMOS logic gate. Y is the output and $A \sim H$ are the inputs of the gate. Derive a Boolean equation as a function of the inputs for the output Y . (Hint: If you want, you can use HSpice to find Y).

