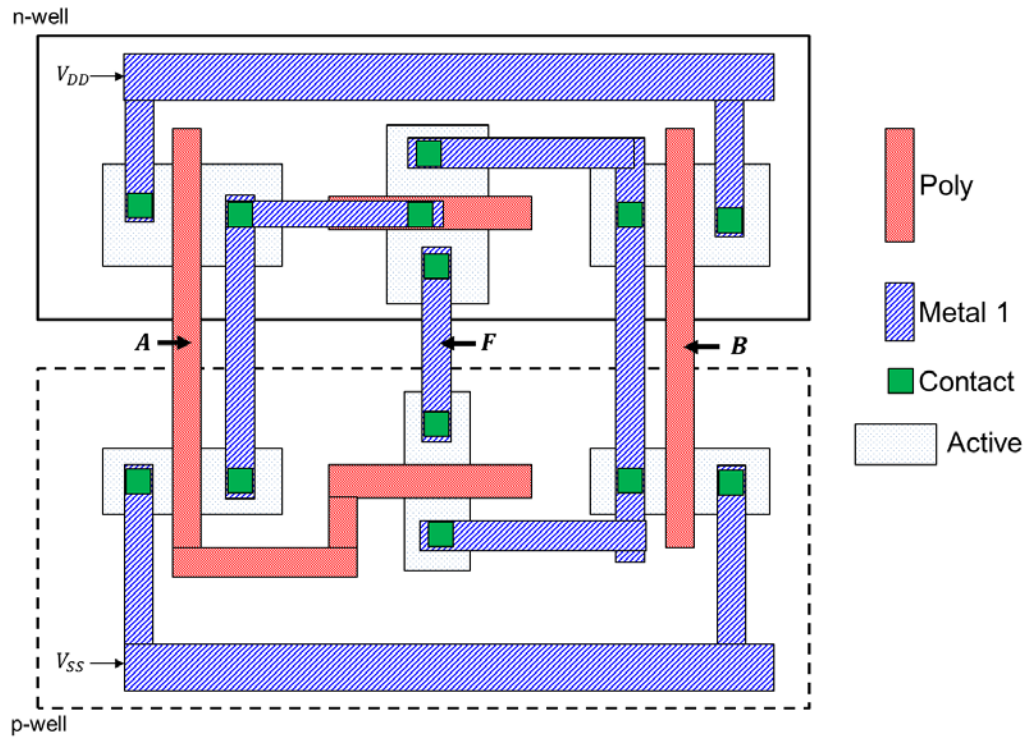


Homework Assignment 10

(Due 4:10pm, Mar. 5, email to daehyun@eecs.wsu.edu)

(1) [Layout, 20 points] Convert the following layout into a transistor-level schematic. Input: A, B. Out: F.



(2) [Layout, 20 points] Convert the following layout into a transistor-level schematic. Input: A, B, C. Out: F.

