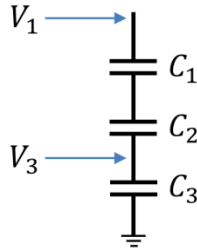


Homework Assignment 15
(Due 4:10pm, Apr. 16, email to daehyun@eecs.wsu.edu)


(1) [Crosstalk, 15 points] Express V_3 as a function of V_1, C_1, C_2, C_3 for the following capacitive network.




The capacitance of the series capacitor composed of C_1 and C_2 is $C_{1,2} = \frac{C_1 C_2}{C_1 + C_2}$.

$$\text{Thus, } V_3 = \frac{C_{1,2}}{C_{1,2} + C_3} V_1 = \frac{\frac{C_1 C_2}{C_1 + C_2}}{\frac{C_1 C_2}{C_1 + C_2} + C_3} V_1 = \frac{C_1 C_2}{C_1 C_2 + C_2 C_3 + C_3 C_1} V_1 = \frac{1}{1 + \frac{C_3}{C_1} + \frac{C_3}{C_2}} V_1$$

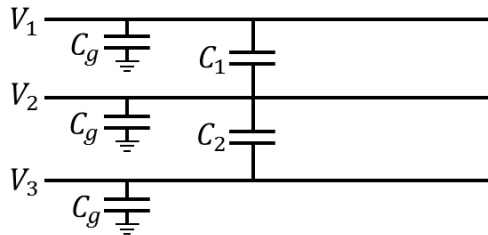(2) [Crosstalk, 15 points] The following shows three nets and their ground and coupling capacitances.



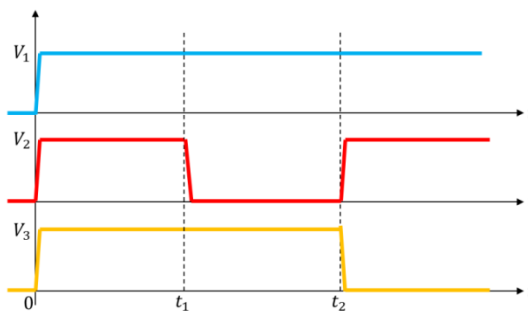The following shows the waveforms of the three nets.



Compute the effective capacitances of V_2 at time $t = 0, t_1, t_2$.

	$t = 0$	$t = t_1$	$t = t_2$
V_2	C_g	$C_g + C_1 + C_2$	$C_g + C_1 + 2C_2$