

*EE 466/586*  
*VLSI Design*

**Partha Pande**  
**School of EECS**  
**Washington State University**  
**pande@eecs.wsu.edu**

## ***Lecture 10***

### ***Propagation delay (Cont'd)***



# *Driving large loads*

- Sometimes, large loads must be driven:
  - off-chip;
  - long wires on-chip.
- Sizing up the driver transistors only pushes back the problem—driver now presents larger capacitance to earlier stage.

# *Sizing Logic Paths for Speed*

- Frequently, input capacitance of a logic path is constrained
- Logic also has to drive some capacitance
- Example: ALU load in an Intel's microprocessor is 0.5pF
- How do we size the ALU datapath to achieve maximum speed?


# Gate Sizing for Optimal Path Delay

  

# *Inverter Characteristics*

- Follow board notes

# Delay of an Inverter

 

$$t_{delay} = R_{eff} [C_{out} + C_{self}]$$


$$t_{delay} \approx R_{eff} C_{in} \left[ \frac{C_{out}}{C_{in}} + \frac{C_{self}}{C_{in}} \right]$$

$$\approx \tau_{inv} \left[ \frac{C_{out}}{C_{in}} + \gamma_{inv} \right]$$

where  $\gamma_{inv}$  is the ratio of self-capacitance to input capacitance for the inverter:

$$\gamma_{inv} = \frac{C_{self}}{C_{in}}$$

# Delay of an inverter chain

 

$$total\_delay = \sum_{j=1}^N \tau_{inv} \left( \frac{C_{j+1}}{C_j} + \gamma_{inv} \right)$$

$$total\_delay = \sum_j \tau_{inv} \left( \frac{C_g W_{j+1}}{C_g W_j} + \gamma_{inv} \right) = \sum_j \tau_{inv} \left( \frac{W_{j+1}}{W_j} + \gamma_{inv} \right)$$




# Scaling up of inverters

$$D_j = \tau_{inv} \left( \frac{W_j}{W_{j-1}} + \gamma_{inv} \right) + \tau_{inv} \left( \frac{W_{j+1}}{W_j} + \gamma_{inv} \right)$$


$$\frac{\partial D_j}{\partial W_j} = \tau_{inv} \frac{W_j}{W_{j-1}} - \tau_{inv} \frac{W_{j+1}}{W_j} = 0$$

$$\therefore \frac{W_j}{W_{j-1}} = \frac{W_{j+1}}{W_j}$$
 
$$\therefore W_j = \sqrt{W_{j+1} W_{j-1}}$$



# Cascaded driver circuit

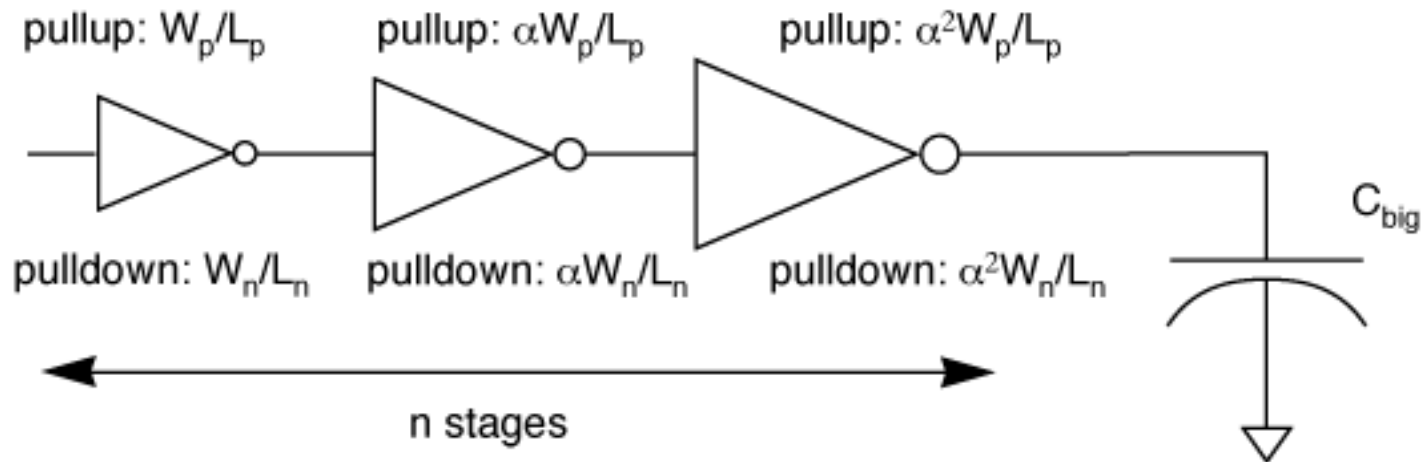

# Optimum Delay

$$f^N C_{IN} = C_{load}$$


$$\therefore N = \frac{\ln(C_{load} / C_{IN})}{\ln f}$$

$$gate\_delay = \tau_{inv} \left( \frac{C_j}{C_{j-1}} + \gamma_{inv} \right)$$

$$total\_delay = N \times \tau_{inv} \left( \frac{C_j}{C_{j-1}} + \gamma_{inv} \right)$$


$$total\_delay = \frac{\ln(C_{load} / C_{IN})}{\ln f} \times \tau_{inv} (f + \gamma_{inv})$$

# Optimal Sizing - FO4 Concept

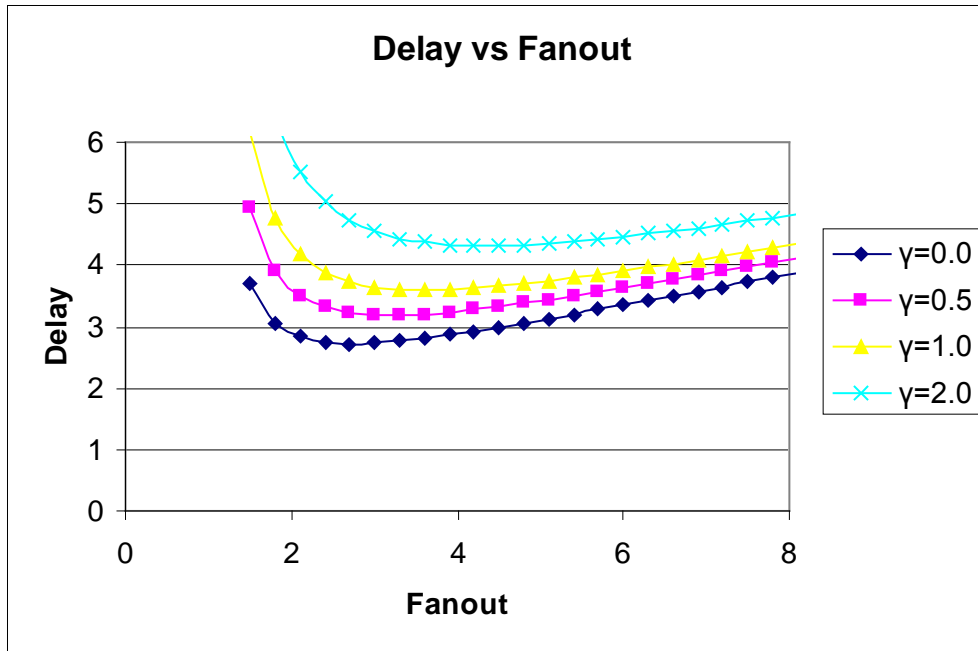

where  $\gamma$  is ratio of  
**Parasitic output  
Capacitance to gate  
capacitance**


Use FO4 delay  
as optimal delay

 


# Older Technology

- ❑ In older technologies, the optimal value of  $f$  was found to be  $e$ , the exponential value.
- ❑ Using the previous formulation, it is clear that this value is obtained when  $\gamma=0$  which implies that the junction capacitance is ignored.
- ❑ The junction capacitance and interconnect capacitance can act to increase the needed drive of the inverter.
- ❑ In a  $0.13\mu\text{m}$  technology,  $\gamma=0.5$ . Therefore, the use of  $f=3$  or  $f=4$  is more suitable in today's technology.

# Clock cycle trend

 

(a)

 

(b)

