

EE 466/586
VLSI Design


Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 13
More on Gates

CMOS Properties


- ❑ Full rail-to-rail swing; **high noise margins**
- ❑ Logic levels not dependent upon the relative device sizes; **ratio less**
- ❑ Always a path to Vdd or Gnd in steady state; **low output impedance**
- ❑ Extremely **high input resistance**; nearly zero steady-state input current
- ❑ No direct path between power and ground; **no static power dissipation**
- ❑ Propagation delay function of load capacitance and resistance of transistors
- ❑ N fan-in gates need 2N transistors

Ratioed Logic

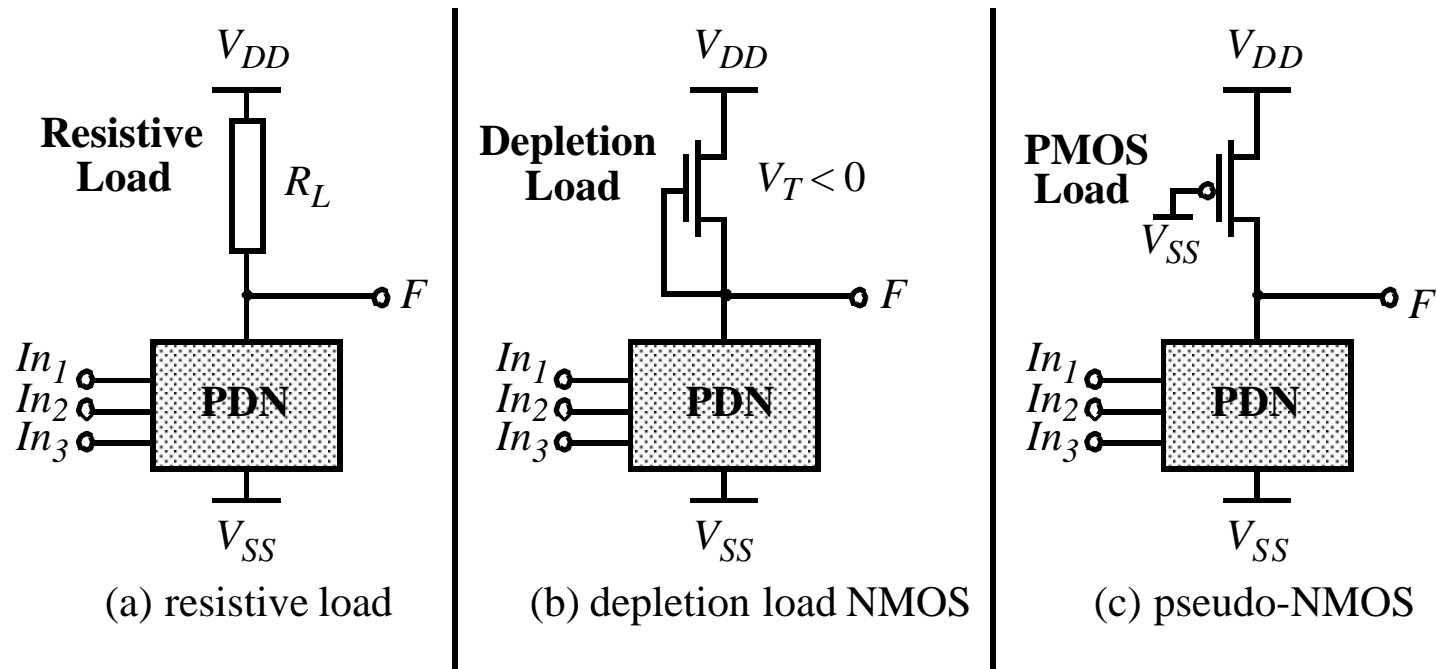


Goal: to reduce the number of devices over complementary CMOS

Ratioed Logic

 


- **N transistors + Load**
- $V_{OH} = V_{DD}$
- $V_{OL} = \frac{R_{PN}}{R_{PN} + R_L}$
- **Assymetrical response**
- **Static power consumption**
- $t_{pL} = 0.69 R_L C_L$

Active Loads

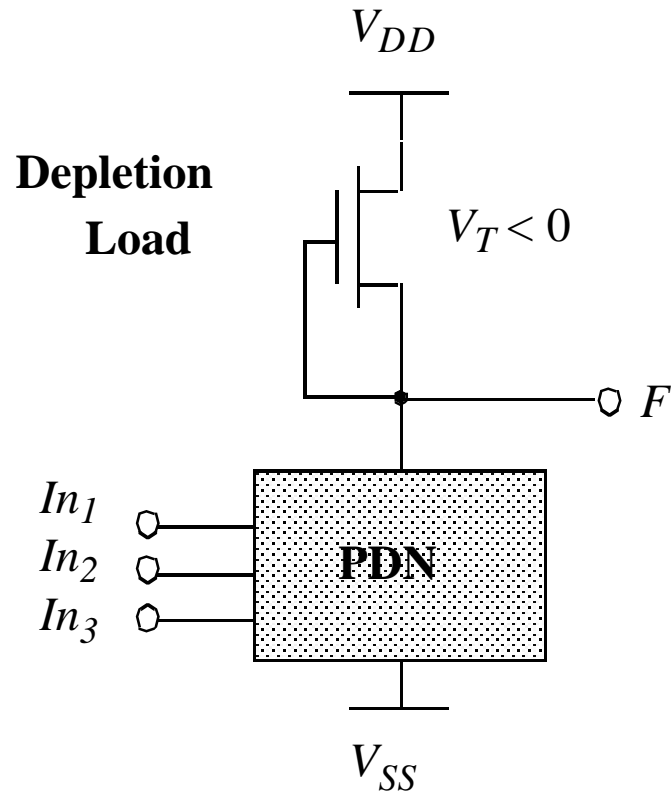


depletion load NMOS

 

pseudo-NMOS

Pseudo-NMOS

 


$$V_{OH} = V_{DD} \text{ (similar to complementary CMOS)}$$

$$k_n \left((V_{DD} - V_{Tn}) V_{OL} - \frac{V_{OL}^2}{2} \right) = \frac{k_p}{2} (V_{DD} - |V_{Tp}|)^2$$

$$V_{OL} = (V_{DD} - V_T) \left[1 - \sqrt{1 - \frac{k_p}{k_n}} \right] \text{ (assuming that } V_T = V_{Tn} = |V_{Tp}|)$$

SMALLER AREA & LOAD BUT STATIC POWER DISSIPATION!!!


Pseudo-NMOS VTC

 

Performance of pseudo-NMOS Inverter


Size	$V_{OL}(V)$	Static Power Dissipation	t_{plh}
4	0.693	564 μW	14 ps
2	0.273	298 μW	56 ps
1	0.133	160 μW	123 ps
0.5	0.064	80 μW	268 ps
0.25	0.031	41 μW	569 ps

Improved Loads

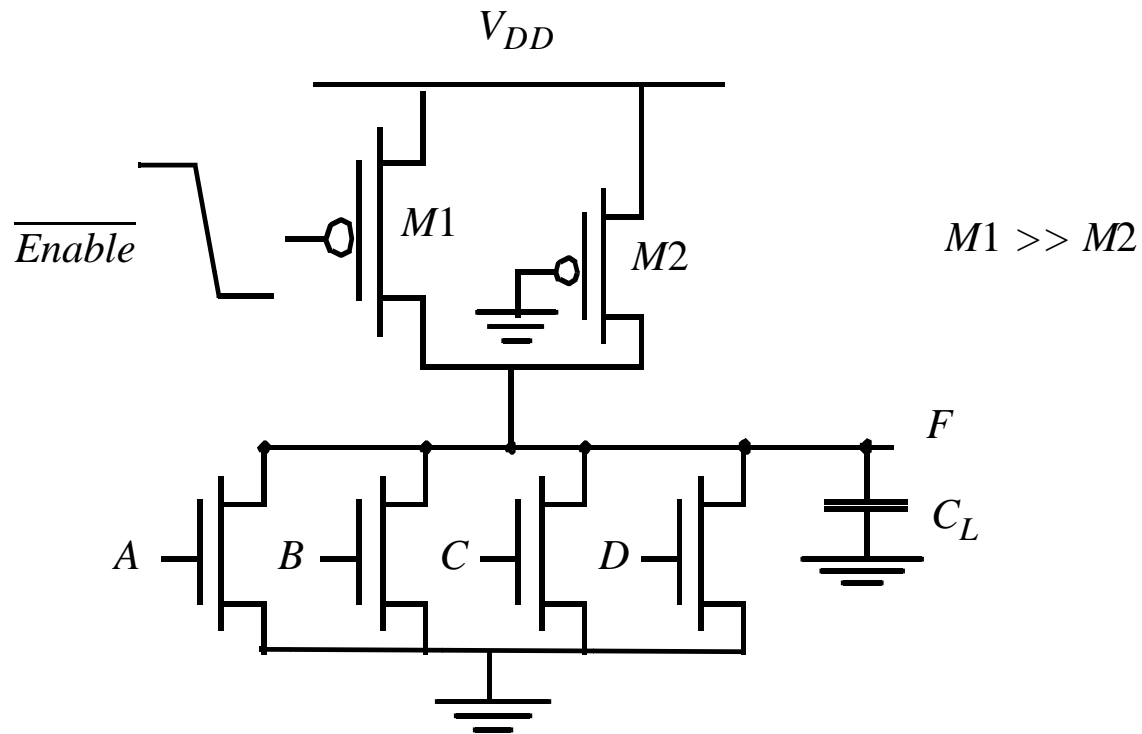


Adaptive Load

Improved Loads (2)

 

Differential Cascode Voltage Switch Logic (DCVSL)

DCVSL Example

 

XOR-NXOR gate