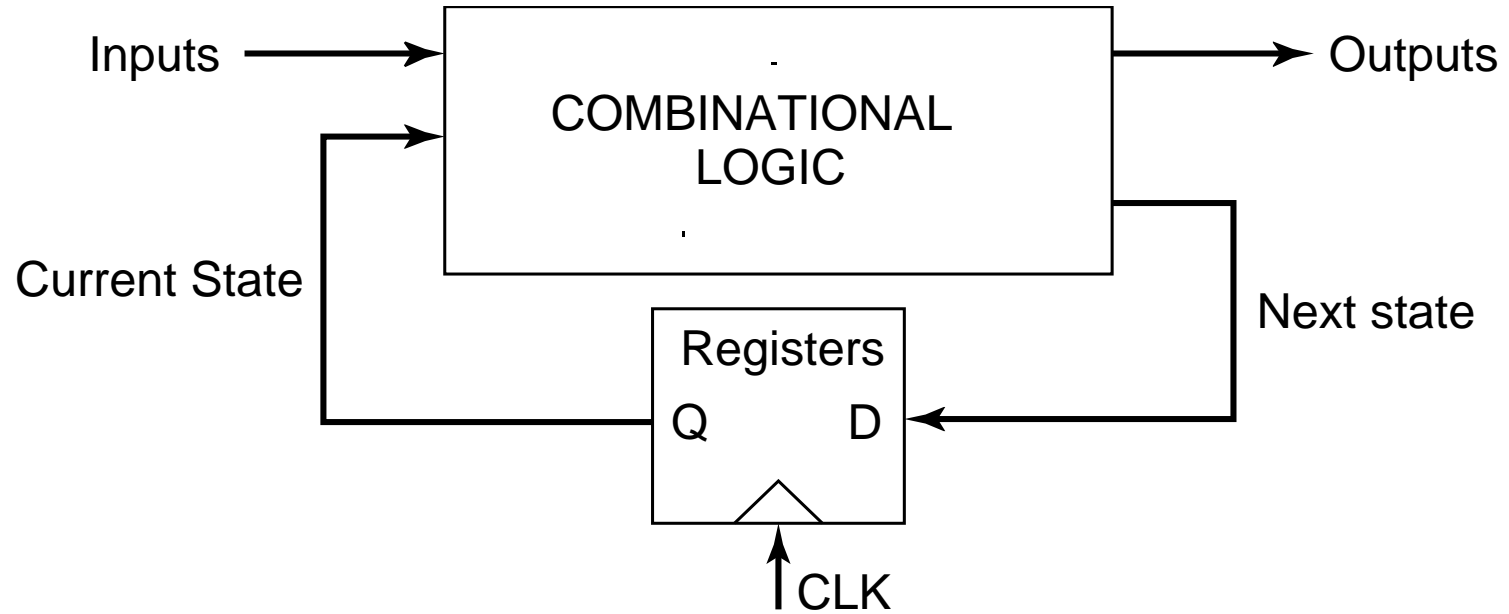


EE 466/586
VLSI Design

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 16
Sequential Logic

Sequential Logic



2 storage mechanisms



- positive feedback
- charge-based

A latch is level sensitive



A register is edge-triggered

Latch versus Register

  - Latch Stores data depending on the level of the clock





- Register stores data when clock rises

 
 


Latches

Positive Latch

  


Negative Latch

  



Latch-Based Design

- N latch is transparent when $\phi = 0$

- P latch is transparent when $\phi = 1$

 


Timing Definitions

  

Timing Definitions


- ❑ T_{su} (Setup time)
 - Incoming data must be stable before the clock arrives
- ❑ T_{hold} (Hold time)
 - The length of time the data remains stable after the clock arrives for proper operation
- ❑ If the data is stable before the setup time and continues to be stable after the hold time, the register will properly capture the data
- ❑ T_{clk-Q} (clk to Q delay)
 - This is the delay from the time the clock arrives to the point at which the Q output stabilizes

Maximum Clock Frequency


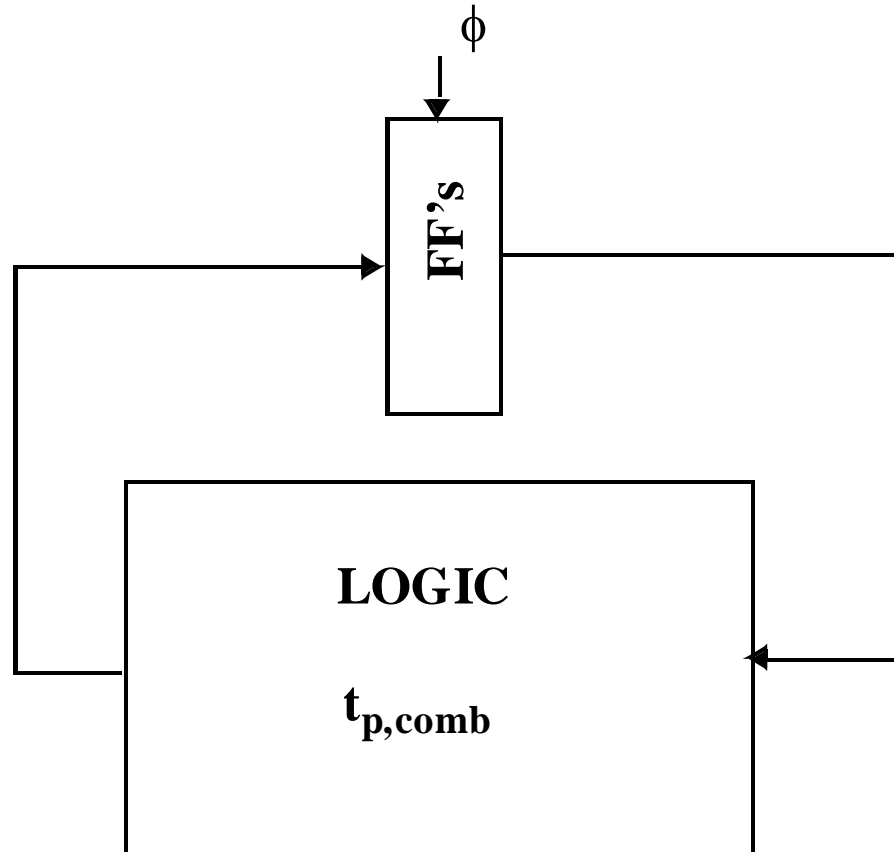


$$t_{clk-Q} + t_{p,comb} + t_{setup} = T$$

Positive Feedback: Bi-Stability

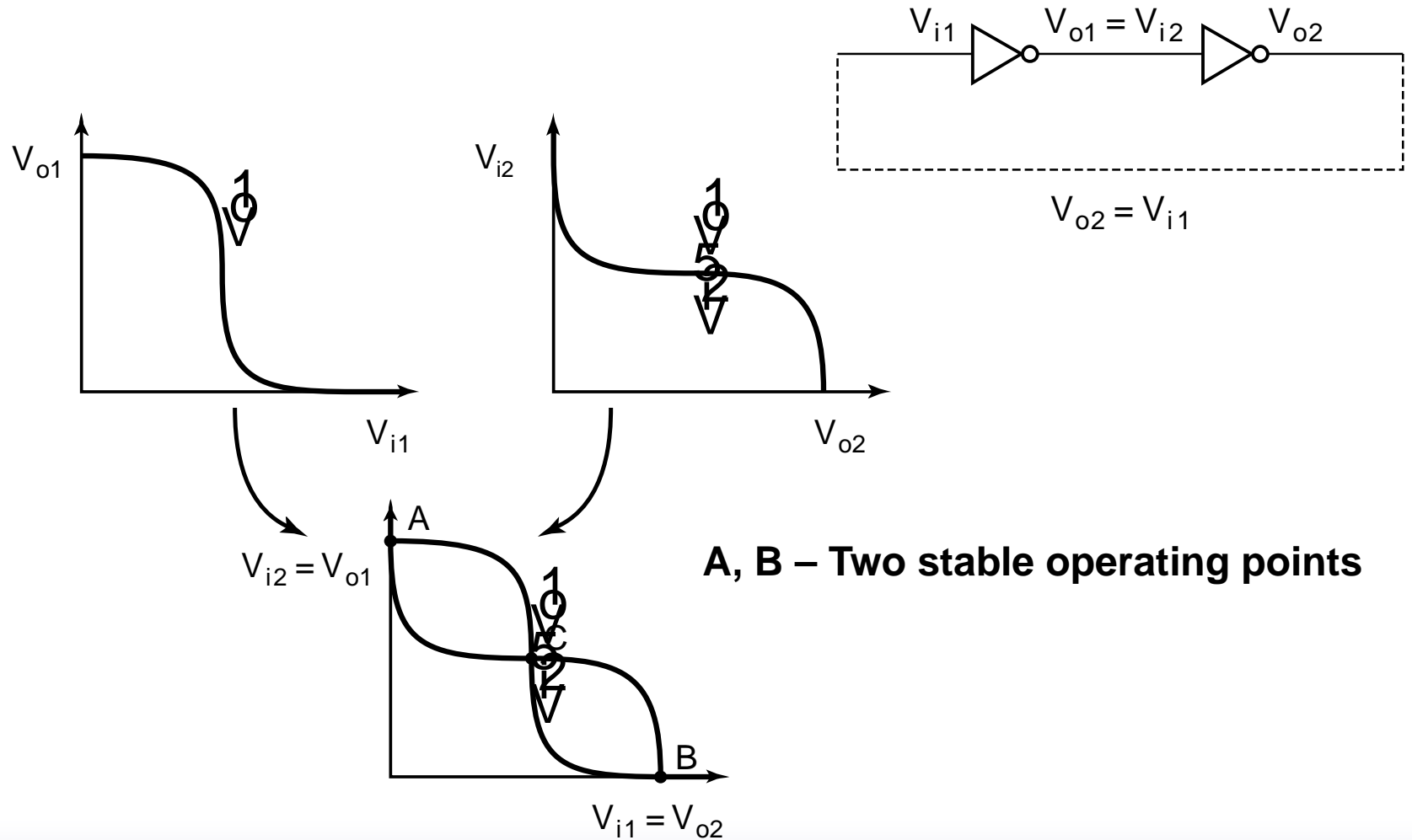



Meta-Stability

  

Gain should be larger than 1 in the transition region

Cross-Coupled Pairs

NOR-based set-reset

 
 


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State

Cross-Coupled NAND

Cross-coupled NANDs

  


This is not used in datapaths any more,
but is a basic building memory cell

Design of D-Latch

- Follow board notes


Storage Mechanisms

Static

 


Need a feedback loop to hold the data

Dynamic (charge-based)


 


Making a Dynamic Latch Pseudo-Static

 

Writing into a Static Latch

  
Use the clock as a decoupling signal, that distinguishes between the transparent and opaque states



Converting into a MUX


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 


$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Positive latch
(transparent when CLK= 1)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$


Mux-Based Latch

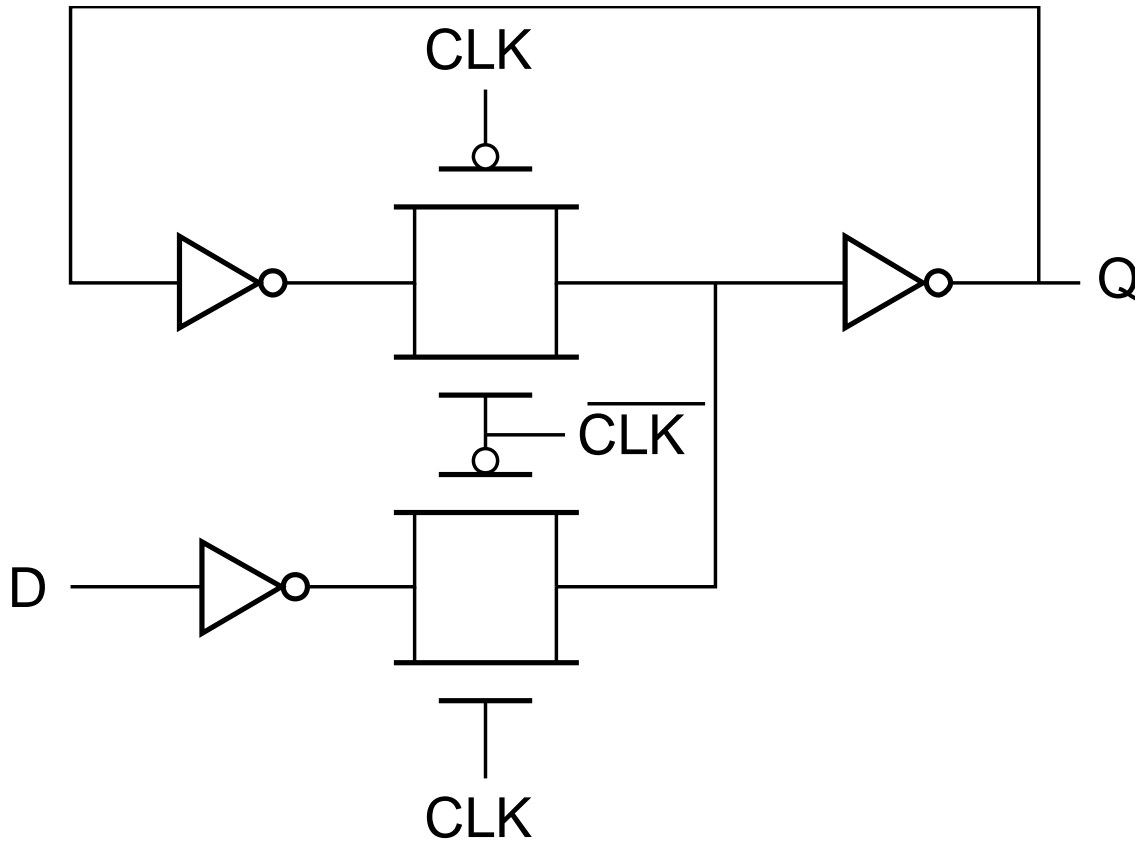

Mux-Based Latch

 


NMOS only

 

Non-overlapping clocks


Master-Slave (Edge-Triggered) Register

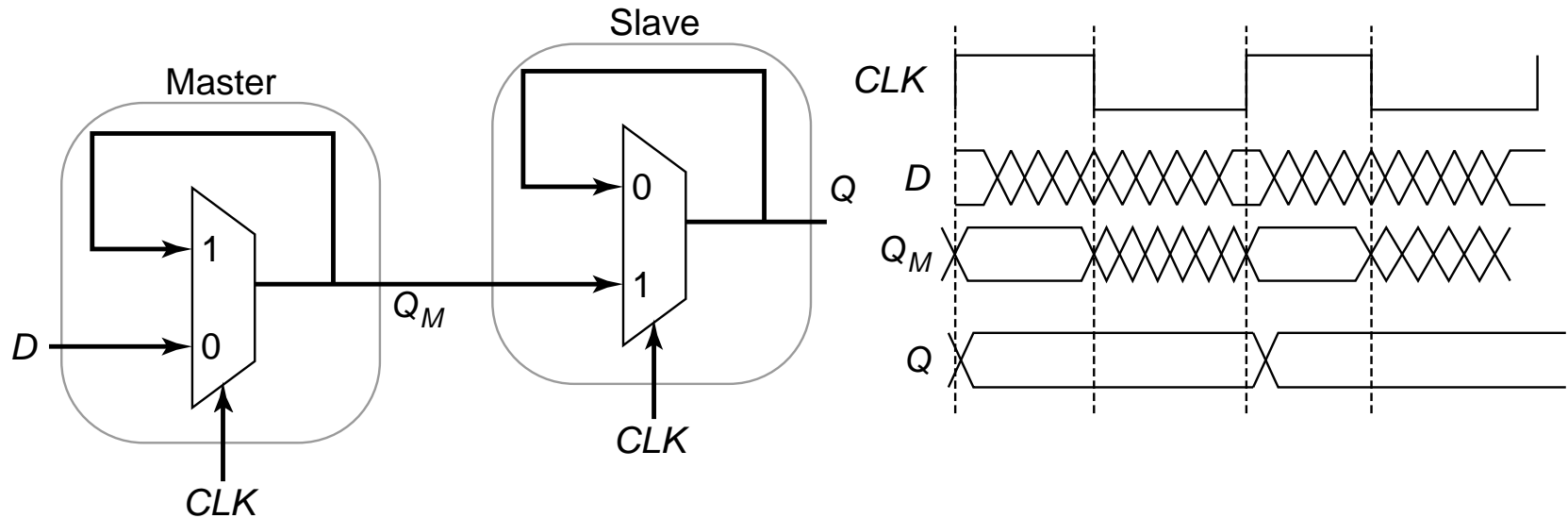


Two opposite latches trigger on edge
Also called master-slave latch pair

Master-Slave Register


Multiplexer-based latch pair

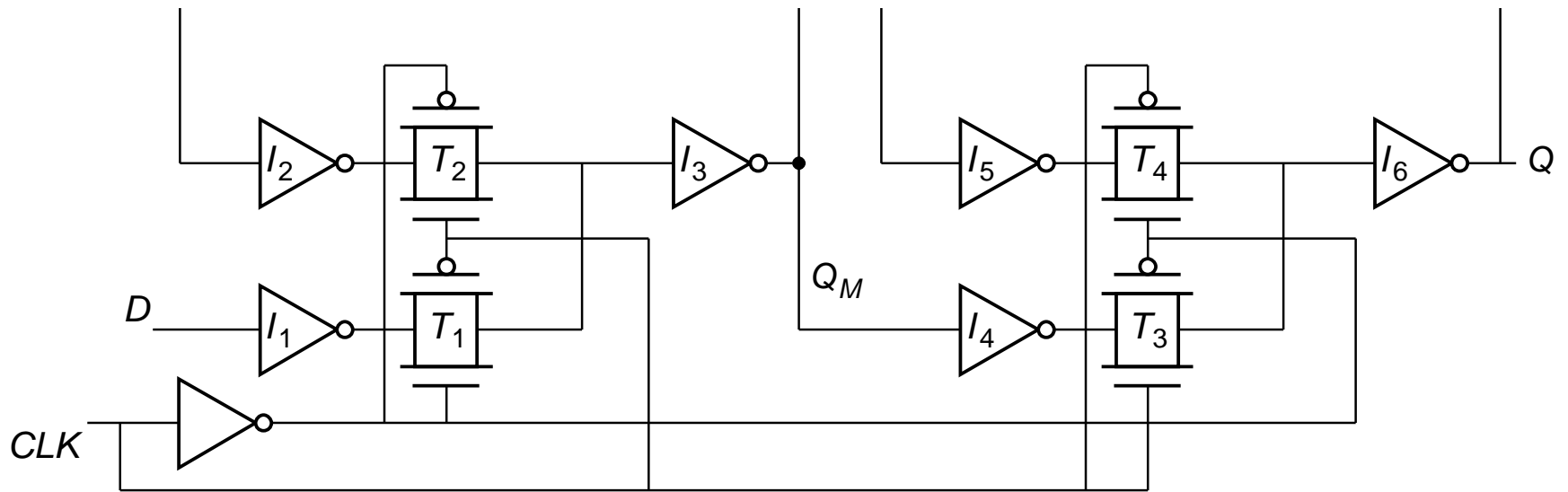


Reduced Clock Load Master-Slave Register

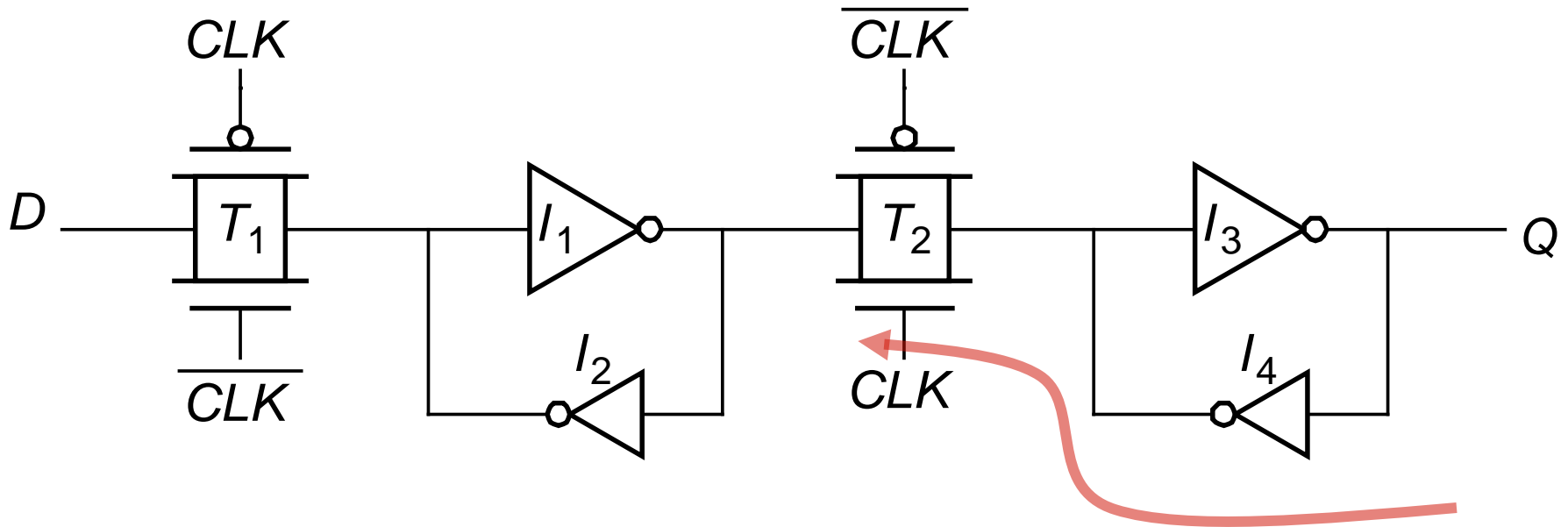

Avoiding Clock Overlap

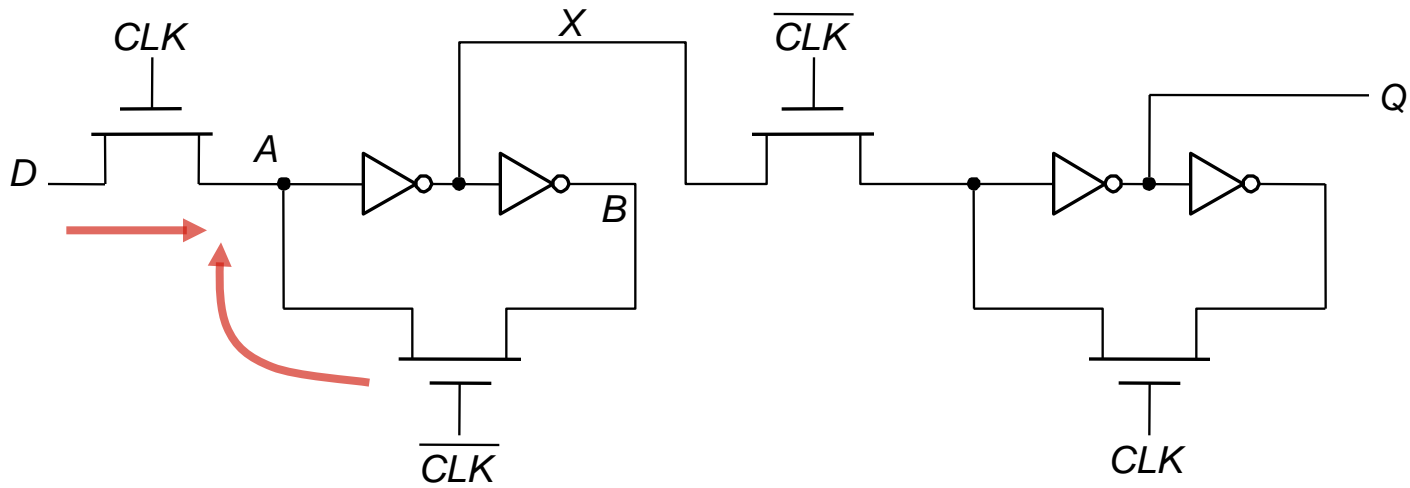

(a) Schematic diagram

 

(b) Overlapping clock pairs