


EE 466/586
VLSI Design

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 17

Sequential Logic (Cont'd)

Dynamic Latches and Registers

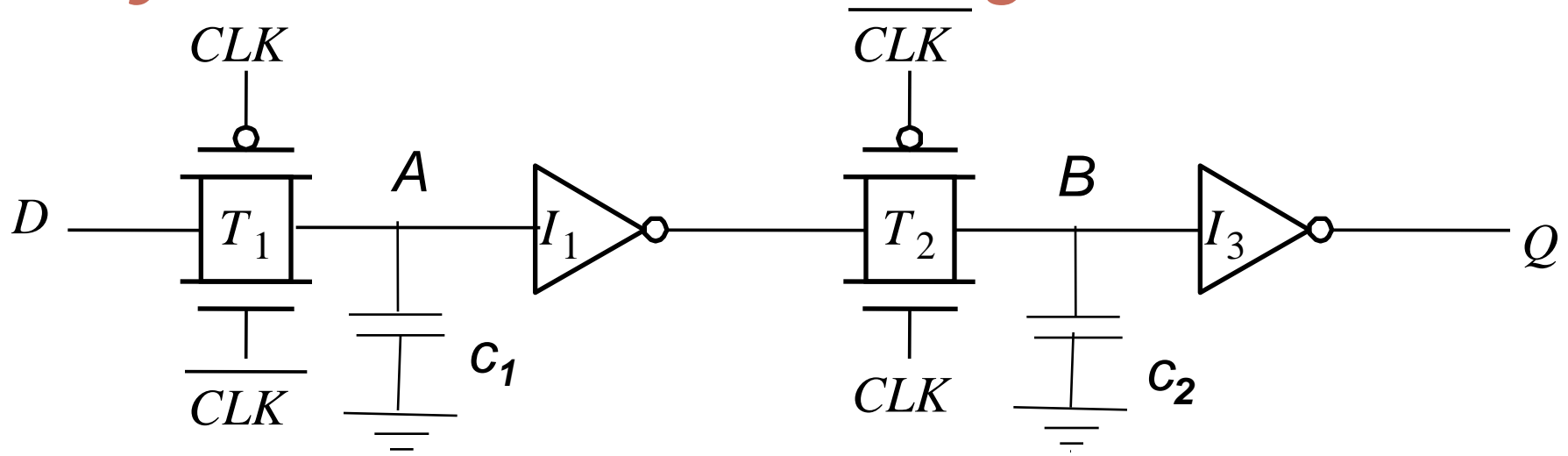

- ❑ The setup time of this circuit is the delay of the transmission gate.
- ❑ It is the time taken by node A to sample the D input.
- ❑ The hold time is approximately zero, as the T_1 is turned off on the clock edge and further input changes are ignored.
- ❑ The propagation delay (**tc-q**) is equal to two inverter delays plus the delay of T_2 .

Clock Overlap

- ❑ During the 0-0 overlap period, the PMOS of T_1 and the PMOS of T_2 are simultaneously on
 - A direct path for data to flow from the D input of the register to the Q output
 - Race condition
- ❑ The output Q can change on the falling edge if the overlap period is large
 - Undesirable effect for a positive edge triggered register.
- ❑ For 1-1 overlap region
 - Path exists through NMOS of T_1 and the NMOS of T_2 .

Clock Overlap (Cont'd)


□ 1-1 Overlap

- Taken care of by enforcing a *hold time* constraint.
- Data must be stable during the high-overlap period.

□ 0-0 Overlap


- Make sure that there is enough delay between the D input and node B
- Ensure that the new data sampled by the master stage does not propagate through to the slave stage.

Other Latches/Registers: C²MOS

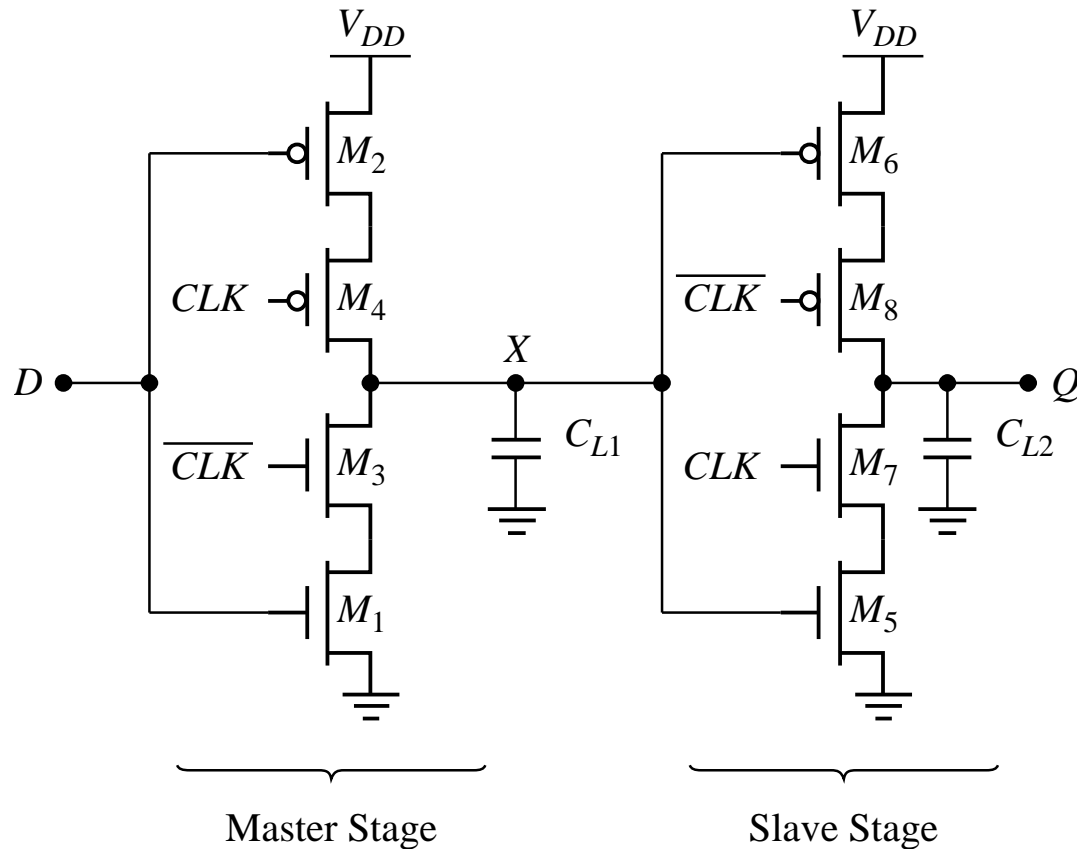


“Keepers” can be added to make circuit pseudo-static

Inensitive to Clock-Overlap

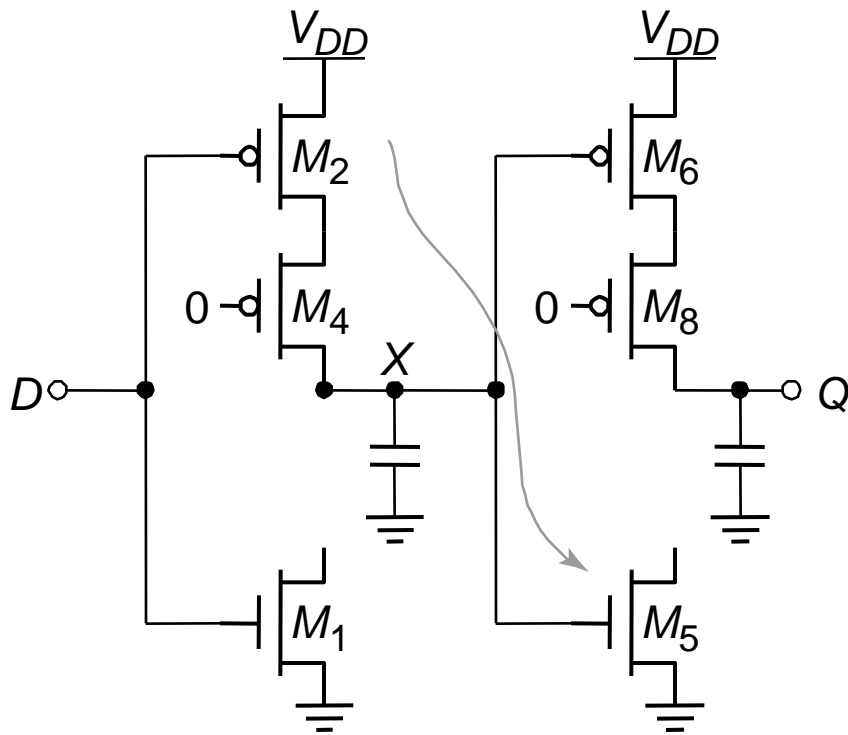


(a) (0-0) overlap

 


(b) (1-1) overlap

Other Latches/Registers: TSPC

 

Positive latch


(transparent when CLK= 1)

 


Negative latch

(transparent when CLK= 0)

Including Logic in TSPC

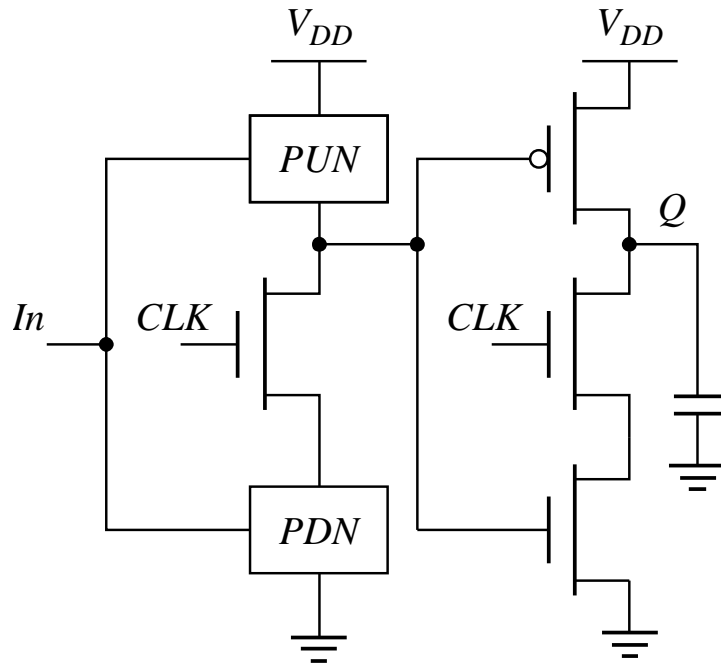


Example: logic inside the latch

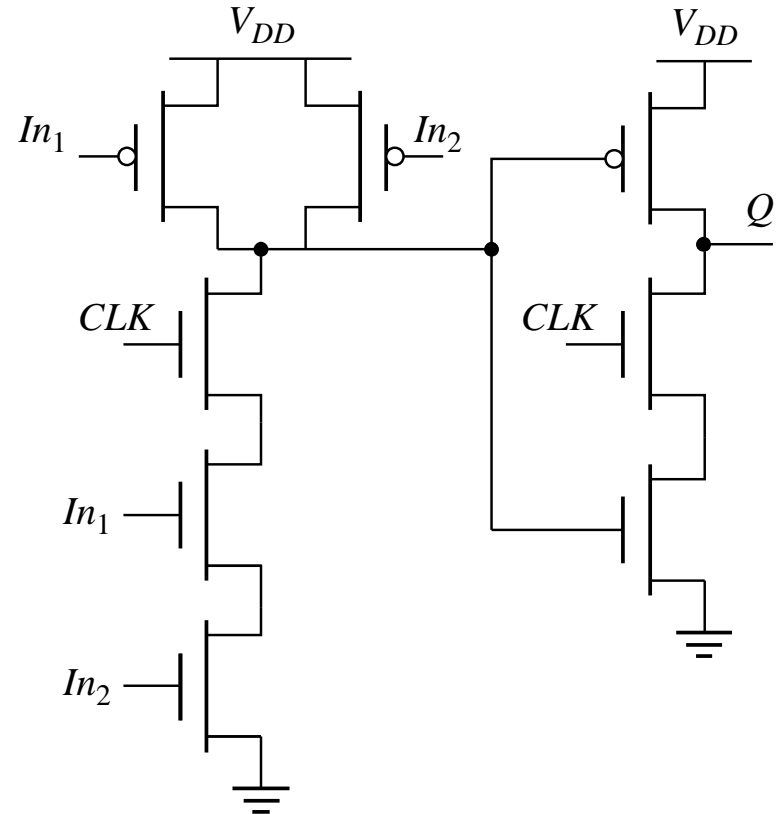

AND latch

TSPC Register

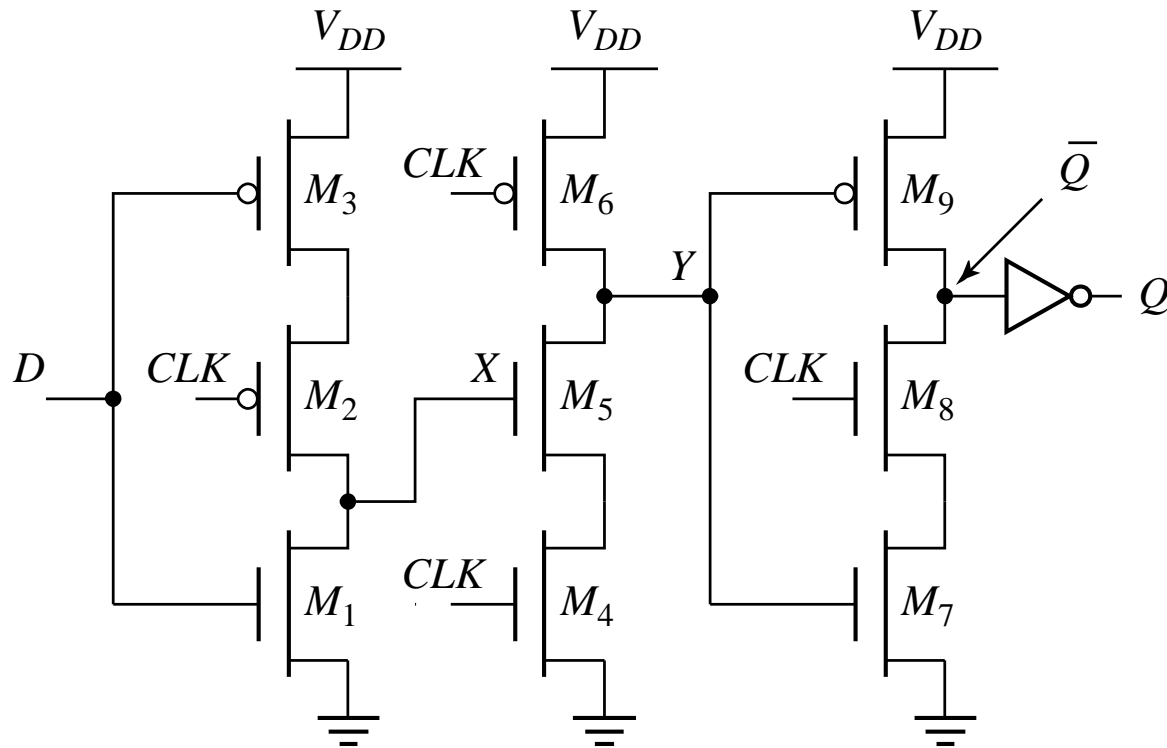


Pulse-Triggered Latches


An Alternative Approach

Ways to design an edge-triggered sequential cell:


Master-Slave
Latches

 


Pulse-Triggered
Latch

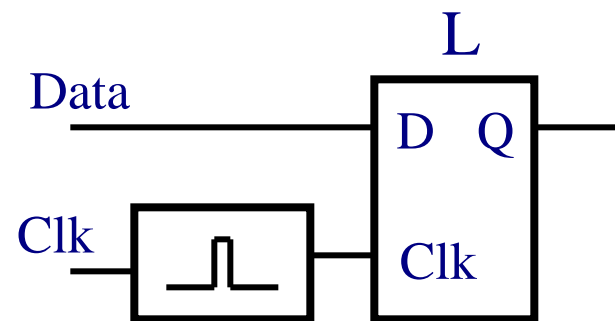


Pulsed Latches

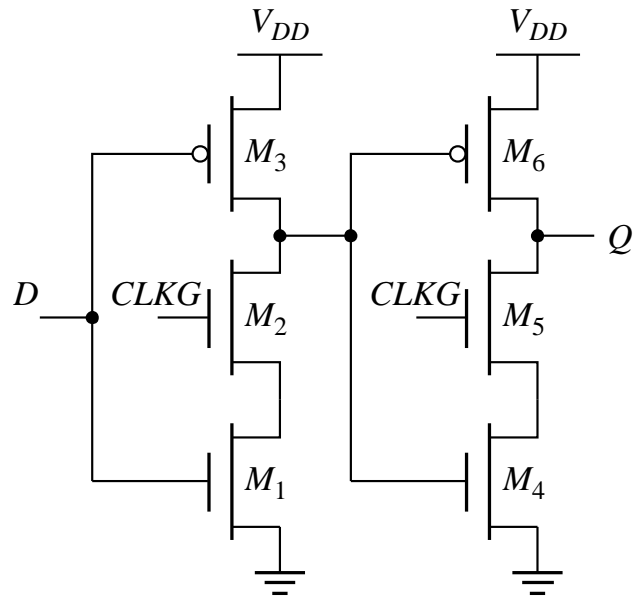

(a) register

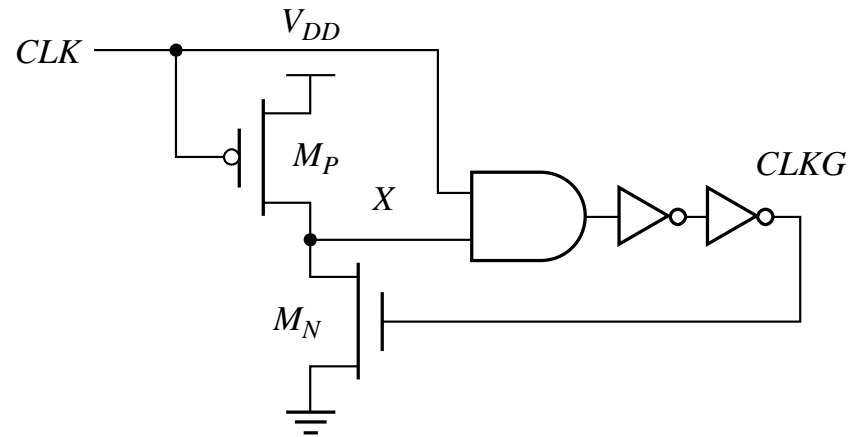


(b) glitch generation

 

 
(c) glitch clock

Pulsed Latches

Hybrid Latch - Flip-flop (HLFF), AMD K-6 and K-7 :



Hybrid Latch-FF Timing

 

Latch-Based Pipeline

