


EE 466/586
VLSI Design

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 22


Arithmetic circuits (Cont'd)

Manchester Carry Chain

 


- ❑ The propagate path passes C_i to C_o output if the propagate signal is true
- ❑ If the propagate condition is not satisfied, the output is either pulled low by the D_i signal or pulled up by \overline{G}_i

Manchester Carry Chain

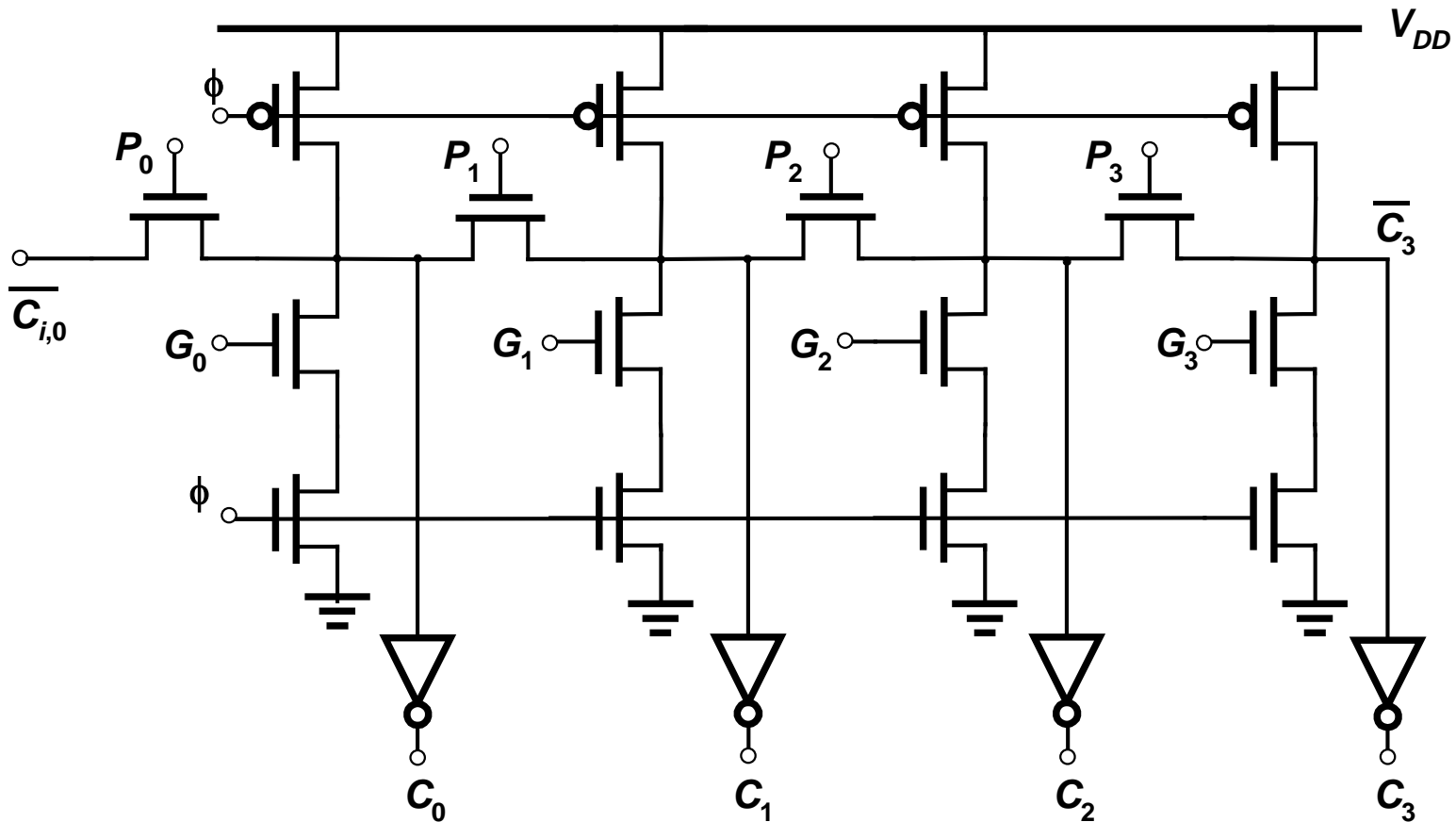


Carry-Bypass Adder

Also called
Carry-Skip

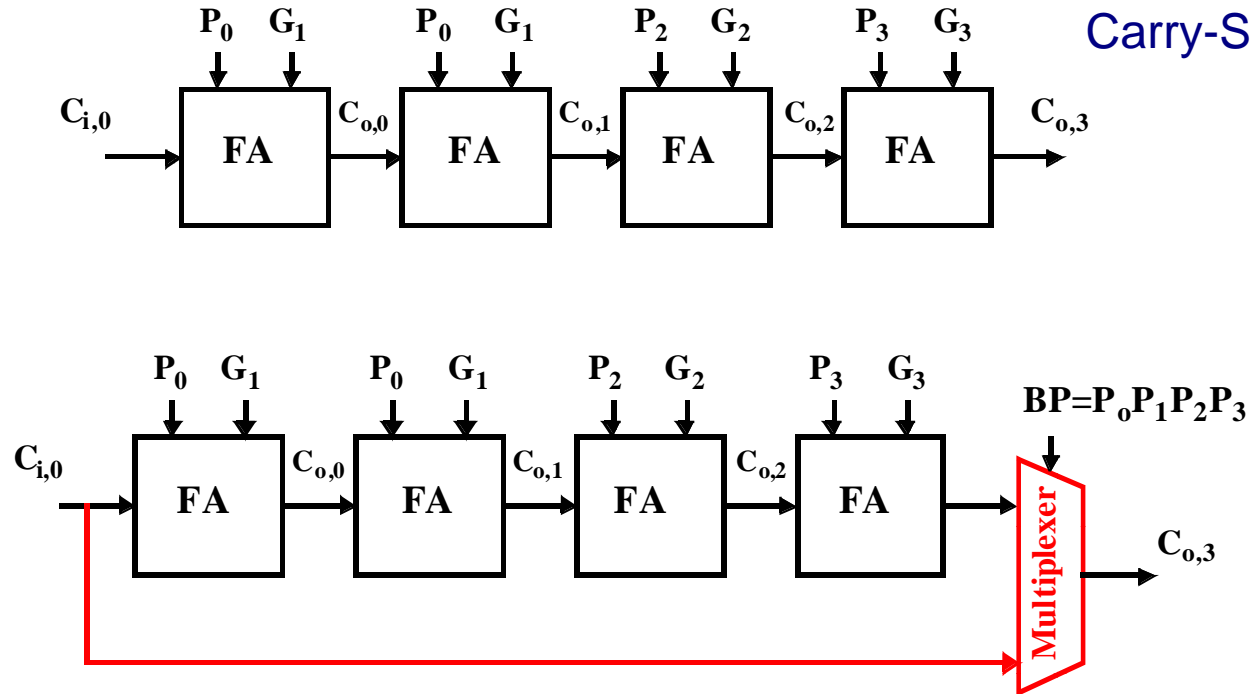

Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$)
then $C_{o3} = C_0$, else “kill” or “generate”.

Carry-Bypass Adder (cont.)

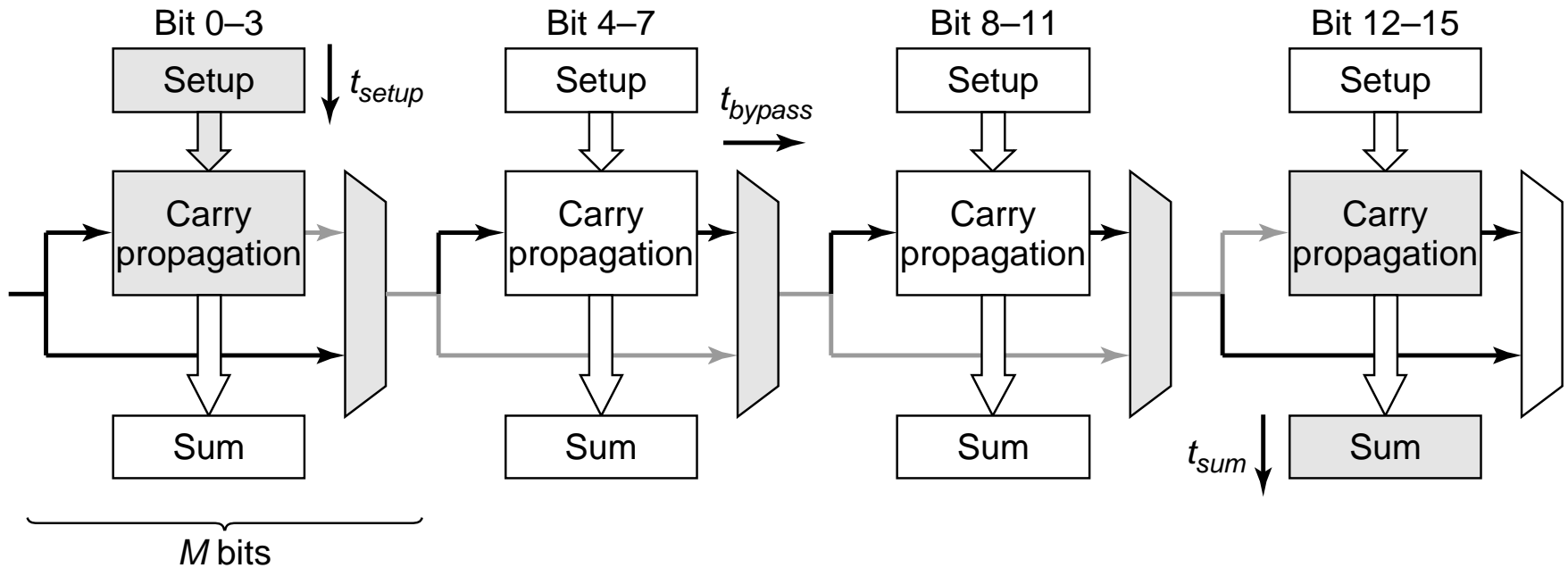


Carry-Bypass Adder (cont.)

- Total adder is divided into (N/M) length bypass stages, each of which contains M bits.

$$t_{adder} = t_{setup} + Mt_{carry} + (N/M-1)t_{bypass} + t_{sum}$$

- t_{setup} = Fixed overhead time to create the generate and propagate signals
- t_{carry} = Propagation delay through a single bit. The worst case carry propagation delay through a single stage of M bits is approximately M times larger.
- t_{bypass} = the propagation delay through the bypass multiplexer of a single stage.
- t_{sum} = the time to generate the sum of the final stage.


Carry Ripple versus Carry Bypass

 


Linear Carry-Select Adder

- ❑ Anticipate both possible values of the carry input and evaluate the result for both possibilities in advance.
- ❑ Once the real value of the incoming carry is known, the correct result is selected with a multiplexer stage.


Carry-Select Adder

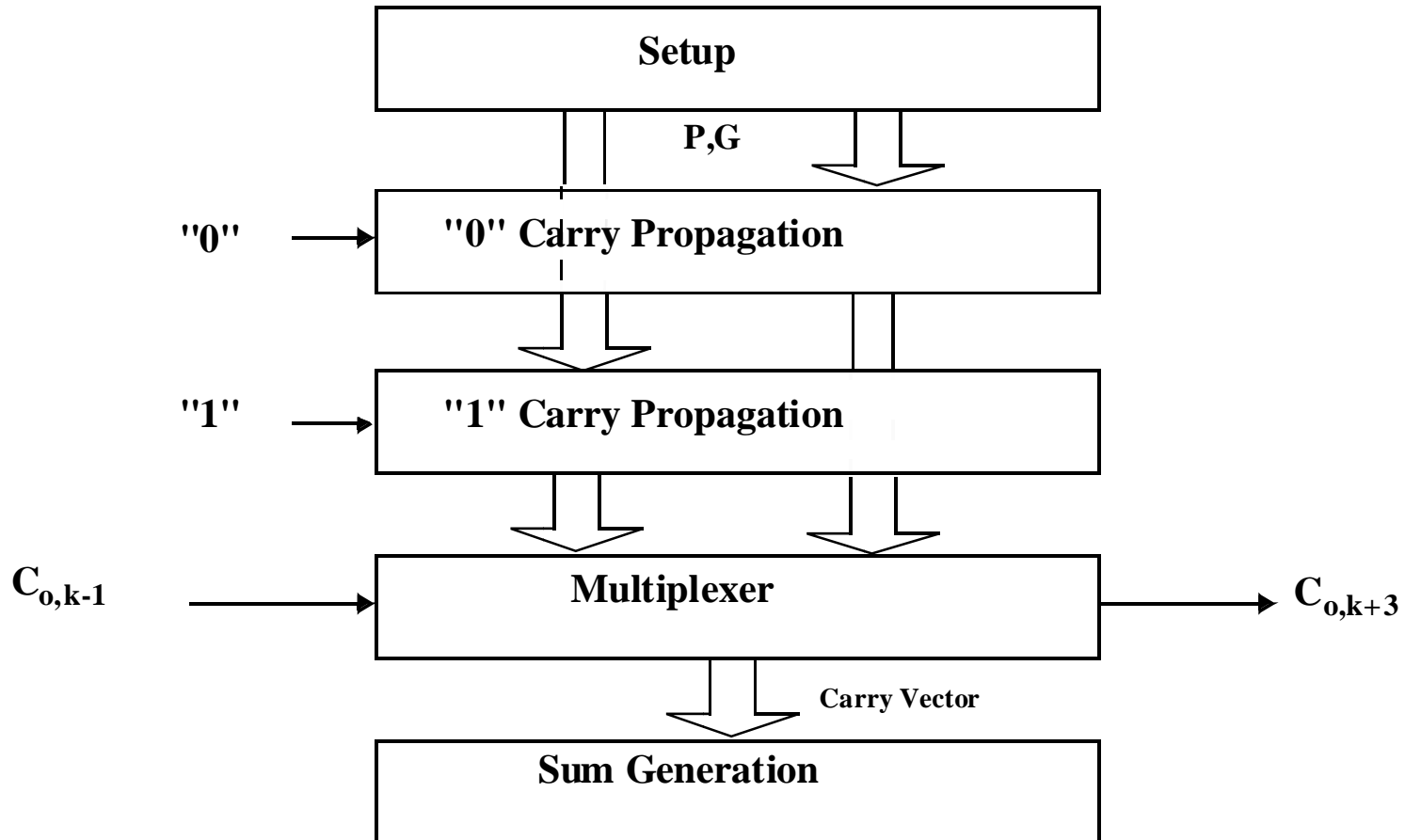


Carry Select Adder: Critical Path

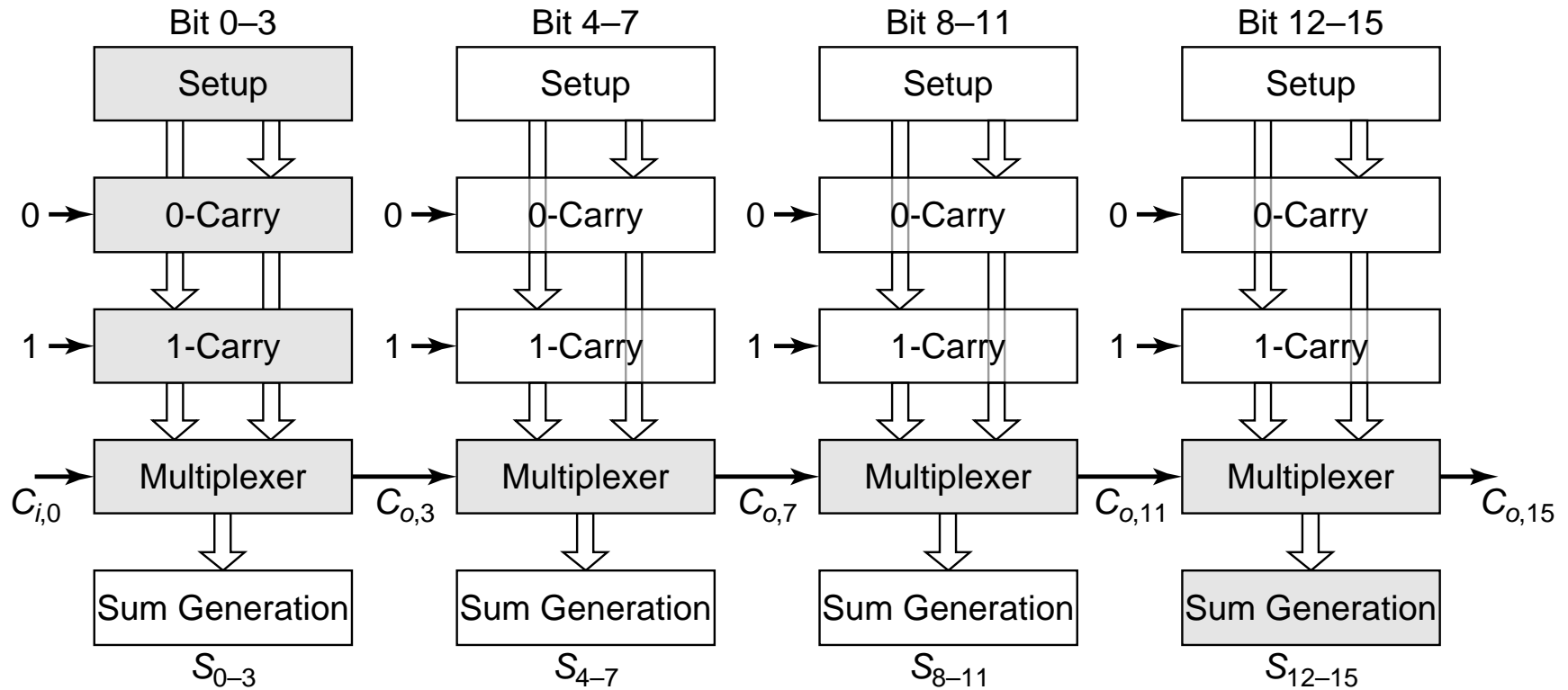

Linear Carry Select

 


Square Root Carry Select

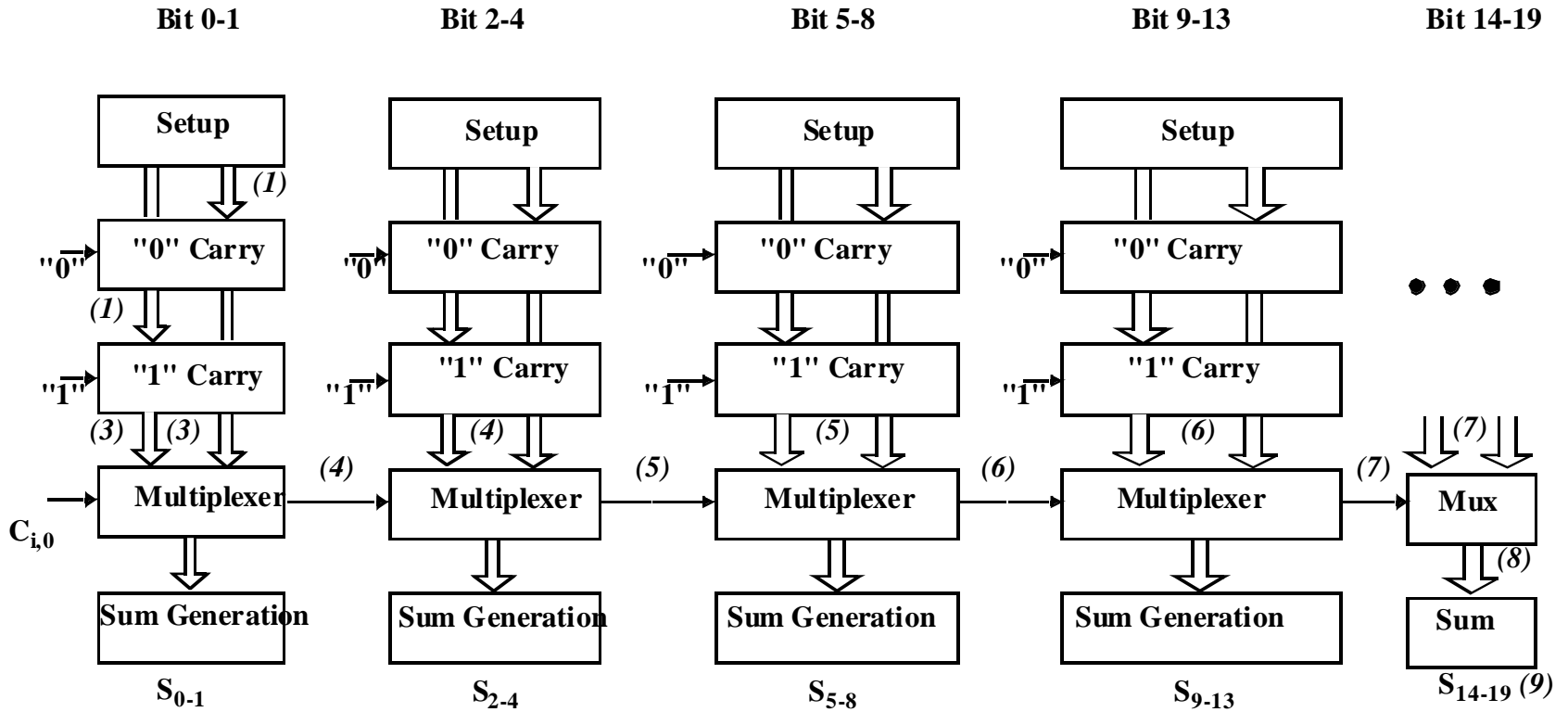


$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$

Adder Delays - Comparison

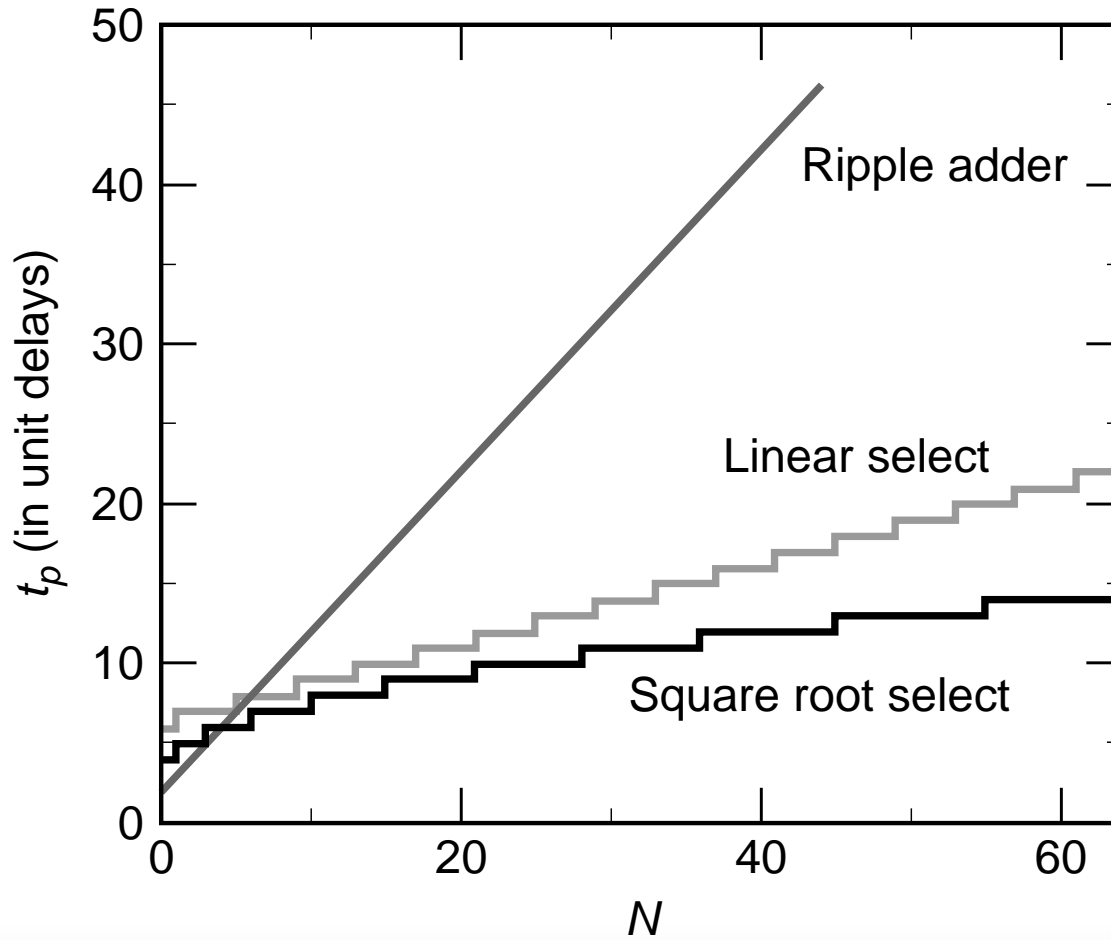

LookAhead - Basic Idea

 

$$C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$$


Look-Ahead: Topology

Expanding Lookahead equations:

$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}C_{o,k-2})$$

All the way:
 
$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}(\dots + P_1(G_0 + P_0C_{i,0})))$$



Look-Ahead: Topology


Expanding Lookahead equations:

$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}C_{o,k-2})$$


All the way:

$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}(\dots + P_1(G_0 + P_0C_{i,0})))$$

Logarithmic Look-Ahead Adder

 

$$t_p \sim N$$

 

$$t_p \sim \log_2(N)$$

Carry Lookahead Trees

$$C_{o,0} = G_0 + P_0 C_{i,0}$$

$$C_{o,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$C_{o,2} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0}$$


$$= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2:1} + P_{2:1} C_{o,0}$$

Can continue building the tree hierarchically.


Carry Lookahead Trees

- The carry-propagation process is decomposed into subgroups of two bits
 - $G_{i:j}$ and $P_{i:j}$ denote the generate and propagate functions, respectively, for a group of bits for positions i to j
 - Block generate and propagate signals.
 - $G_{i:j}$ equals 1 if the group generates a carry, independent of the incoming carry
 - The block propagate $P_{i:j}$ is true if an incoming carry propagates through the complete group.

Example: Domino Adder

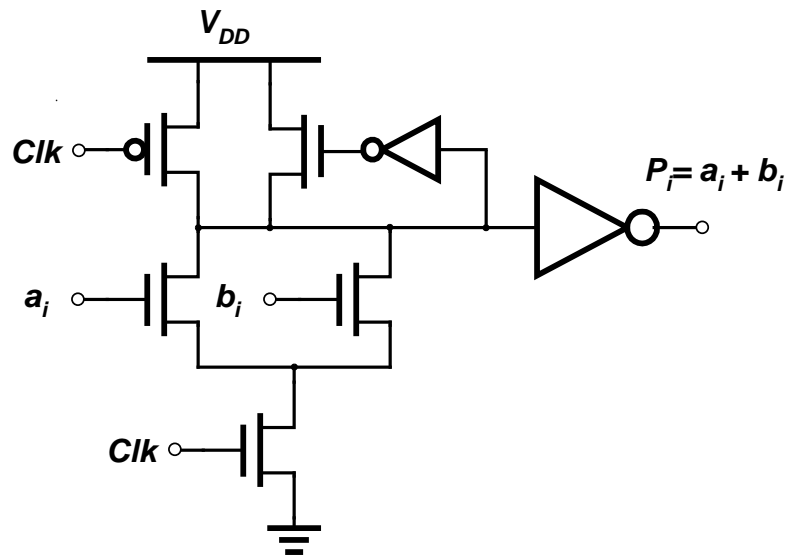


Propagate

 


Generate

Example: Domino Adder

 

Propagate

 

Generate

Example: Domino Sum

