

*EE 466/586*  
*VLSI Design*

**Partha Pande**  
**School of EECS**  
**Washington State University**  
**pande@eecs.wsu.edu**


*Lecture 26*

**Semiconductor  
Memories**


# Semiconductor Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		

# Memory Timing: Definitions

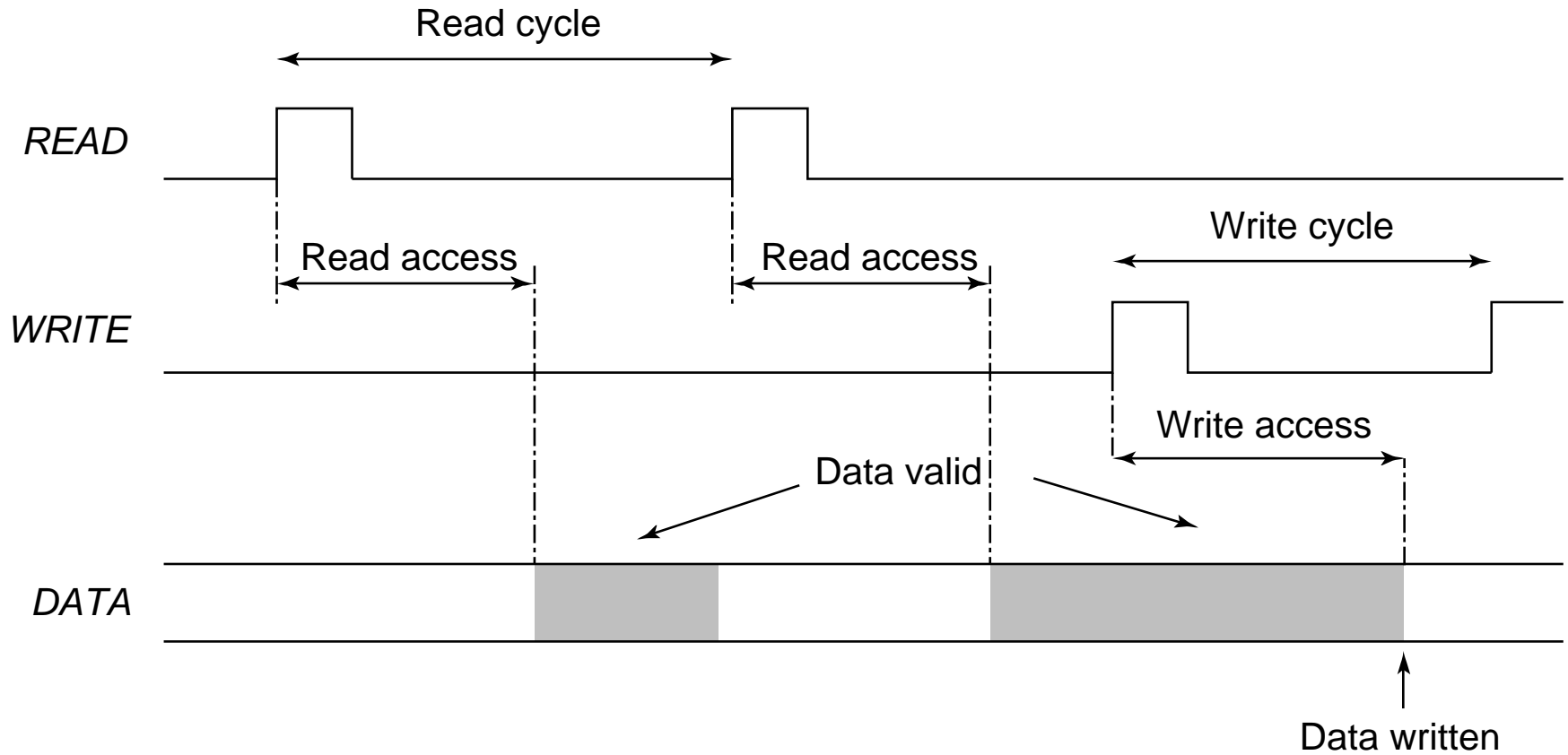

# Memory Architecture: Decoders

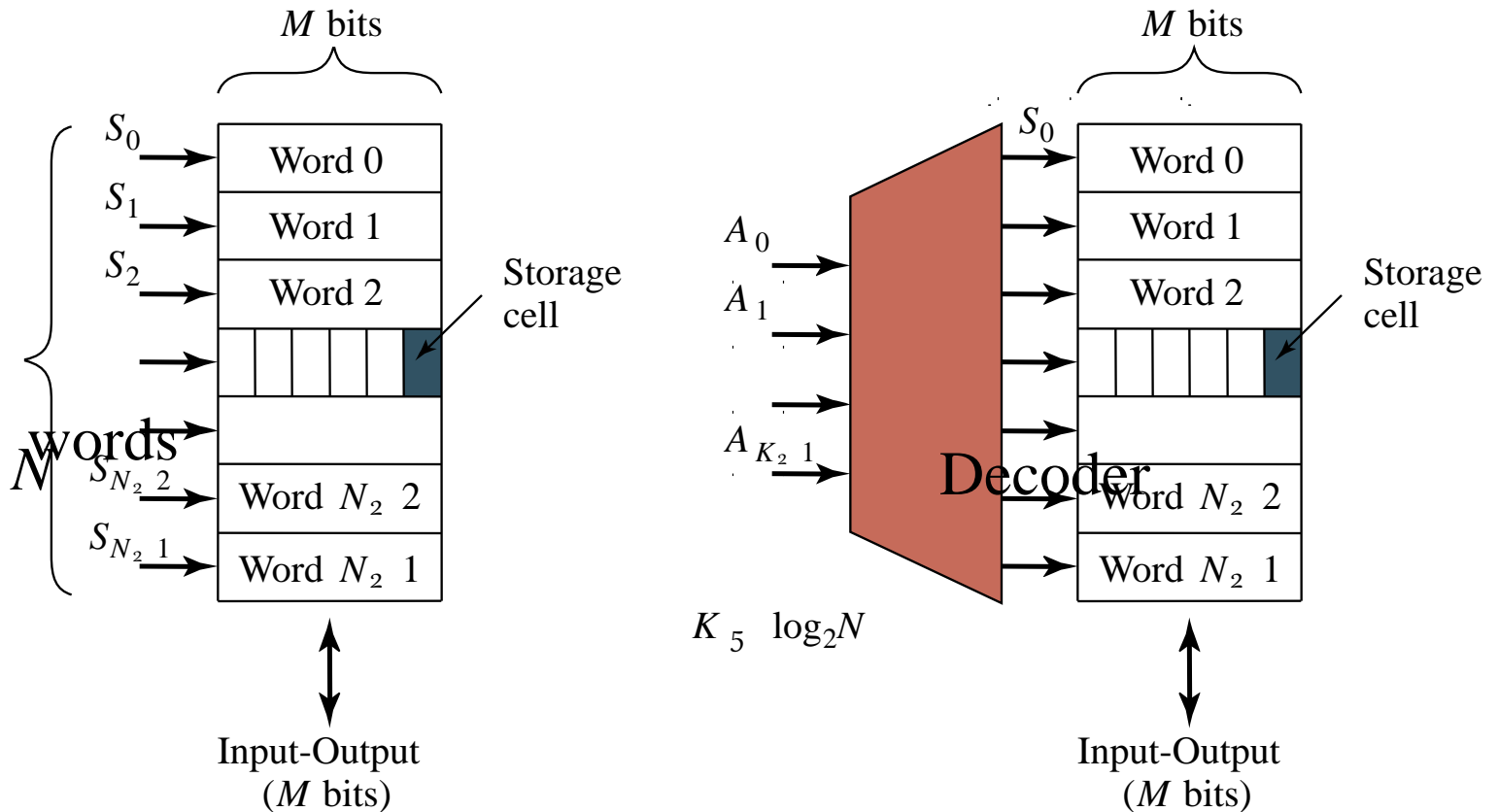


Intuitive architecture for  $N \times M$  memory  
 Too many select signals:  
 $N$  words ==  $N$  select signals


Decoder reduces the number of select signals  
 $K = \log_2 N$

# Array-Structured Memory Architecture

 **Problem: ASPECT RATIO or HEIGHT >> WIDTH**



# Hierarchical Memory Architecture

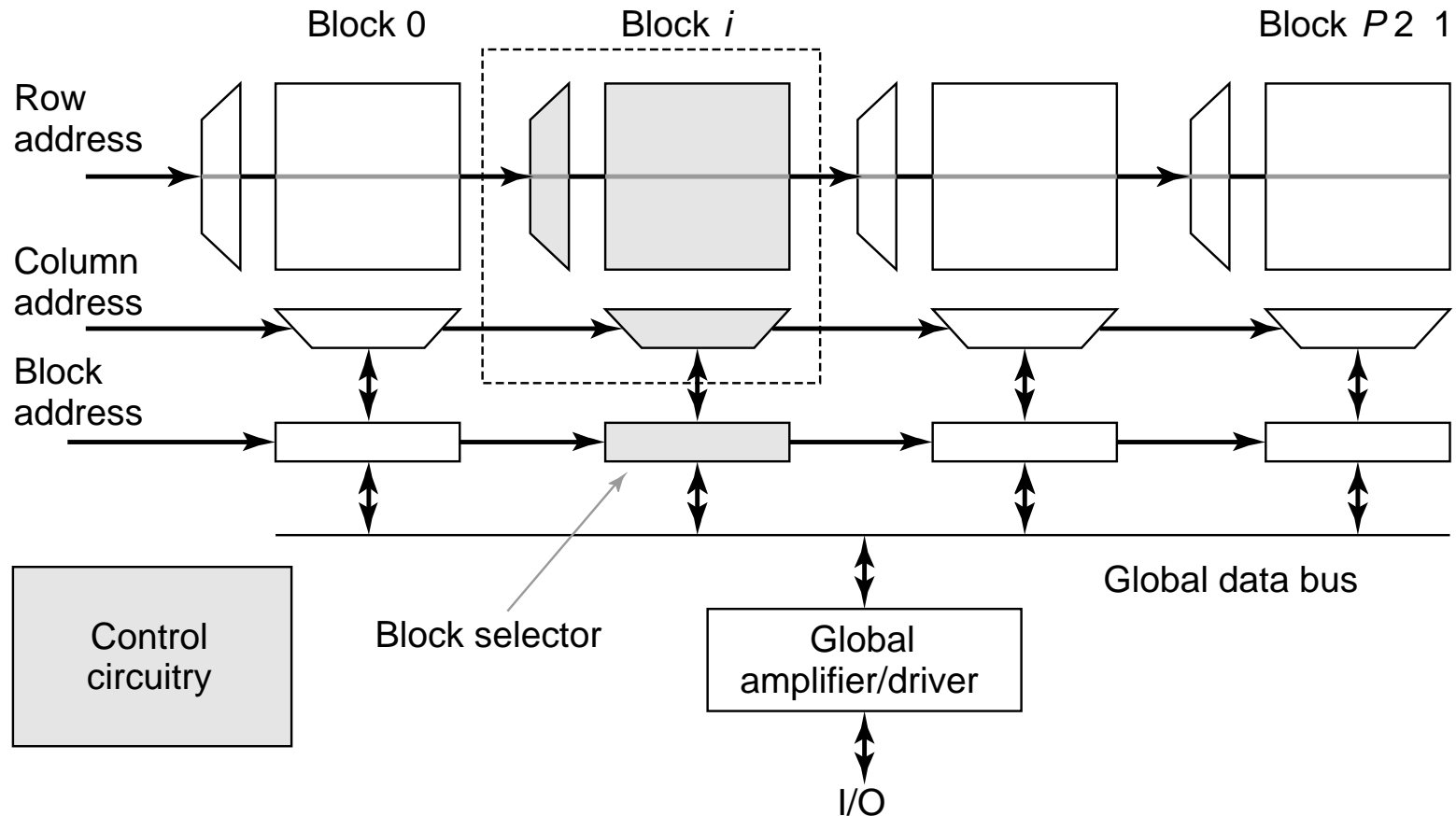

## Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings

# Row Decoders

Collection of  $2^M$  complex logic gates  
Organized in regular and dense fashion

## (N)AND Decoder

$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \bar{A}_4 \bar{A}_5 \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$

## NOR Decoder


$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{\bar{A}_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$


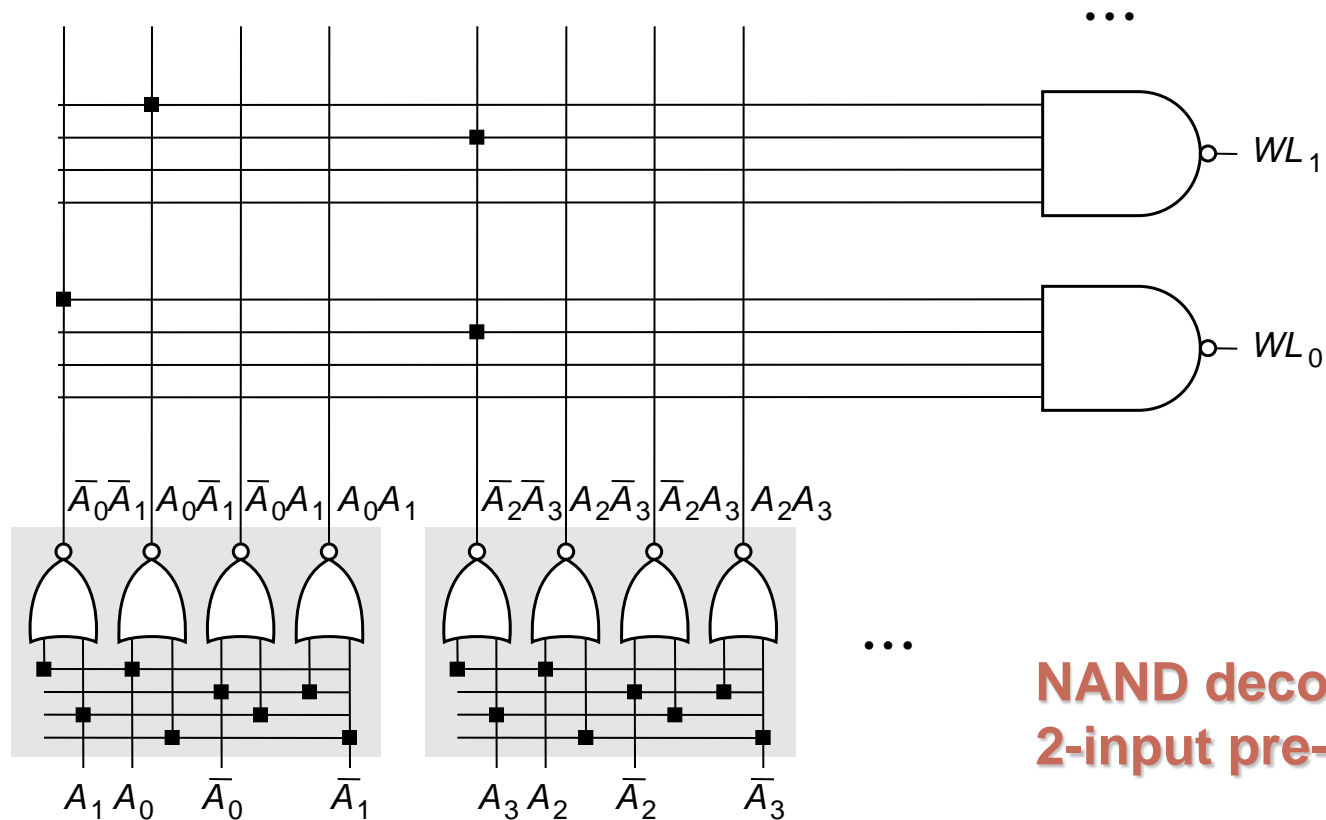
# Hierarchical Decoders

*Multi-stage implementation improves performance*



**NAND decoder using  
2-input pre-decoders**

# *Read-Write Memories (RAM)*

## ❑ STATIC (SRAM)

Data stored as long as supply is applied

Large (6 transistors/cell)

Fast

Differential

## ❑ DYNAMIC (DRAM)


Periodic refresh required

Small (1-3 transistors/cell)

Slower

Single Ended


# 6-transistor CMOS SRAM Cell

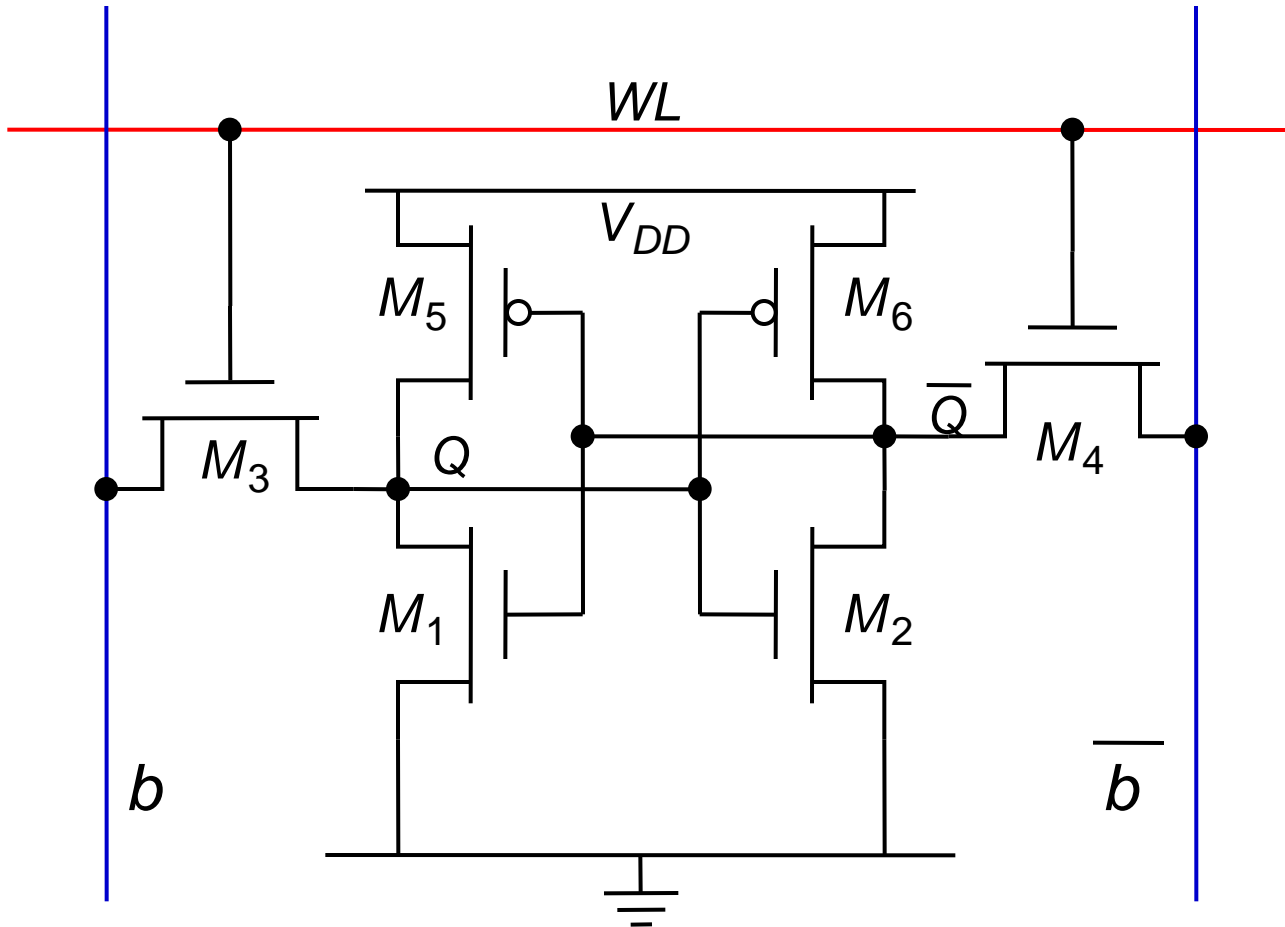

# *Wordline and Bitline*

- Follow board notes

# CMOS SRAM Analysis (Read)

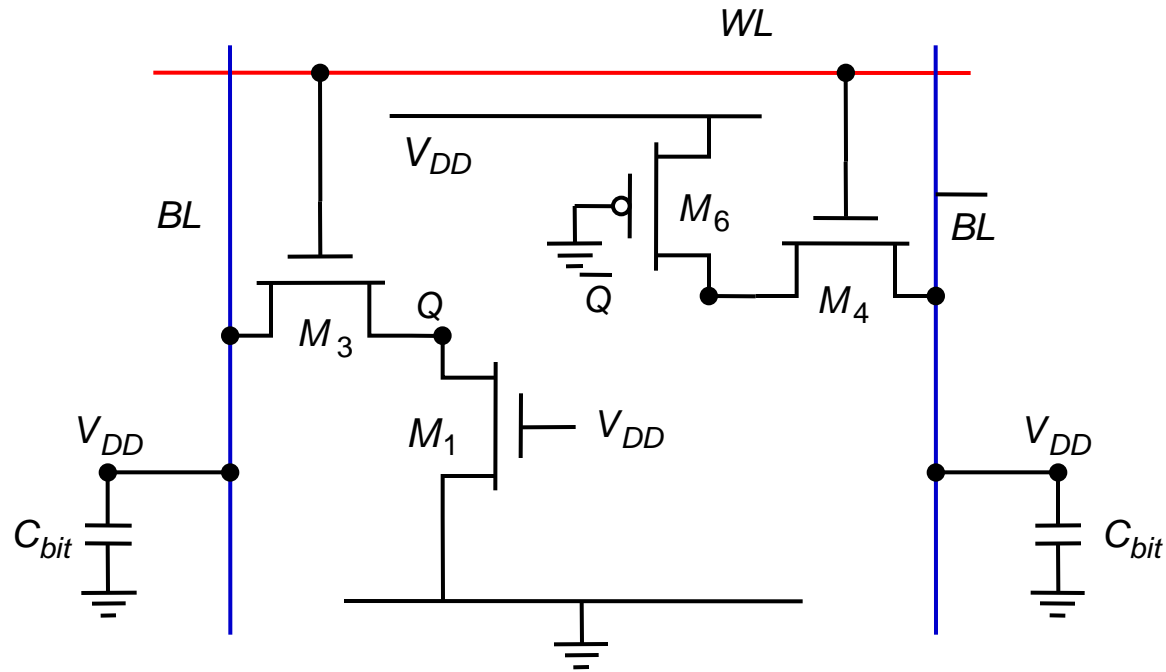


# Read Operation

- ❑ Assume a “0” is stored on the left side of the cell, and a “1” on the right side.
- ❑  $M_1$  is on and  $M_2$  is off.
- ❑ The row selection line is raised to  $V_{dd}$  which turns on the access transistors
- ❑ Current begins to flow through  $M_3$  and  $M_1$  to ground.
- ❑ The resulting cell current slowly discharges the capacitance  $C_{bit}$ .
- ❑ On the other side of the cell, voltage on  $\overline{b}$  remains high since there is no path to ground through  $M_2$ .
- ❑ The difference between  $b$  and  $\overline{b}$  is fed to a sense amplifier

# Read Operation


- Current flowing through  $M_3$  and  $M_1$  raises the output voltage at node  $q$  which could turn on  $M_2$  and bring down the voltage at node  $\bar{q}$ 
  - It should not fall below  $V_S$
  - Size  $M_3$  and  $M_1$  appropriately.
  - Make conductance of  $M_1$  3 to 4 times that of  $M_3$  so that the drain voltage of  $M_1$  does not rise above  $V_{TN}$
- Cell discharge current
  - Follow board notes

# CMOS SRAM Analysis (Read)

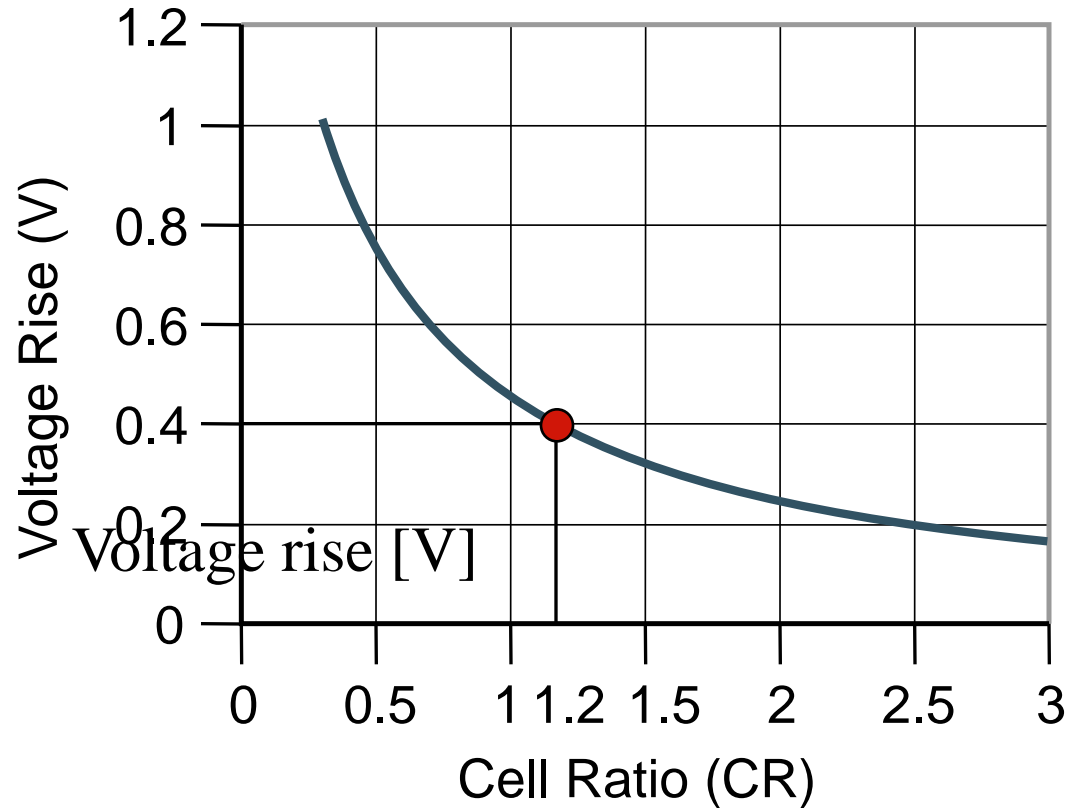



# CMOS SRAM Analysis (Write)

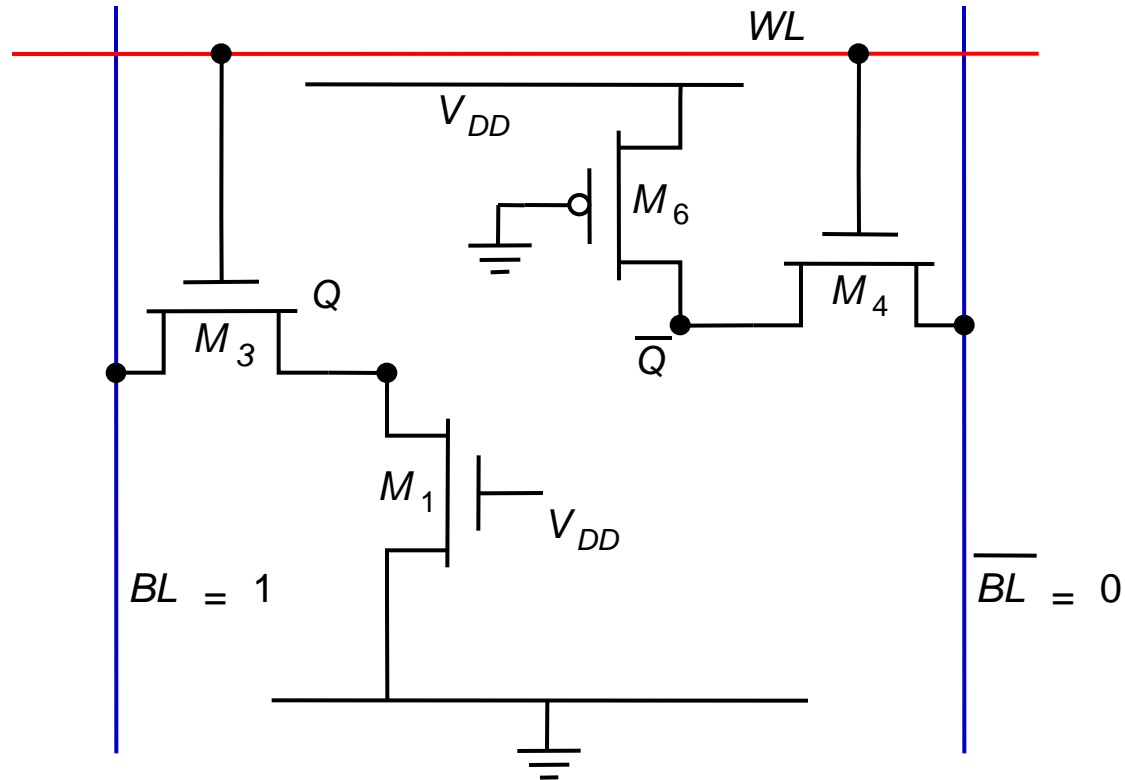

# Write Operation

- ❑ The operation of writing 0 or 1 is accomplished by forcing one bit line low while the other bit line remains at about  $V_{dd}$ .
- ❑ To write 1,  $\overline{b}$  is forced low, and to write 0,  $b$  is forced low
- ❑ Conditions for writing 1
  - Conductance of  $M_4$  is several times larger than  $M_6$  so that the drain of  $M_2$  is pulled below  $V_S$ .
  - $M_1$  turns off and its drain voltage rises to  $V_{DD}$  due to the pull up action of  $M_5$  and  $M_3$ .
  - $M_2$  turns on and assists  $M_4$  in pulling output  $\overline{q}$  to its intended low value.

# *Write Operation*

- Size transistor pair  $M_6$  and  $M_4$
- When the cell is first turned on for the write operation,  $M_6$  and  $M_4$  form a pseudo-NMOS inverter.
- Current flows through the two devices and lowers the voltage at node  $\bar{q}$  from its starting value of  $V_{dd}$
- The design of device sizes is based on pulling the node below  $V_s$

# CMOS SRAM Analysis (Write)

