

EE 466/586
VLSI Design


Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 25
SRAM Design

Column I/O Operation

- *Circuits that perform read and write on the array are column I/O*
 - *Bitline load*
 - *Can be static or precharged to around Vdd*
 - *Proper configuration depends on amplifier design*
 - *For write*
 - *Bit lines must start at around Vdd*
 - *Need to drive one of the bit lines to Gnd*
 - *Mux and write driver design*
 - *For read*
 - *Bit lines must start at around Vdd*
 - *Swings should be small for fast operation*
 - *Involves Mux and sense amplifier design*
 - *Often use different I/O lines for read and write*

Bit Line load options

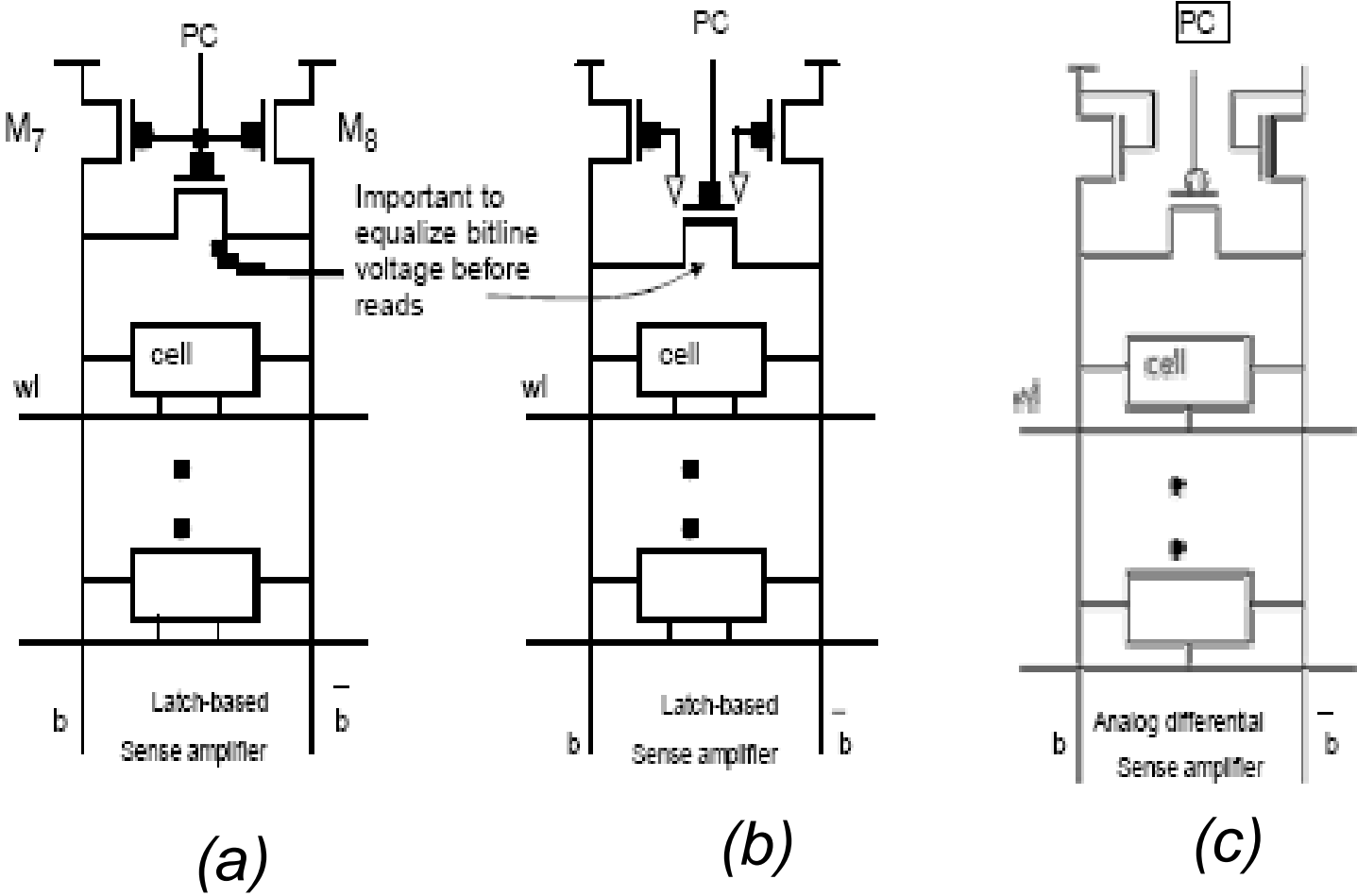

Column Pull-Ups

□ Circuit (a)

- The precharge signal PC, is applied to the two pull-ups and to a third transistor, called the balance transistor, connected between the two bit lines to equalize their voltage levels.
- When the wordline ($w/$) signal goes high, one bit line remains high and the other falls at a linear rate until $w/$ goes low
- The difference between the bit lines is feed into a voltage-sensing latch-based amplifier that is triggered when the differential voltage exceeds a certain threshold

Column Pull-Ups

□ Circuit (b)

- Pseudo-NMOS circuits
- Two static loads and a balance transistor form the precharge circuit
- When PC is applied to the balance transistor, it equalizes the two voltage levels.
- Once the bit lines are precharged, the PC signal is turned off
- At this point the wordline can be activated
- Suitable for current sensing amplifiers since there is continuous current flow


Column Pull-Ups

□ Circuit (c)

- NMOS saturated enhancement load
- Maximum possible voltage on the bit line $V_{DD}-V_T$.
- Suitable for differential voltage sensing amplifiers


Generation of PC signal

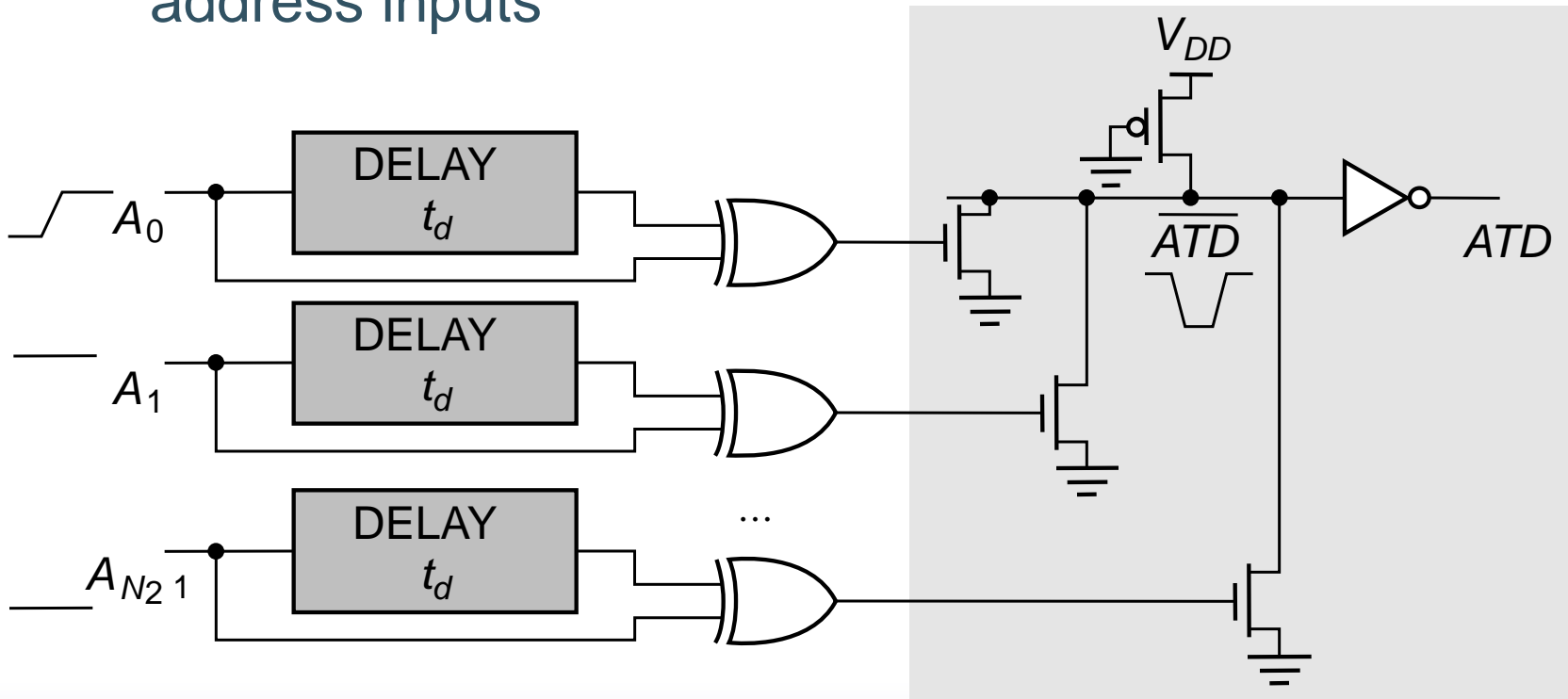- ❑ Address Transition Detection (ATD) circuit.
- ❑ The ATD signal is triggered by any transition on the address inputs




Write Circuitry

 - Precharge bitlines high
- Pull one column line low
- Turn on word line
- Wait until internal values of cell are established
- Turn off word line
- Design precharge transistors to pull bit lines high
- Design write drivers to pull one side going low depends on data value (in this case the left side, b, is pulling low)




Read Circuitry

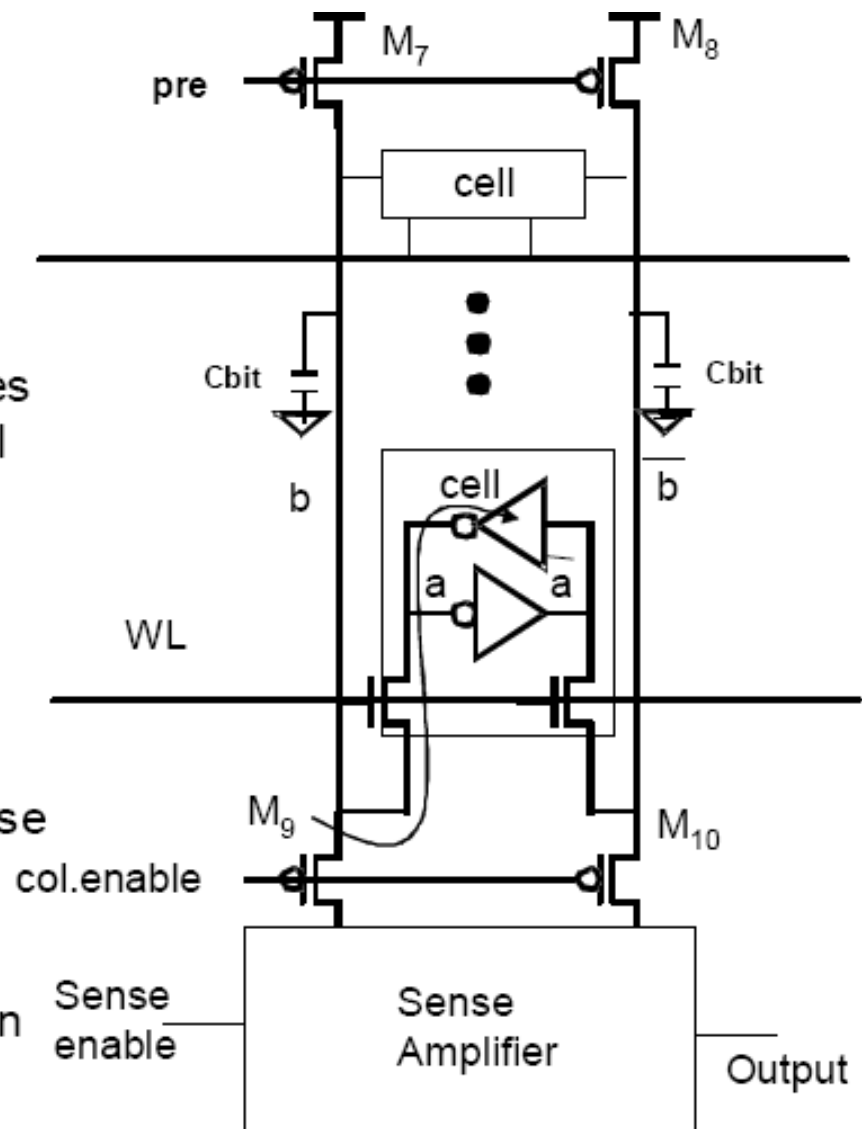- Precharge bitlines high
- Turn on word line
- One line will slowly discharge
- Wait until bit line reaches required low voltage level
- Turn on column select
- Amplify difference with sense amplifier
- Design sense amplifier based on desired response time and power requirements
- Use precharge based on type of sense amp used.




Column Decoder

- Need decoder for column address followed by a mux to select column for input or output operations
- Require two outputs to drive complementary pass gates
- Since the requirements for read and write are different can use separate read and write IO lines
- Have PMOS access for the read IO lines, since the read happens near Vdd
- Have NMOS devices for the write IO lines, since you need to drive bitlines to Gnd (see next slide)

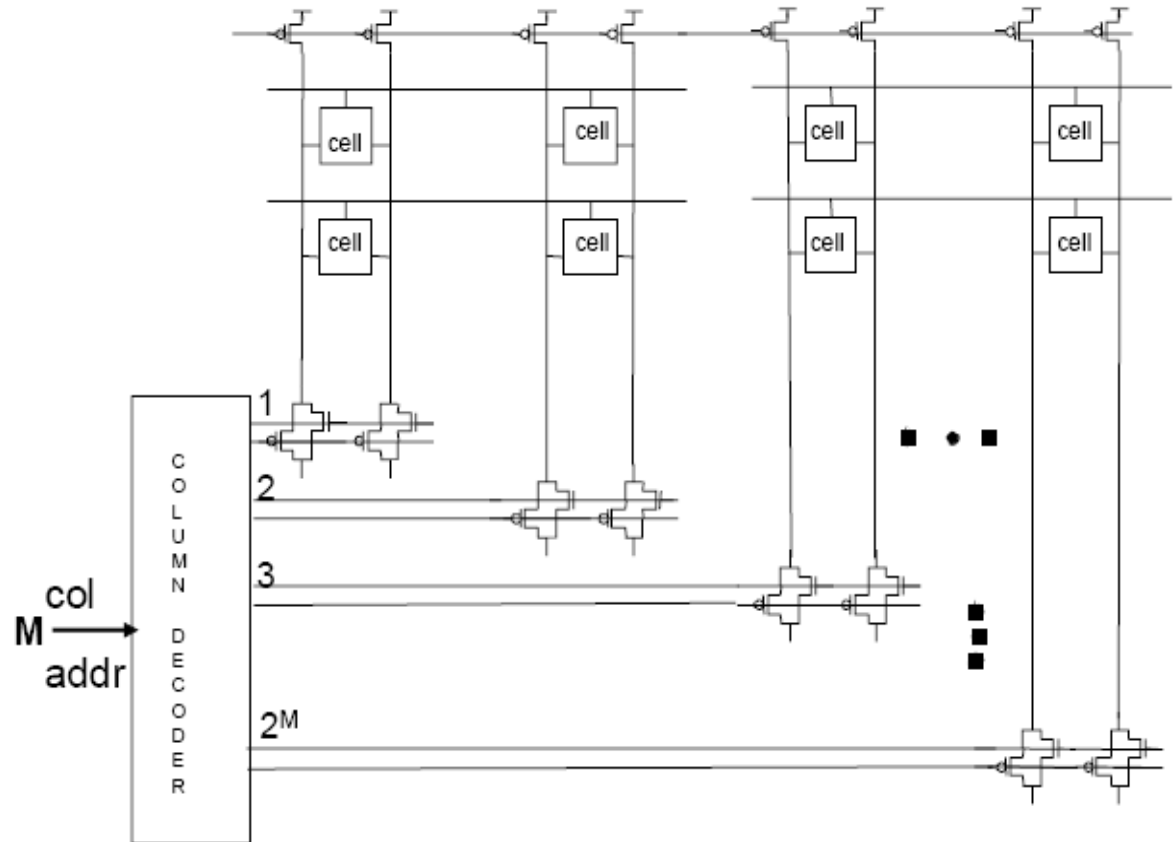


Column Muxing

SINGLE I/O PER BIT

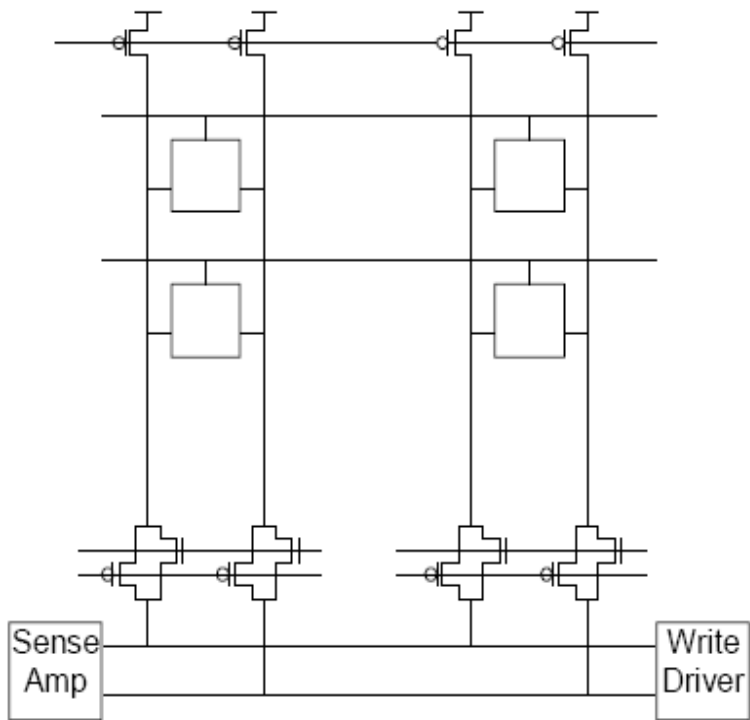

SEPARATE I/O PER BIT

 


Multi-Level Column Decoding


- Alternatives for column selection are tree decoder, regular decoder + pass transistor, or some combination of the two
- Shown on the right is a tree decoder

- switches driven directly by address bits and their complements
- total of 2^{M+1} devices
- large devices to reduce resistance
- long paths -> large C
-> SLOW

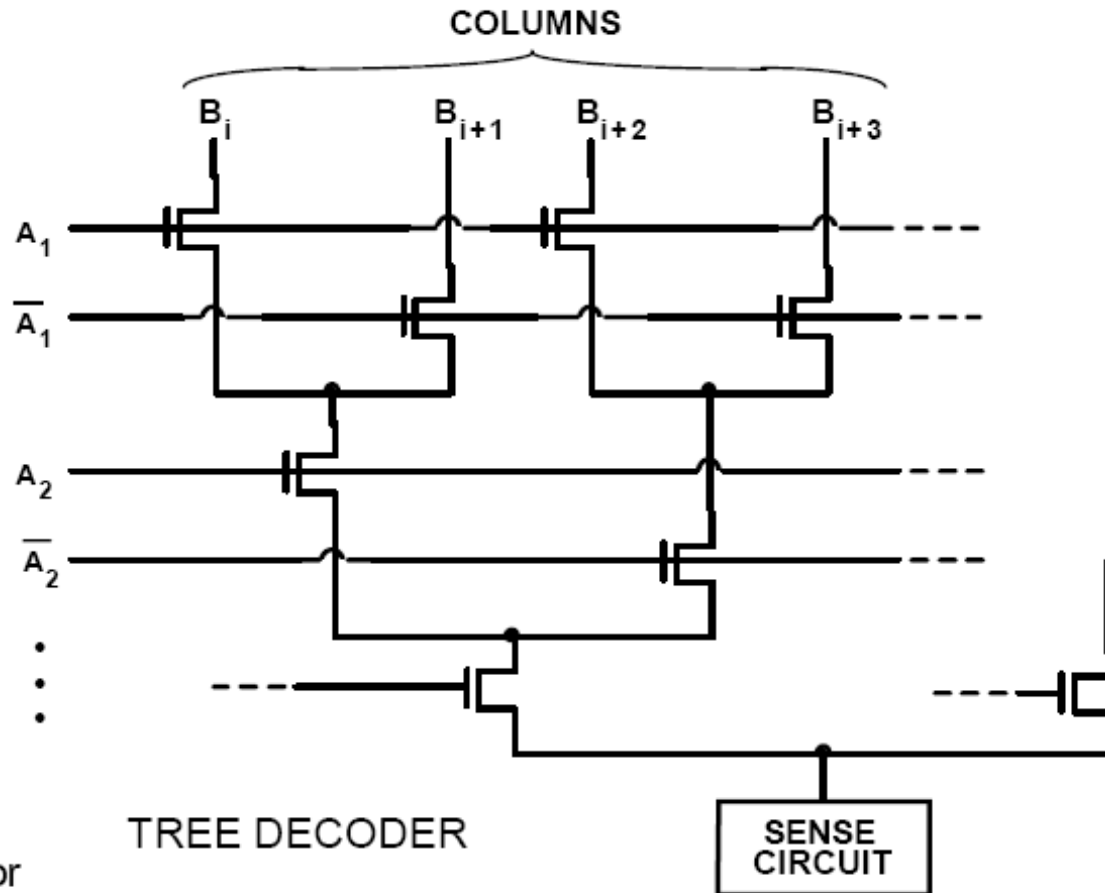- To speed up, add buffers or use adjust sizing of devices



Other Options for Column Decoder

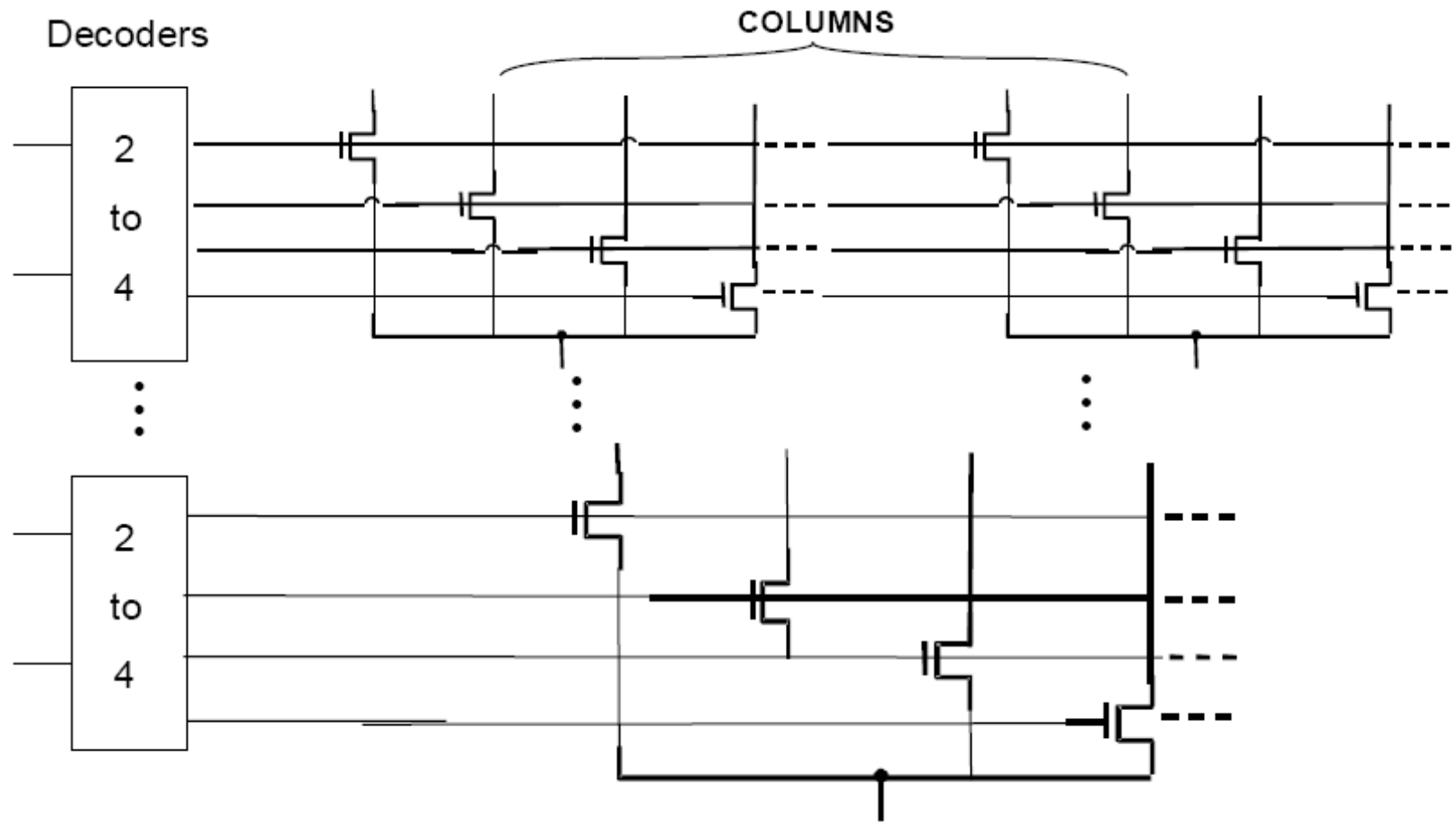


Sense Amplifiers

- ❑ We need a sense amplifier to handle small voltage swings on the bit lines for fast operation
- ❑ Normally you need to choose between
 - Drawing DC power (analog differential sense amplifier)
 - Using a clock edge (latch-based amplifier)
- ❑ For Analog Sense Amplifier
 - All devices in high-gain saturation region – fast switching
- ❑ For Latch-based Amplifier
 - Nothing can happen until an enable transistor turns on
 - And even then you need to wait some more for gate to switch
 - low gain region of transfer curve (slow)
- ❑ We will use latch-based amplifier for lower power


Latch-Based Sense Amplifier

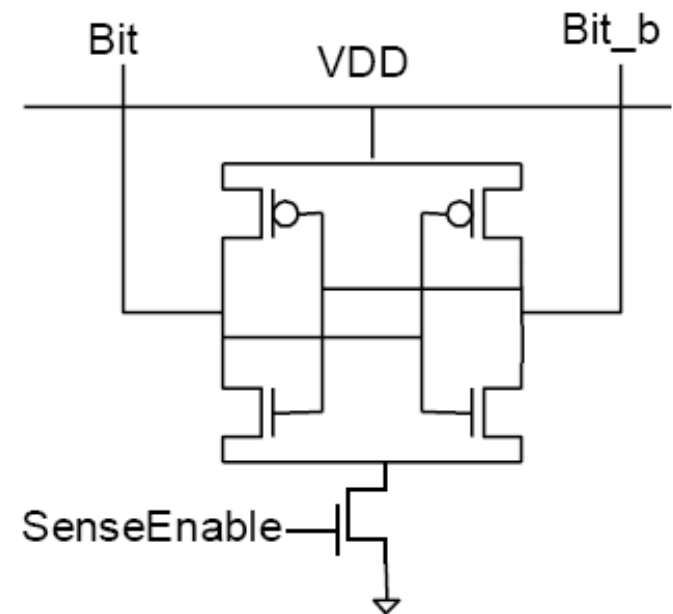- It must sense a very small signal
- It must consume a small area
 - Need one for each bitline
 - Or sets of bitline (4 or 8)
- Simplest design:
 - Two back-to-back inverters
 - Add a clocked pulldown
- Once Bit and Bit_b are established, turn on pulldown device to activate inverters
- Side with lower voltage will drop to 0V while the other side stays high




Latch-Based Sense Amplifier

 - Three stages of operation
 - Precharge
 - Sample
 - Regenerate
- At the end of sample
 - Small bitline voltage on sense and sense_b
- Regenerate
 - M2 and M3 turn on
 - Voltage difference causes current difference
 - Which causes larger voltage difference




Timing Issues

 


Need to guarantee that signal arrives at this point even with process variations.

BUT HOW?

 

Replica Circuit

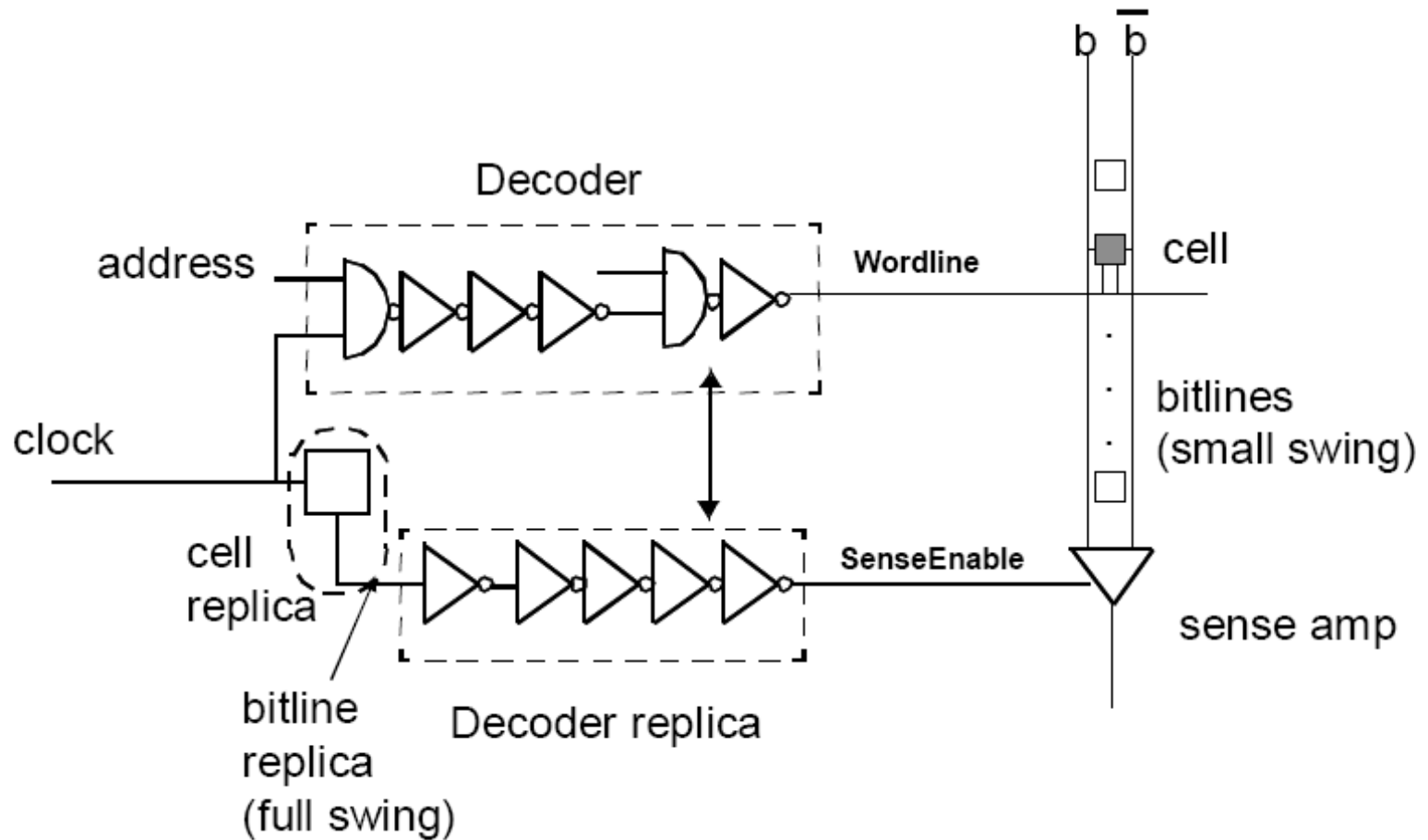

Bit Line Replica

