
EE434

ASIC & Digital Systems

Arithmetic Circuits

Spring 2015
Dae Hyun Kim
daehyun@eecs.wsu.edu


Arithmetic Circuits

- What we will learn
 - Adders
 - Basic
 - High-speed

Adder


- 1-bit adder
 - $Sum = A \oplus B \oplus CI$
 - $CO = A \cdot B + B \cdot CI + A \cdot CI$

A	B	CI		Sum	CO
0	0	0		0	0
0	0	1		1	0
0	1	0		1	0
0	1	1		0	1
1	0	0		1	0
1	0	1		0	1
1	1	0		0	1
1	1	1		1	1

 

Adder


- n-bit Adder

 

Adder


- Two-operand adders
 - Ripple carry adder
 - Carry select adder
 - Conditional sum adder
 - Carry skip adder
 - Prefix adders
 - Carry lookahead adder
 - Ling adder

Ripple Carry Adder

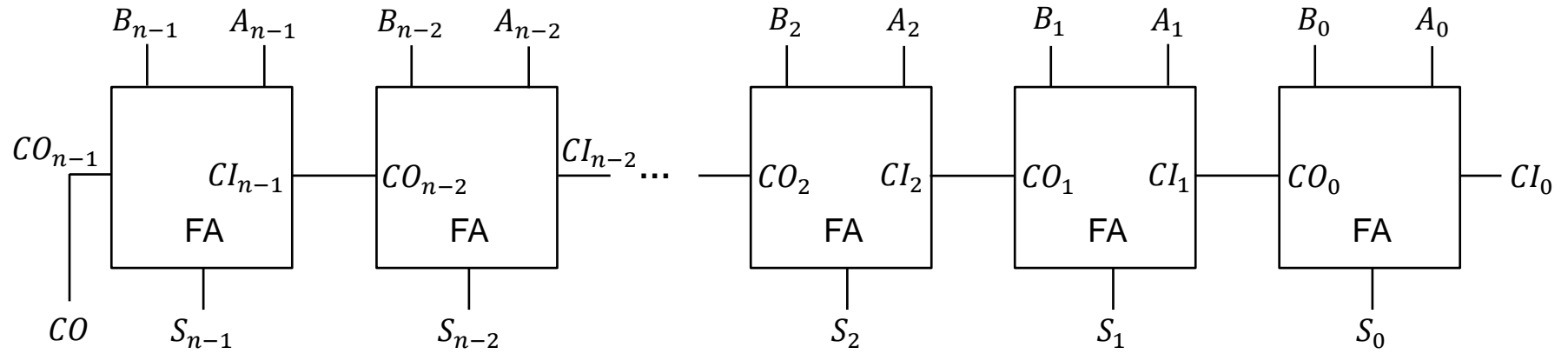

Ripple Carry Adder

 
- Delay computation
 - FA delay: Δ_{FA}
 - n-bit RCA delay: $n \cdot \Delta_{FA}$



Adder

- Bottleneck
 - Carry propagation
- How to improve
 - Parallelization


Carry Select Adder

 

Carry Select Adder

- Example

$i:$	7	6	5	4		3	2	1	0	$CI_0 = 0$
$A_i:$	1	0	1	1		0	1	1	0	
$B_i:$	0	0	1	0		1	1	0	1	

 


Carry Select Adder

- Optimization example
 - 64-bit carry select adder
- Assumptions
 - The k-bit adder is a ripple-carry adder.
 - Delay of a k-bit adder: $k \cdot \Delta_{FA}$
 - Delay of a carry-out logic or a MUX: ε

Carry Select Adder

- Optimization

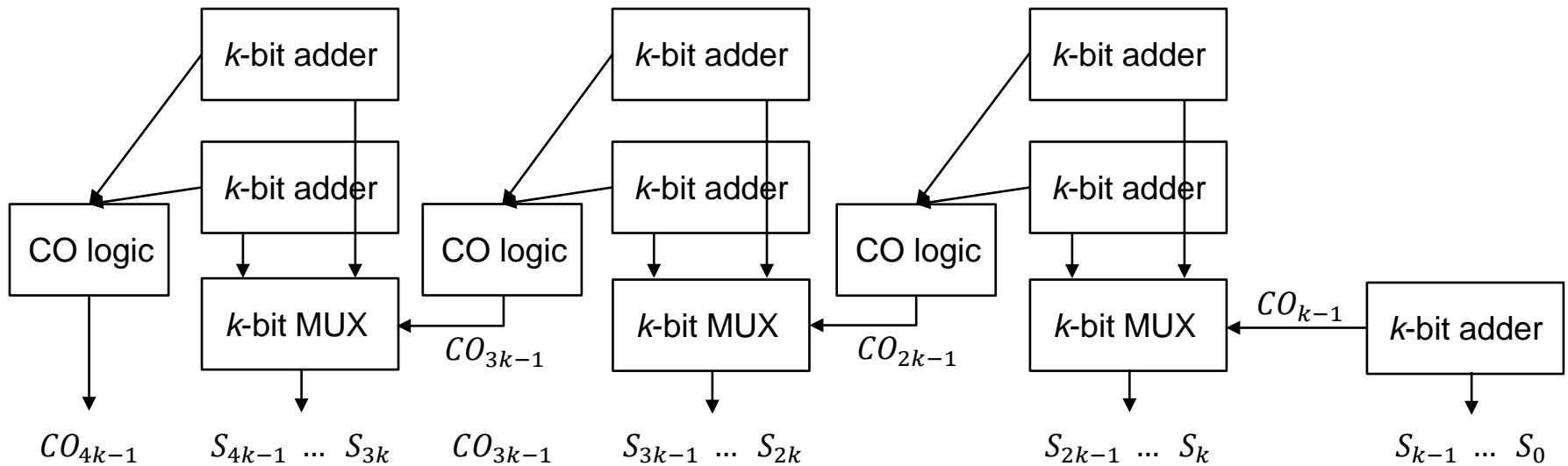

- Delay: $k \cdot \Delta_{FA} + 3 \cdot \varepsilon$

Carry Select Adder

- Optimization (N-bit adder)
 - k -bit adder
 - # groups: N/k
 - # Carry-out logic stages: $N/k - 1$
 - Delay: $\tau = k \cdot \Delta_{FA} + \varepsilon \left(\frac{N}{k} - 1 \right)$

$$\frac{d\tau}{dk} = \Delta_{FA} - \frac{N \cdot \varepsilon}{k^2} = 0$$

$$k = \sqrt{\frac{N \cdot \varepsilon}{\Delta_{FA}}}$$

Carry Select Adder


- Delay: $k = \sqrt{\frac{N \cdot \varepsilon}{\Delta_{FA}}}$
- Example
 - 64-bit adder, $\Delta_{FA} = 200ps$, $\varepsilon = 40ps$
 - $k = \sqrt{\frac{64 \cdot 40}{200}} = 3.57 \rightarrow k = 4.$
 - Delay: $\tau = 4 \cdot 200ps + 40ps \cdot \left(\frac{64}{4} - 1\right) = 1400ps$

Conditional Sum Adder

- Generate two sets of outputs for a given group of operand bits.
 - Set 1: assumes the incoming carry is zero.
 - Set 2: assumes the incoming carry is one.
- Once the incoming carry is known, select the correct set of outputs.

Conditional Sum Adder

 - Generate two sets of outputs for a given group of operand bits.



Assuming incoming carry (CI_i) = 0

$$S_i = S_i^0 = A \oplus B \oplus 0 \rightarrow \text{Delay} = \Delta_{FA}$$

$$CO_i = CO_i^0 = A \cdot B + 0 \cdot (A + B) \rightarrow \text{Delay} = \Delta_{FA}$$

Assuming incoming carry (CI_i) = 1

$$S_i = S_i^1 = A \oplus B \oplus 1 \rightarrow \text{Delay} = \Delta_{FA}$$

$$CO_i = CO_i^1 = A \cdot B + 1 \cdot (A + B) \rightarrow \text{Delay} = \Delta_{FA}$$

Conditional Sum Adder

- Generate two sets of outputs

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	

$$CI_0 = 0$$

Conditional Sum Adder

- Merge two bits

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
Step 1	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 2	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0		1		1		0	
Step 2	$S_i^1:$	1	1	1	0	0	1		
	$CO_i^1:$	0		1		1			

$$CI_0 = 0$$

Conditional Sum Adder

- Merge four bits

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
Step 2	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 3	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0				1			
Step 3	$S_i^1:$	1	1	1	0	0	1		
	$CO_i^1:$	0				1			

$$CI_0 = 0$$

Conditional Sum Adder

- Final

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
Step 2	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 3	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0		1		1		0	
Step 3	$S_i^1:$	1	1	1	0	0	1		
	$CO_i^1:$	0		1		1			
Result		1	1	1	0	0	0	1	1

$$CI_0 = 0$$

Conditional Sum Adder

- Exercise

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$								
	$CO_i^0:$								
Step 2	$S_i^1:$								
	$CO_i^1:$								
Step 3	$S_i^0:$								
	$CO_i^0:$								
Step 3	$S_i^1:$								
	$CO_i^1:$								
Result									

$$CI_0 = 1$$

Conditional Sum Adder

- Analysis

	$i:$	7	6	5	4	3	2	1	0
	$A_i:$	1	0	1	1	0	1	1	0
	$B_i:$	0	0	1	0	1	1	0	1
Step 1	$S_i^0:$	1	0	0	1	1	0	1	1
	$CO_i^0:$	0	0	1	0	0	1	0	0
	$S_i^1:$	0	1	1	0	0	1	0	
	$CO_i^1:$	1	0	1	1	1	1	1	
Step 2	$S_i^0:$	1	0	0	1	0	0	1	1
	$CO_i^0:$	0		1		1			
	$S_i^1:$	1	1	1	0	0	1		
	$CO_i^1:$	0		1		1			
Step 3	$S_i^0:$	1	1	0	1	0	0	1	1
	$CO_i^0:$	0				1			
	$S_i^1:$	1	1	1	0				
	$CO_i^1:$	0							

$$\tau = \Delta_{FA}$$

$$\tau = \Delta_{FA} + \Delta_{MUX}$$


$$\tau = \Delta_{FA} + 2\Delta_{MUX}$$

Conditional Sum Adder

- Analysis
 - N-bit conditional sum adder
 - Delay of a 1-bit adder: Δ_{FA}
 - Delay of a MUX: Δ_{MUX}
 - Delay: $\tau = \Delta_{FA} + (\log_2 N - 1) \cdot \Delta_{MUX}$
 - $\Delta_{FA} = 200ps, N = 64, \Delta_{MUX} = 80ps \rightarrow \tau = 600ps$

Carry Skip Adder


- Split the input into a few groups.

 

- Carry generation ($C_4, C_8, C_{12}, C_{16}, \dots$)
 - Generated internally
- Carry propagation
 - Propagated only when p is 1.
 - $p_i = A_i \oplus B_i$
 - $p_{i+3:i} = p_{i+3} \cdot p_{i+2} \cdot p_{i+1} \cdot p_i$


Carry Skip Adder

 - Split the input into a few groups.
- Propagate carries.



Carry Skip Adder

 - Exercise
 - $A = 1101101101111010$
 - $B = 0101010111010101$
 - $C_{I_0} = 1$



Carry Skip Adder

- Analysis
 - N-bit carry skip adder
- Assumptions
 - The k-bit adder is a ripple-carry adder.
 - Delay of a k-bit adder: $k \cdot \Delta_{FA}$
 - Delay of a MUX: ε
- Delay: $\tau = k \cdot \Delta_{FA} + \frac{N}{k} \cdot \varepsilon$


Prefix Adder

- Carry generate
 - $G_i = A_i \cdot B_i$
 - $G_i = 1$ only when $(A_i, B_i) = (1,1)$
- Carry propagate
 - $P_i = A_i \oplus B_i$ (conceptually $A_i \oplus B_i$, practically $A_i + B_i$)
 - $P_i = 1$ only when $(A_i, B_i) = (1,0)$ or $(0,1)$
- Carry out
 - $C_{i+1} = A_i \cdot B_i + A_i \cdot C_i + B_i \cdot C_i = A_i \cdot B_i + C_i \cdot (A_i + B_i) = A_i \cdot B_i + C_i \cdot (A_i \oplus B_i) = G_i + C_i \cdot P_i$
- Sum
 - $S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$

Prefix Adder


- Two blocks, B_1 and B_2 overlap.
- (generate, propagate) of B_1 : (g_1, p_1)
- (generate, propagate) of B_2 : (g_2, p_2)

 
- Merge B_1 and B_2 into B
 - (generate, propagate) of B : (g, p)
 - $g = g_1 + p_1 \cdot g_2$
 - $p = p_1 \cdot p_2$



Prefix Adder

- Example

 

 P_i and G_i
generation

Prefix Adder

- Basic principle
 - Carry determination

Given

$$(g_0, p_0) \quad (g_1, p_1) \quad \dots \quad (g_{i-2}, p_{i-2}) \quad (g_{i-1}, p_{i-1})$$

Find

$$(g_{[0:0]}, p_{[0:0]}) \quad (g_{[1:0]}, p_{[1:0]}) \quad \dots \quad (g_{[i-2:0]}, p_{[i-2:0]}) \quad (g_{[i-1:0]}, p_{[i-1:0]})$$

- Sum

Given


$$x_0 \quad x_1 \quad \dots \quad x_{i-2} \quad x_{i-1}$$

Find


$$x_0 \quad x_0 + x_1 \quad \dots \quad x_0 + x_1 + \dots + x_{i-2} \quad x_0 + x_1 + \dots + x_{i-1}$$

Prefix Adder

- Basic principle

 

Sum network

 


Carry network

Prefix Adder


- $S_i = A_i \oplus B_i \oplus C_i$
- Propagate carries
 
$$\begin{aligned} G_i &= A_i \cdot B_i \\ P_i &= A_i \oplus B_i \\ S_i &= P_i \oplus C_i \\ C_{i+1} &= G_i + C_i \cdot P_i \end{aligned}$$




Prefix Adder

- Example (ripple carry adder)

 


Prefix Adder

 - Kogge-Stone (min. logic depth, min. fanout, large area, routing)




Prefix Adder

 - Brent-Kung (max. logic depth, min. area)




Prefix Adder

 - Ladner-Fischer (min. logic depth, large fanout)




Prefix Adder

- Han-Carlson (Brent-Kung + Kogge-Stone)

 

Prefix Adder

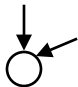- Analysis
 - Generation of P_i and G_i : Δ_c
 - Merging: Δ_m 
 - Sum: Δ_s
 - Delay: $\Delta_c + k \cdot \Delta_m + \Delta_s$
- Example (16-bit adder)
 - Ripple carry: $\Delta_c + 15 \cdot \Delta_m + \Delta_s$
 - Kogge-Stone: $\Delta_c + \log_2 16 \cdot \Delta_m + \Delta_s = \Delta_c + 4 \cdot \Delta_m + \Delta_s$
 - Brent-Kung: $\Delta_c + 6 \cdot \Delta_m + \Delta_s$
 - Ladner-Fischer: $\Delta_c + \log_2 16 \cdot \Delta_m + \Delta_s = \Delta_c + 4 \cdot \Delta_m + \Delta_s$
 - Han-Carlson: $\Delta_c + 5 \cdot \Delta_m + \Delta_s$

Carry Lookahead Adder

- Carry generate
 - $G_i = A_i \cdot B_i$
 - $G_i = 1$ only when $(A_i, B_i) = (1,1)$
- Carry propagate
 - $P_i = A_i \oplus B_i$
 - $P_i = 1$ only when $(A_i, B_i) = (1,0)$ or $(0,1)$
- Sum
 - $S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$
- Carry out
 - $C_{i+1} = A_i \cdot B_i + A_i \cdot C_i + B_i \cdot C_i = A_i \cdot B_i + C_i \cdot (A_i + B_i) = A_i \cdot B_i + C_i \cdot (A_i \oplus B_i) = G_i + C_i \cdot P_i$


Carry Lookahead Adder

- Carry-out logic

- $C_1 = G_0 + P_0 C_0$
- $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
- $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
- $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$

$$\begin{aligned} G_i &= A_i \cdot B_i \\ P_i &= A_i \oplus B_i \\ S_i &= P_i \oplus C_i \\ C_{i+1} &= G_i + C_i \cdot P_i \end{aligned}$$

- Carry lookahead unit

 

Carry Lookahead Adder


- Delay computation

- G_i, P_i : 1 gate delay
- S_0 : 2 gate delays
- $C_1 = G_0 + P_0 C_0$: 3 gate delays
- $C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$: 3 gate delays
- $C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$: 3 gate delays
- $C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$: 3 gate delays
- S_1, S_2, S_3 : 4 gate delays

$$\begin{aligned}G_i &= A_i \cdot B_i \\P_i &= A_i \oplus B_i \\S_i &= P_i \oplus C_i \\C_{i+1} &= G_i + C_i \cdot P_i\end{aligned}$$


Carry Lookahead Adder


- A 4-bit carry lookahead adder

 


Carry Lookahead Adder

- A 16-bit carry lookahead adder


 



 P_i and G_i generation


 4-bit carry lookahead unit

Carry Lookahead Adder

- Multi-level carry lookahead adder

  


 P_i and G_i generation

 4-bit carry lookahead unit with P_i' and G_i' .


 Multi-level carry lookahead unit


Carry Lookahead Adder

- Multi-level carry lookahead adder

 

- $G_{[i+3,i]}$: Block generate
- $P_{[i+3,i]}$: Block propagate

 P_i and G_i generation

 4-bit carry lookahead unit with P_i' and G_i' .

 Multi-level carry lookahead unit

Carry Lookahead Adder

- Carry recurrence formula

- $C_{i+1} = G_i + P_i \cdot C_i$

- $C_{i+4} = G_{i+3} + P_{i+3} \cdot C_{i+3}$

- $= G_{i+3} + P_{i+3} \cdot (G_{i+2} + P_{i+2} \cdot C_{i+2}) = G_{i+3} + P_{i+3} \cdot G_{i+2} + P_{i+3} \cdot P_{i+2} \cdot C_{i+2}$

- $= \dots$

- $= G_{i+3} + P_{i+3} \cdot G_{i+2} + P_{i+3} \cdot P_{i+2} \cdot G_{i+1} +$

- $P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot G_i + P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot P_i \cdot C_i$

- Block generate

- $G_{[i+3,i]} = G_{i+3} + P_{i+3} \cdot G_{i+2} + P_{i+3} \cdot P_{i+2} \cdot G_{i+1} + P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot G_i$

- Block propagate

- $P_{[i+3,i]} = P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot P_i$


- Carry out

- $C_{i+4} = G_{[i+3,i]} + C_i \cdot P_{[i+3,i]}$

Carry Lookahead Adder

- Delay computation
 - G_i, P_i : 1 gate delay
 - Block propagate
 - $P_{[i+3,i]} = P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot P_i$: 2 gate delays
 - Block generate
 - $G_{[i+3,i]} = G_{i+3} + P_{i+3} \cdot G_{i+2} + P_{i+3} \cdot P_{i+2} \cdot G_{i+1} + P_{i+3} \cdot P_{i+2} \cdot P_{i+1} \cdot G_i$: 3 gate delays
 - Carry out
 - $C_4 = G_{[3,0]} + C_0 \cdot P_{[3,0]}$: 4 gate delays
 - $C_8 = G_{[7,4]} + C_4 \cdot P_{[7,4]} = G_{[7,4]} + P_{[7,4]} \cdot G_{[3,0]} + P_{[7,4]} \cdot P_{[3,0]} \cdot C_0$: 5 gate delays
 - C_{12} : 5 gate delays
 - C_{16} : 5 gate delays
 - Sum
 - $S_{[7,4]}$: 7 gate delays
 - $S_{[11,8]}$: 8 gate delays
 - $S_{[15,12]}$: 8 gate delays

Carry Lookahead Adder

 

Ling Adder

- A type of carry lookahead adder
- Achieves significant hardware savings.
- Modifications

$$- P_i = A_i \oplus B_i \rightarrow t_i = A_i + B_i$$

$$- h_i = C_i + C_{i-1}$$

$$- C_i = G_{i-1} + C_{i-1} \cdot P_{i-1}$$

$$\begin{aligned} - C_{i-1} \cdot P_{i-1} &= C_{i-1} \cdot P_{i-1} + \overset{=0}{G_{i-1} \cdot P_{i-1}} + \overset{\text{repeated}}{P_{i-1} \cdot C_{i-1} \cdot P_{i-1}} \\ &= C_{i-1} \cdot P_{i-1} + (G_{i-1} + P_{i-1} \cdot C_{i-1}) \cdot P_{i-1} \\ &= (C_{i-1} + C_i) \cdot P_{i-1} \quad = C_i \\ &= h_i \cdot P_{i-1} \end{aligned}$$

Ling Adder

- Modifications

- $t_i = A_i + B_i$

- $h_i = C_i + C_{i-1}$

- $G_{i-1} \Rightarrow h_i \cdot G_{i-1}$

- $C_i = G_{i-1} + C_{i-1} \cdot P_{i-1} = G_{i-1} + h_i \cdot P_{i-1} = h_i \cdot G_{i-1} + h_i \cdot P_{i-1}$
 $= h_i \cdot (G_{i-1} + P_{i-1}) = h_i \cdot t_{i-1}$

- $h_i = C_i + C_{i-1} = (G_{i-1} + C_{i-1} \cdot P_{i-1}) + C_{i-1} = G_{i-1} + C_{i-1}$
 $= G_{i-1} + h_{i-1} \cdot t_{i-2}$

- $h_i = G_{i-1} + h_{i-1} \cdot t_{i-2}$
 $= G_{i-1} + t_{i-2} \cdot (G_{i-2} + h_{i-2} \cdot t_{i-3})$

- $= G_{i-1} + G_{i-2} + h_{i-2} \cdot t_{i-2} \cdot t_{i-3} \quad \longleftarrow \boxed{t_{i-2} \cdot G_{i-2} = G_{i-2}}$

- $= G_{i-1} + G_{i-2} + G_{i-3} \cdot t_{i-2} + G_{i-4} \cdot t_{i-2} \cdot t_{i-3} + h_{i-4} \cdot t_{i-2} \cdot t_{i-3} \cdot t_{i-4}$

Ling Adder

- Modifications

- $C_{i+4} = G_{i+3} + G_{i+2} \cdot t_{i+3} + G_{i+1} \cdot t_{i+3} \cdot t_{i+2} + G_i \cdot t_{i+3} \cdot t_{i+2} \cdot t_{i+1} + C_i \cdot t_{i+3} \cdot t_{i+2} \cdot t_{i+1} \cdot t_i$
- $S_i = t_i \oplus h_{i+1} + G_i \cdot t_{i-1} \cdot h_i$

- Advantages

- Lower fan-in
- Suitable for some specific technologies.