 


EE586
VLSI Design



Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 4
MOS Inverter Circuits

The CMOS Inverter: A First Glance



 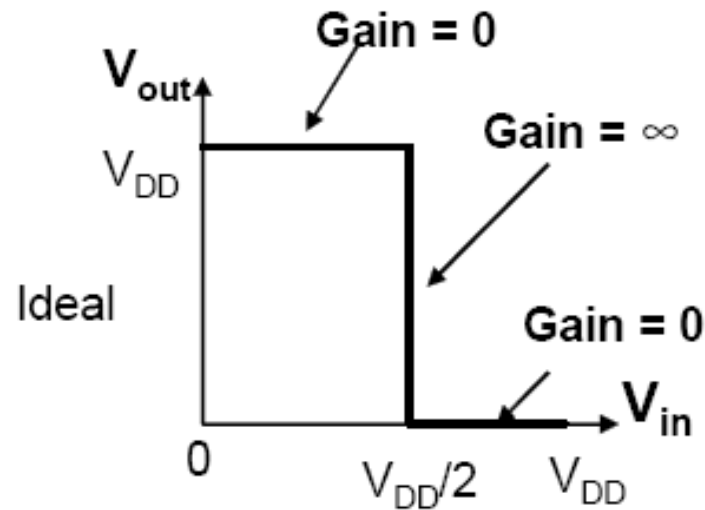
Ideal Voltage Transfer Characteristics (VTC)



Characteristics of Ideal VTC


- ❑ **Switching point occurs at $V_{DD}/2$.**
- ❑ **Three gain regions in the ideal inverter VTC**
 - **Two zero gain regions and one infinite gain region**
- ❑ **The high gain region, separating the high output from the low output, is a feature required by all useful logic gates to reject noise in the system.**
- ❑ **The input range is very large while the output range is small for the ideal inverter.**
 - **The range refers to the voltage interval over which a signal is considered to be a logic 0 or logic 1**
- ❑ **Having a large input range and small output range is a desirable characteristic of a logic gate for noise immunity.**
 - **It implies that the input can vary significantly with little or no effect on the output.**

Realistic VTC

 


- ❖ In practical inverters, the low output voltage, V_{OL} , may not reach Gnd, and the high output voltage V_{OH} , may not reach V_{DD} .
- ❖ The output does not abruptly switch from V_{DD} to Gnd at $V_{DD}/2$.
- ❖ Switching point, V_S , is defined as the point where $V_{OUT}=V_{IN}$

Realistic VTC

 


- ❖ **The input range for logic 0 is from $0V$ to a point called V_{IL} where the input is still considered to be low.**
- ❖ **The input range for logic 1 is the interval from V_{OH} to V_{IH} , where the input is still considered to be high.**
- ❖ **The output ranges are from V_{OL} to V_{OUL} for logic 0 and V_{OH} to V_{OUH} for logic 1**

Effects of Noise

 


- ❖ *Input variation remains within the valid logic 0 range.*
- ❖ *The output varies by a smaller amount but remains in the range considered to be a valid logic 1*
- ❖ *Input is varying in the range where the logic gate acts as a low-gain amplifier, from V_{OL} to V_{IL} .*
- ❖ *This attenuates the noise since the gain is less than one in this range.*
- ❖ *the output remains in the range V_{OUH} to V_{OH}*
- ❖ *The next few inverters in the chain will attenuate the noise even further and eventually the noise is damped out of the system.*

Noise Margin

 



(a) Noiseless System

 


(b) System with Single Stage Noise of Magnitude v_n

Noise Margin (Cont'd)

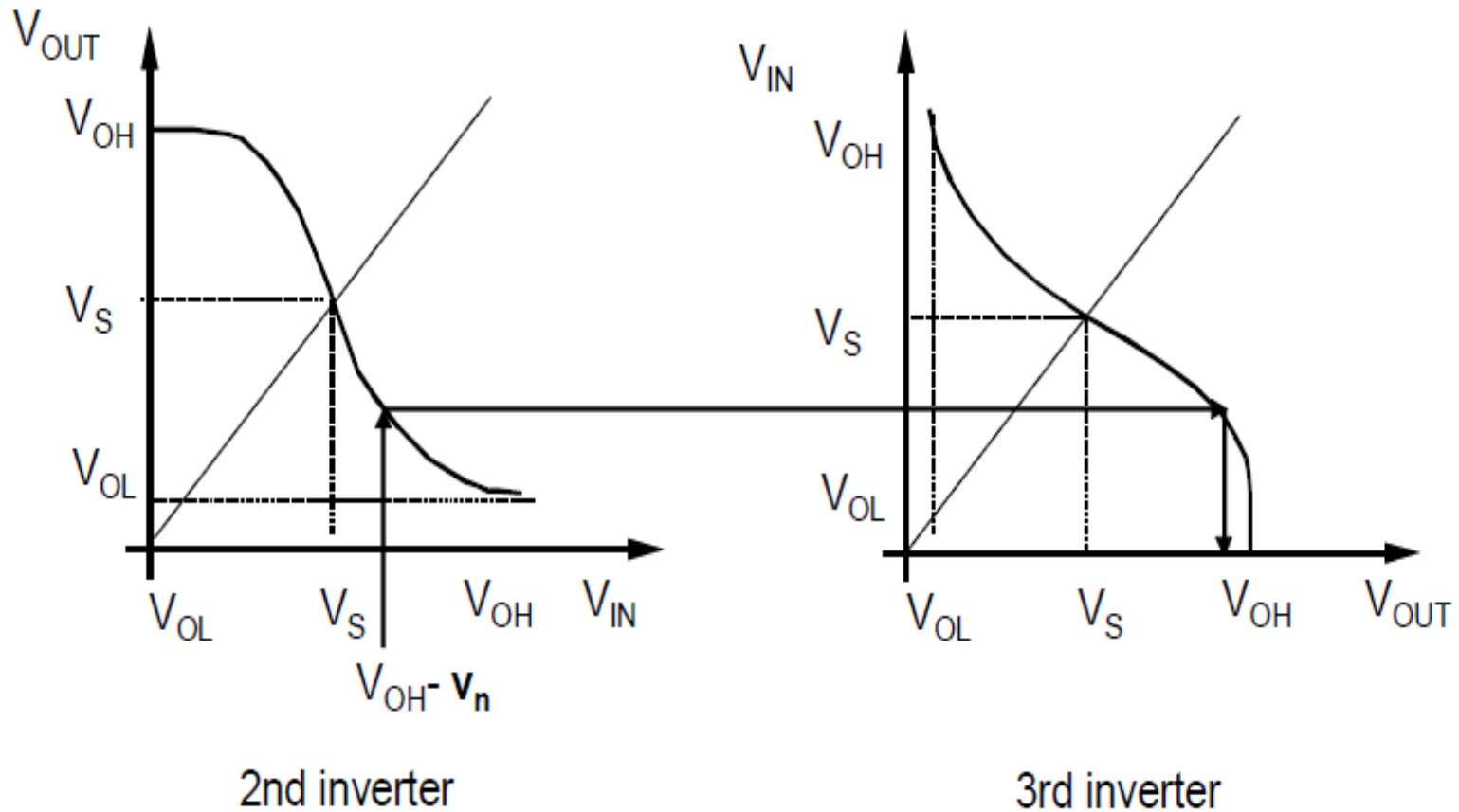

 


Multiple-Source Noise Margin (MSNM)

 

❖ *Follow board notes*


Multiple-Source Noise Margin (MSNM)

 


$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

RESISTIVE-LOAD INVERTER DESIGN

 

(a) Inverter

 

(b) Drain characteristics and load line

VTC

- ❑ The value of V_{OH} can be obtained by setting the input voltage below the transistor threshold voltage V_T .
- ❑ No current flows and inverter output voltage V_{out} remains at V_{DD} . The nominal voltage representing a logic high level is $V_{OH} = V_{DD}$
- ❑ When a logic value of 1, represented by V_{OH} , applied at the input of this inverter, the transistor is driven into the linear region of operation
- ❑ Follow board notes

VTC (Cont'd)

- At $V_{in} = V_{IL}$, the output voltage is near V_{DD} and the transistor is operating in the saturation region.
- Follow board notes

VTC (Cont'd)

- At the other unity gain point, where $V_{in} = V_{IH}$, the output voltage is near 0 V and the transistor is operating in the linear region.
- Follow board notes

VTC (Cont'd)

- Switching threshold
- NMOS transistor is in saturation

$$\frac{WV_{sat}C_{ox}(V_S - V_T)^2}{(V_S - V_T) + E_C L} = \frac{V_{DD} - V_S}{R_L}$$