



*EE 466/586*  
*VLSI Design*

**Partha Pande**  
**School of EECS**  
**Washington State University**  
**pande@eecs.wsu.edu**

***Lecture 5***  
***MOS Inverter Circuits***
  
# Saturated Enhancement Load

- A single NMOS transistor with the gate connected to the drain can be used as a load device.



# *Saturated Enhancement Load (Cont'd)*

- The load transistor can operate only in saturation or cutoff ( $V_{GS} = V_{DS}$ )
- The other NMOS device pulls down the output node
- The relative sizes of the two transistors determine the output voltage

# *Saturated Enhancement Load (cont'd)*



- The output high level  $V_{OH}$  is not equal to  $V_{DD}$
- The pull-up transistor ceases to conduct after its gate-source voltage decreases to the threshold voltage.
  - The output node never rises above  $V_{DD}-V_{TL}$
  - $V_{TL}$  is no longer  $V_{T0}$
  - Output voltage appears as a body bias
  - Follow board notes

## *Saturated Enhancement Load (Cont'd)*

- How to find  $V_{OL}$ ?
- For the inverting transistor, with  $V_{GS}=V_{OH}$  the output voltage should be lower than  $V_{T0}$
- Pull down transistor is in the linear region  
 $V_{DS} < V_{GS} - V_{TI}$
- $I_{DI}(\text{lin}) = I_{DL}(\text{Sat})$
- Follow board notes
  
# Linear Enhancement load

- The output high level of the saturated enhancement load configuration is not sufficient



## *Linear Enhancement Load (Cont'd)*

- The load device can pull the output all the way to  $V_{DD}$
- For the pull up device  $V_{DS} < V_{GS} - V_{TL}$
- The pull-up device, operates in the linear region