

*EE 466/586*  
*VLSI Design*

**Partha Pande**  
**School of EECS**  
**Washington State University**  
**pande@eecs.wsu.edu**


# ***Lecture 9***

## ***Propagation delay***


# *Power and delay Tradeoffs*

- Follow board notes


# Propagation Delay

 


(a)

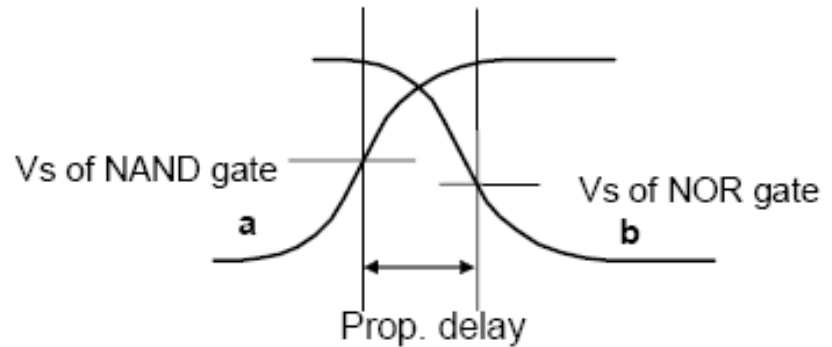

(b)

 


(c)

 


(d)


# Switching Time

 

(a)

 




(b)

 

(c)

❖ *Follow board notes*

# Gate sizing-Velocity Saturation

   


❖ Size of the stacked devices will be smaller

# Gate sizing-Velocity Saturation

- ❑ A single device of size  $W$  takes longer to discharge the load capacitance than two series stacked  $2W$  devices
- ❑ The single  $W$  device is in saturation for the entire transition of the output from  $V_{DD}$  to  $V_{DD}/2$
- ❑ The two series devices operate in the different regions
- ❑ Transistor lower in the stack will be in linear, with  $V_{GS1}=V_{DD}$
- ❑ Upper transistor operates in saturation,  $V_{GS2}=V_{DD}-V_{DS1}$


# Load Capacitance

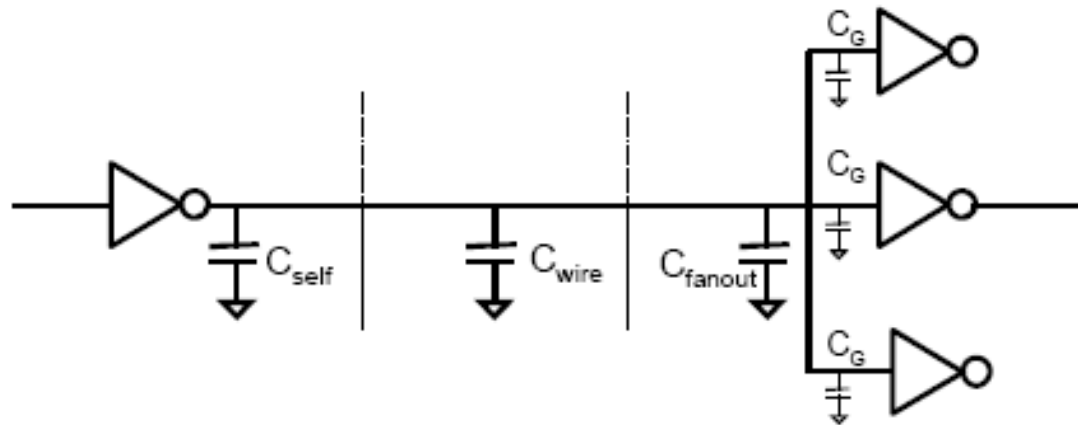

$$C_{load} = C_{self} + C_{wire} + C_{fanout}$$




# Fanout Gate Capacitance

 

$$C_{fanout} = \sum C_G$$

$$\begin{aligned} C_G &= C_{Gn} + 2C_{OL} + C_{Gp} + 2C_{OL} \\ &= C_{ox}LW_n + 2C_{ol}W_n + C_{ox}LW_p + 2C_{ol}W_p \\ &= (C_{ox}L + 2C_{ol})(W_n + W_p) \end{aligned}$$


# Self-Capacitance

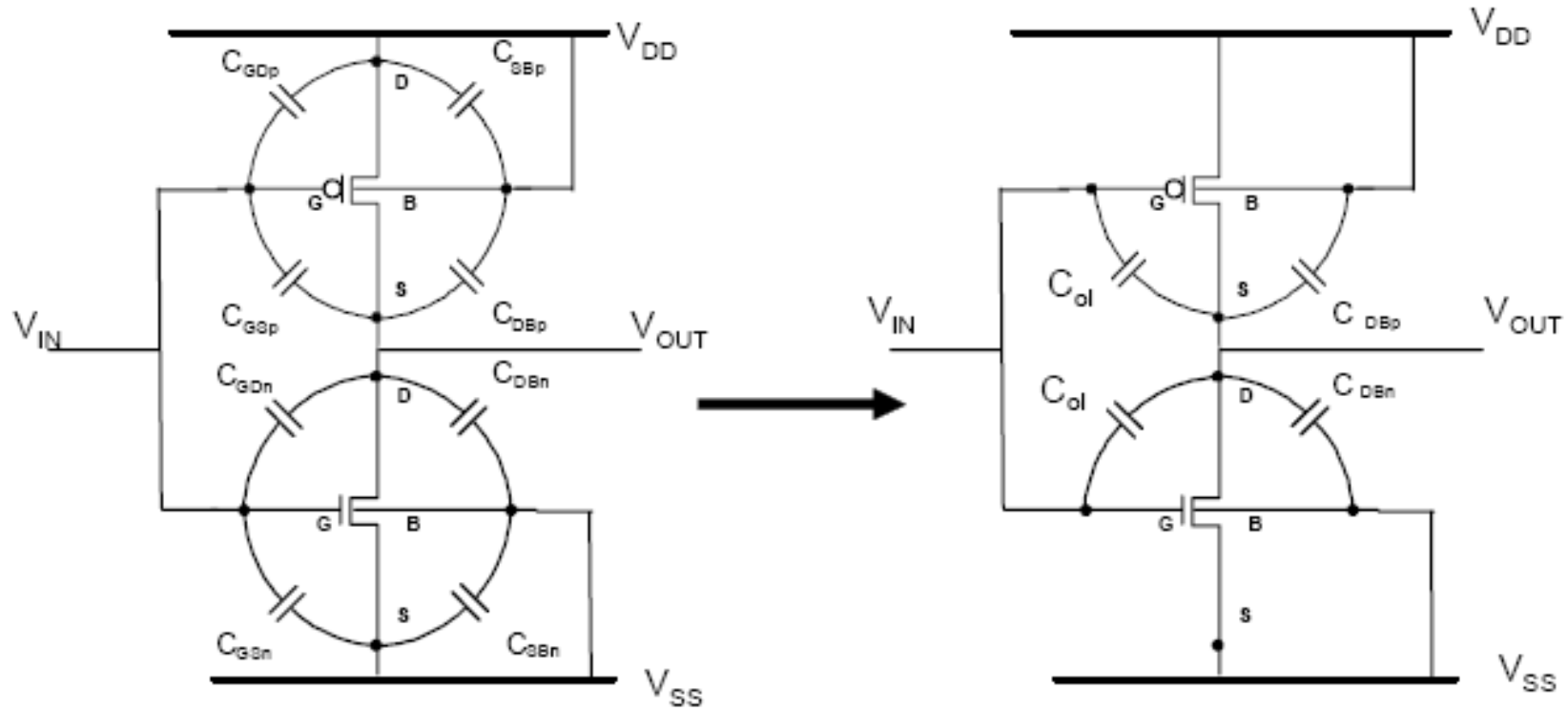

# Self-Capacitance



- ❑ Four main capacitances:  $C_{GS}$ ,  $C_{GD}$ ,  $C_{DB}$ ,  $C_{SB}$ .
- ❑ Eliminate:  $C_{GSn}$ ,  $C_{GSp}$ ,  $C_{SBn}$ , and  $C_{SBp}$ .
- ❑ Apply a step input
  - One transistor is always off and the other is in saturation
  - In either region  $C_{GD}$  is negligible
  - We are left with only the overlap capacitances from gate-to-source and gate-to-drain, and one junction capacitance per device,  $C_{DBn}$  and  $C_{DBp}$ .

# Overlap Capacitance

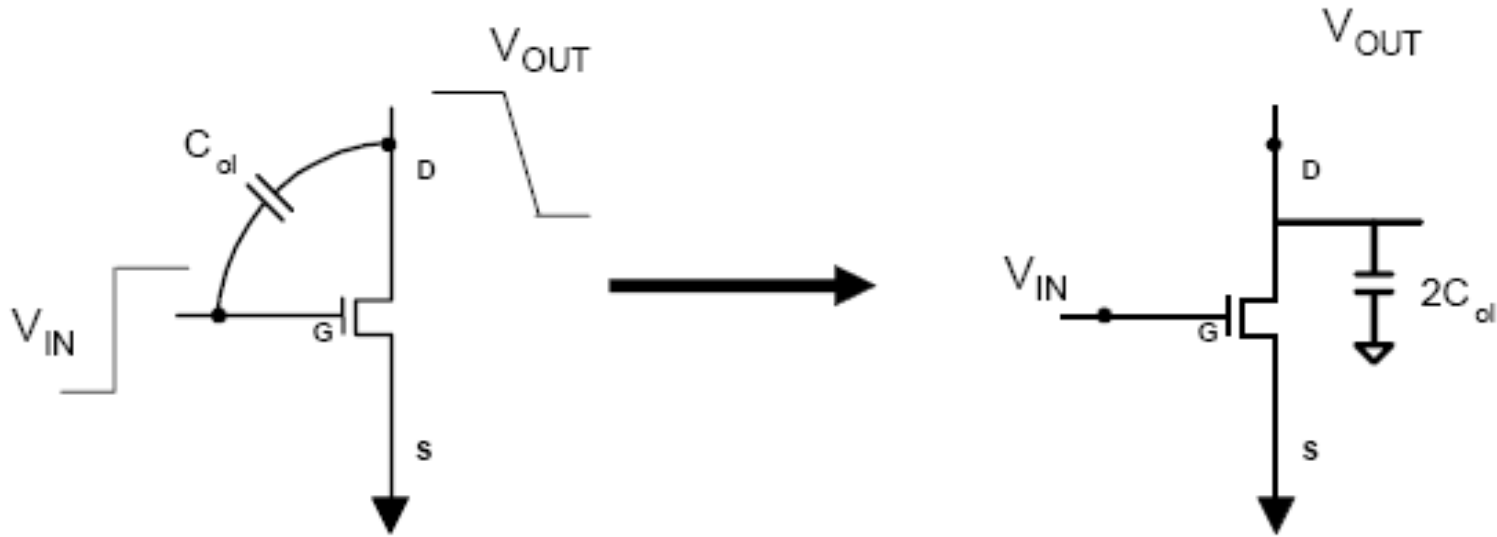

- ❖ *The input makes a transition from 0 to  $V_{DD}$  while the output makes a transition from  $V_{DD}$  to 0.*
- ❖ *The overlap capacitance experiences a voltage swing of  $2V_{DD}$ .*
- ❖ *Model this by assuming that the swing is only  $V_{DD}$  and then double the size of the capacitance and place it at the output.*

# Effect of shared Source and Drain

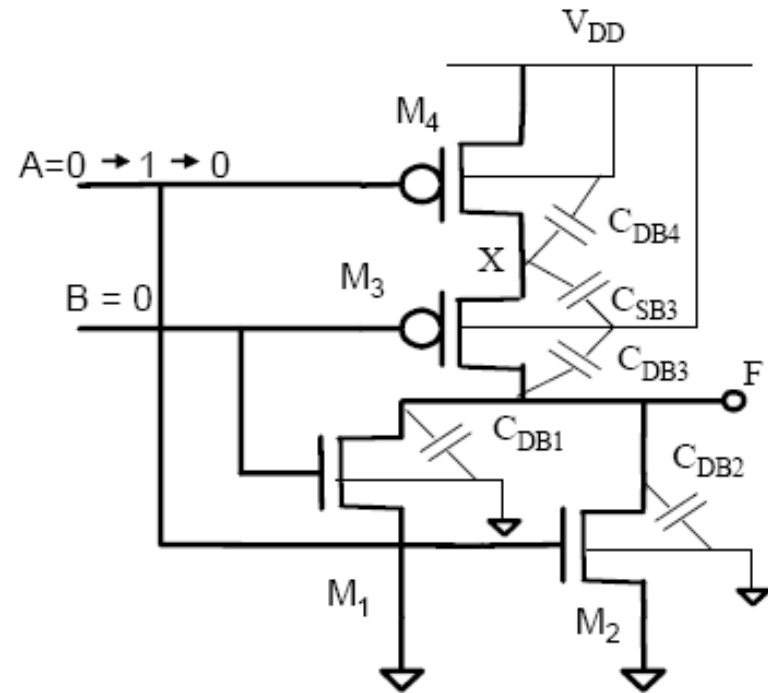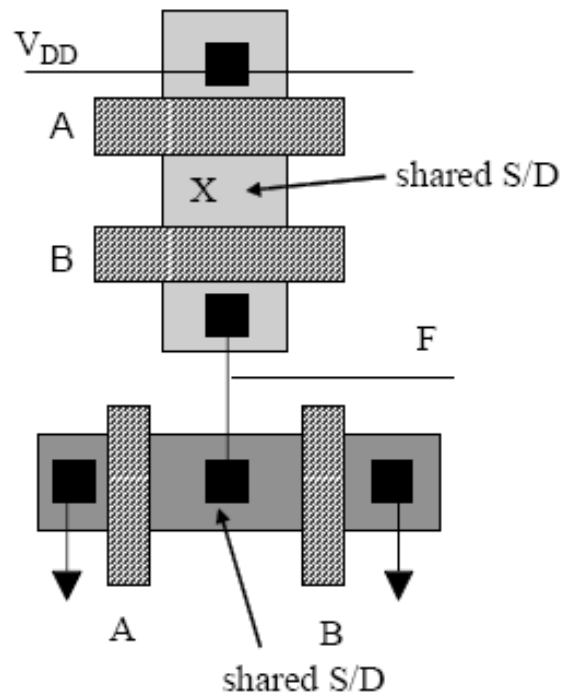

# Shared Source and Drain





- Let's examine the pull-down case
- In the worst-case, input A switches from low to high while B remains low since the capacitances at both the output node and the internal node X must also be discharged.

$$\begin{aligned} C_{self} &= \underbrace{C_{DB1} + C_{DB2}}_{n^+ \text{ shared } S/D} + C_{DB3} + \underbrace{C_{SB3} + C_{DB4}}_{p^+ \text{ shared } S/D} \\ &= C_{DB12} + C_{DB3} + C_{SDB34} \end{aligned}$$


*Note: If A stays low but B goes high, the only output capacitances to be charged are  $C_{DB12} + C_{DB3}$ .*

*If we assume that input A switches from high to low while input B remains low, then the total capacitance to be charged is given by the above equation*

# Switch Delay Model

    


# Input Pattern Effects on Delay

 

- Delay is dependent on the **pattern** of inputs
- Low to high transition
  - both inputs go low
    - delay is  $0.69 R_p/2 C_L$
  - one input goes low
    - delay is  $0.69 R_p C_L$
- High to low transition
  - both inputs go high
    - delay is  $0.69 2R_n C_L$





# Delay Dependence on Input Patterns

 

NMOS =  $0.5\mu\text{m}/0.25\mu\text{m}$   
PMOS =  $0.75\mu\text{m}/0.25\mu\text{m}$   
 $C_L = 100\text{ fF}$

# Fan-In Considerations

 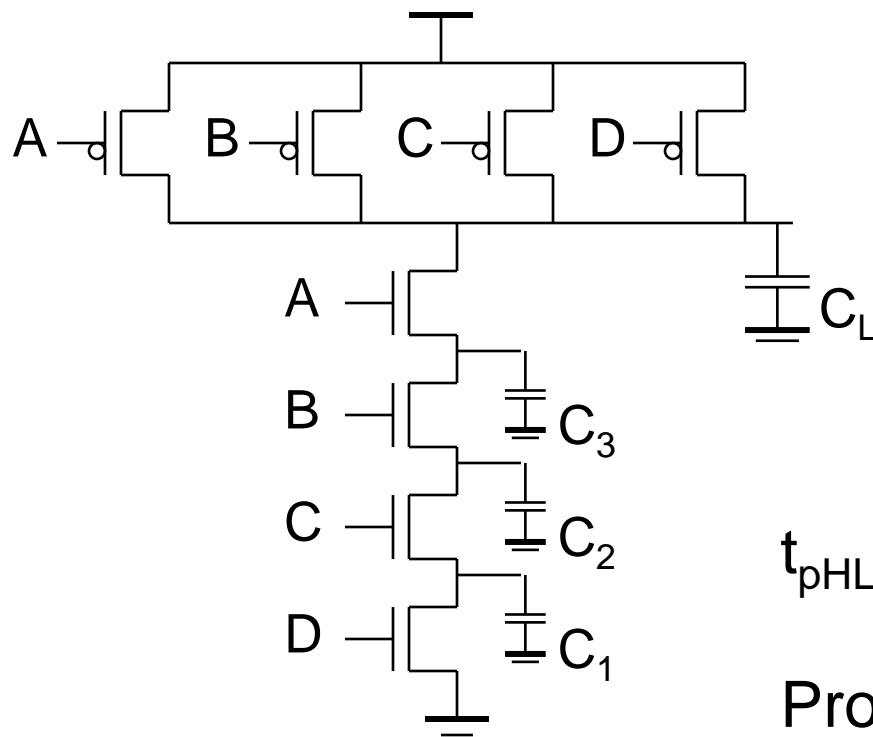

Distributed RC model  
(Elmore delay)

$$t_{pHL} = 0.69 R_{eqn}(C_1 + 2C_2 + 3C_3 + 4C_L)$$


Propagation delay deteriorates rapidly as a function of fan-in – **quadratically** in the worst case.

# *$t_p$ as a Function of Fan-In and Fan-Out*

- Fan-in: **quadratic** due to increasing resistance and capacitance
- Fan-out: each additional fan-out gate adds **two** gate capacitances to  $C_L$
 
# Fast Complex Gates: Design Technique 1

- Transistor sizing
  - as long as fan-out capacitance dominates
- Progressive sizing




Distributed RC line

$M1 > M2 > M3 > \dots > MN$   
(the FET closest to the output is the smallest)


Can reduce delay by more than 20%; decreasing gains as technology shrinks

# Fast Complex Gates: Design Technique 2

## □ Transistor ordering

 

 delay determined by time to discharge  $C_L$ ,  $C_1$  and  $C_2$



delay determined by time to discharge  $C_L$


# *Propagation Delay Depends on the order of arrivals of the inputs*

- ❑ In a series stack, the delay increases as the late arriving input is further from the output.
- ❑ Reorder the inputs such that the earliest signals arrive lower in the stack and the latest signals arrive near the top of the stack.
- ❑ Each device is progressively larger as we move from the output to ground
- ❑ Each one must discharge a progressively larger capacitance.

# Fast Complex Gates: Design Technique 3


## □ Alternative logic structures

$$F = ABCDEFGH$$

 
 
# *Fast Complex Gates: Design Technique 4*

- Isolating fan-in from fan-out using buffer insertion





# *Fast Complex Gates: Design Technique 5*

- Reducing the voltage swing
  - linear reduction in delay
  - also reduces power consumption
- But the following gate is much slower!
- Or requires use of “sense amplifiers” on the receiving end to restore the signal level (memory design)