


*EE 466/586*  
*VLSI Design*

**Partha Pande**  
**School of EECS**  
**Washington State University**  
**pande@eecs.wsu.edu**

# **Lecture 11**

## ***Propagation delay***

# Optimizing Paths with NANDs and NORs


 


$$total\_delay = \sum_{j-1}^i \tau_{nand} \left( \frac{C_{j+1}}{C_j} + \gamma_{nand} \right)$$

- $\tau_{nand}$  is the intrinsic time constant for the NAND gate
- $\gamma_{NAND}$  is the ratio of the self-capacitance to the input gate capacitance.
- For a chain of NOR gates


$$total\_delay = \sum \tau_{nor} \left( \frac{C_{j+1}}{C_j} + \gamma_{nor} \right)$$

# *Intrinsic Time constants*

  

❑ *Follow board notes*

# Mixed Gates in a Logic path

 

$$total\_delay = \tau_{nand} \left( \frac{C_{j+1}}{C_j} + \gamma_{nand} \right) + \tau_{inv} \left( \frac{C_{j+2}}{C_{j+1}} + \gamma_{inv} \right) + \tau_{nor} \left( \frac{C_{j+3}}{C_{j+2}} + \gamma_{nor} \right)$$

- Optimization of Delay
- Follow board notes


# Minimum Delay

$$\tau_{nand} FO_j = \tau_{inv} FO_{j+1}$$

- ❑ *The delay is minimized when the  $\tau \times FO$  of a given gate is equal to  $\tau \times FO$  of the next gate*
- ❑ *Fanout portions of the delays must be equal to reach the optimum solution.*
- ❑ *Follow board notes*
 
# Example

- Find the device sizes that optimizes the delay through the indicated path



- Follow board notes

# Logical Effort

- Logical Effort (LE) is the ratio of the intrinsic time constant for a gate to the intrinsic time constant of an inverter.

$$\frac{total\_delay}{\tau_{inv}} = \frac{\tau_{nand}}{\tau_{inv}} \left( \frac{C_{j+1}}{C_j} + \gamma_{nand} \right) + \frac{\tau_{inv}}{\tau_{inv}} \left( \frac{C_{j+2}}{C_{j+1}} + \gamma_{inv} \right) + \frac{\tau_{nor}}{\tau_{inv}} \left( \frac{C_{j+3}}{C_{j+2}} + \gamma_{nor} \right)$$

$$D = (LE_{nand} FO_1 + P_{nand}) + (LE_{inv} FO_2 + P_{inv}) + (LE_{nor} FO_3 + P_{nor})$$

$$D = \sum (LE \times FO + P)$$

- Follow board notes.




# Delay in a Logic Gate

Gate delay:

$$d = h + p$$

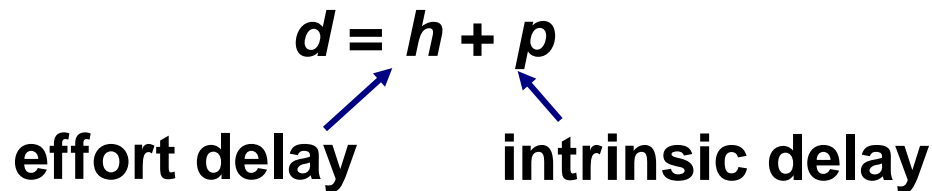
effort delay                  intrinsic delay



Effort delay:

$$h = g f$$

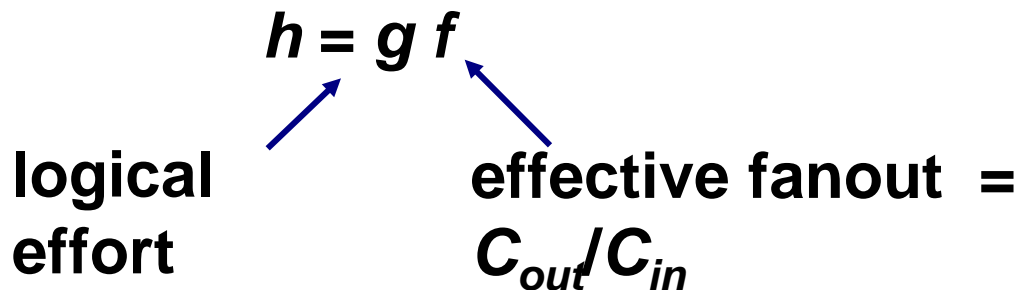logical effort                  effective fanout =  $C_{out}/C_{in}$



Logical effort is a function of topology, independent of sizing  
Effective fanout (electrical effort) is a function of load/gate size


# *Logical Effort*

- ❑ Inverter has the smallest logical effort and intrinsic delay of all static CMOS gates
- ❑ Logical effort of a gate presents the ratio of its input capacitance to the inverter capacitance when sized to deliver the same current
- ❑ Logical effort increases with the gate complexity


# *LE Calculation*

- ❑ Set the delays of the inverter and the gate to be the same; then, take the ratio of the input capacitances.
- ❑ Set the input capacitances to be same; then, take the delay ratio

 
# Logical efforts for gates with equal delays



LE=1

 


LE = 4/3

 


LE=5/3

 
# Logical Effort Using Equal Input Capacitances



$$LE=1$$

 

$$LE = 4/3$$

 

$$LE=5/3$$

□ *Why NAND is better?*

# *LE of simple gates*

Type of Gate	1 input	2 inputs	3 inputs	4 inputs
Inverter	1	-	-	-
NAND	-	4/3	5/3	6/3
NOR	-	5/3	7/3	9/3

# Computation of parasitics

Type of Gate	1 input	2 inputs	3 inputs	4 inputs
Inverter	$P_{inv}=1/2$	-	-	-
NAND	-	$2P_{inv}=1$	$3P_{inv}=3/2$	$4P_{inv}=2$
NOR	-	$3P_{inv}=3/2$	$4.5P_{inv}=9/4$	$6P_{inv}=3$

❑ *Follow board notes*