


EE 466/586
VLSI Design

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Lecture 14


Pass Transistor Logic

Pass Transistor Logic

 



- **N transistors**
- **No static consumption**

Example: AND Gate

 


Issues with Pass Transistor Logic

  - ❑ Threshold drop
- ❑ Capacitive feed through
- ❑ Charge sharing
- ❑ Follow board notes




NMOS Only Logic: Level Restorer

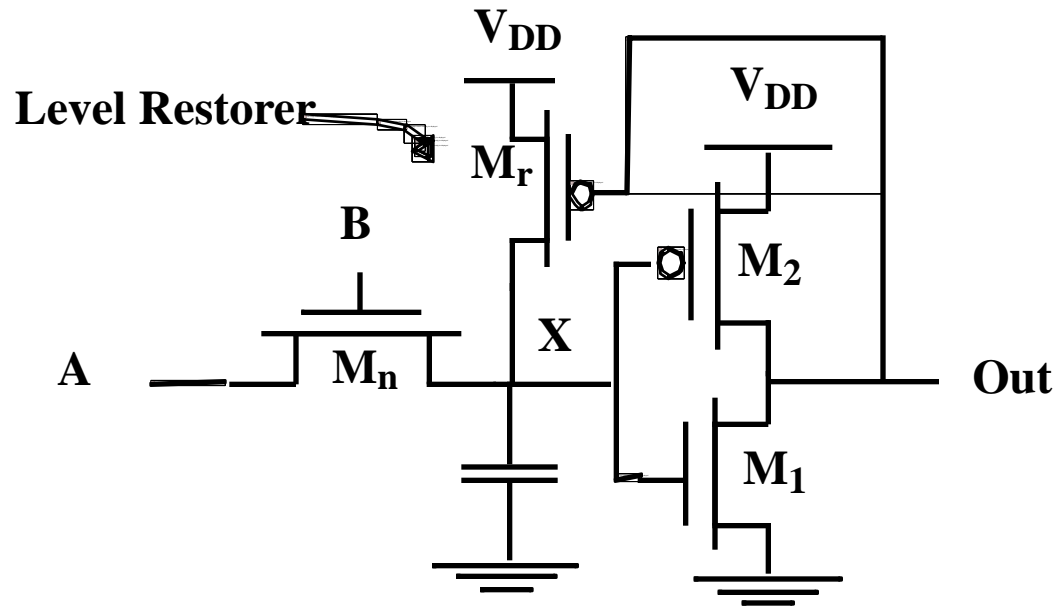


- Advantage: Full Swing
- Restorer adds capacitance, takes away pull down current at X
- Ratio problem

Restorer Sizing

 



- Upper limit on restorer size
- Pass-transistor pull-down can have several transistors in stack

 Solution 2: Single Transistor Pass Gate with $V_T=0$



WATCH OUT FOR LEAKAGE CURRENTS




Complementary Pass Transistor Logic

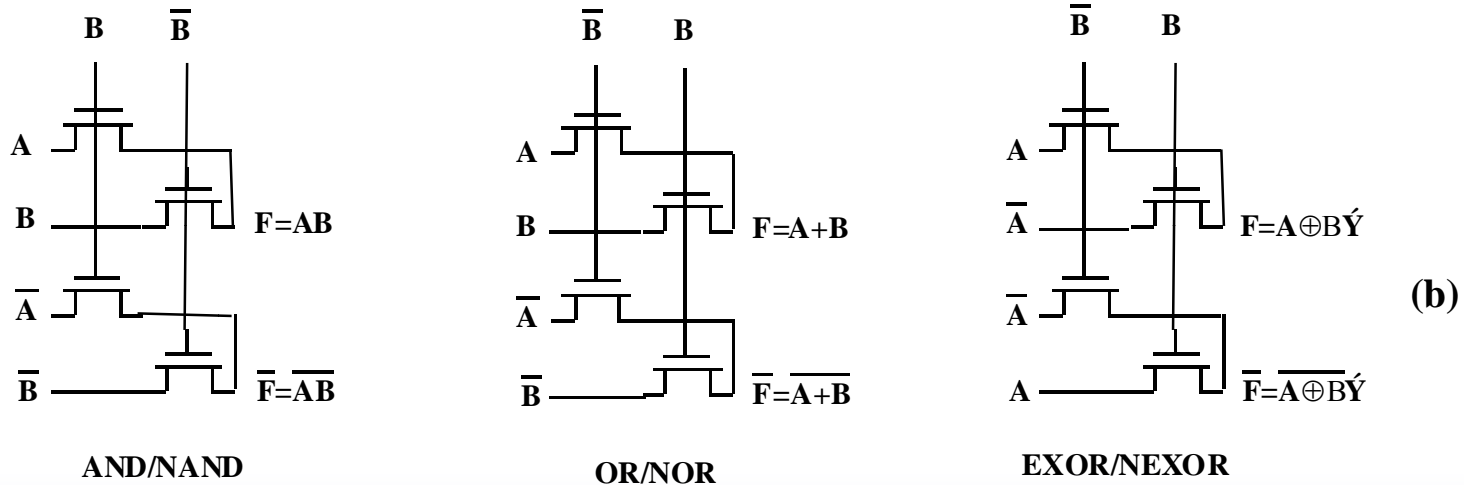 

Advantages of CPL



- Circuits are *Differential*
- Static Gate. Advantageous for noise resilience
- Modular design

Solution 3: Transmission Gate

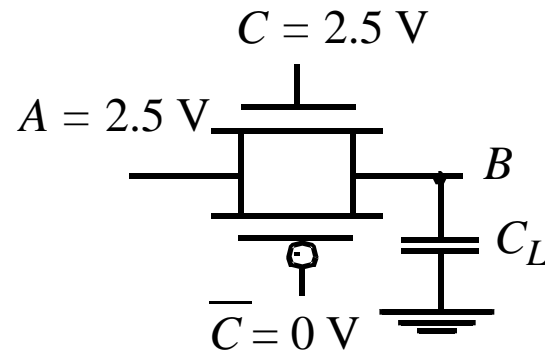  

Resistance of Transmission Gate


□ Follow board notes

  


Transfer gate Capacitances

- Follow board notes


Delay in Transmission Gate Networks

 

(a)

 


(b)

 

(c)


Pass-Transistor Based Multiplexer

 


- The control signal S turns the transfer gates on and off depending on its value.
- When $s=1$, the upper transfer gate is on and that allows A to follow to the output

- Implement the Multiplexer with static CMOS and compare with this

Transmission Gate XOR

 

Transmission Gate Full Adder

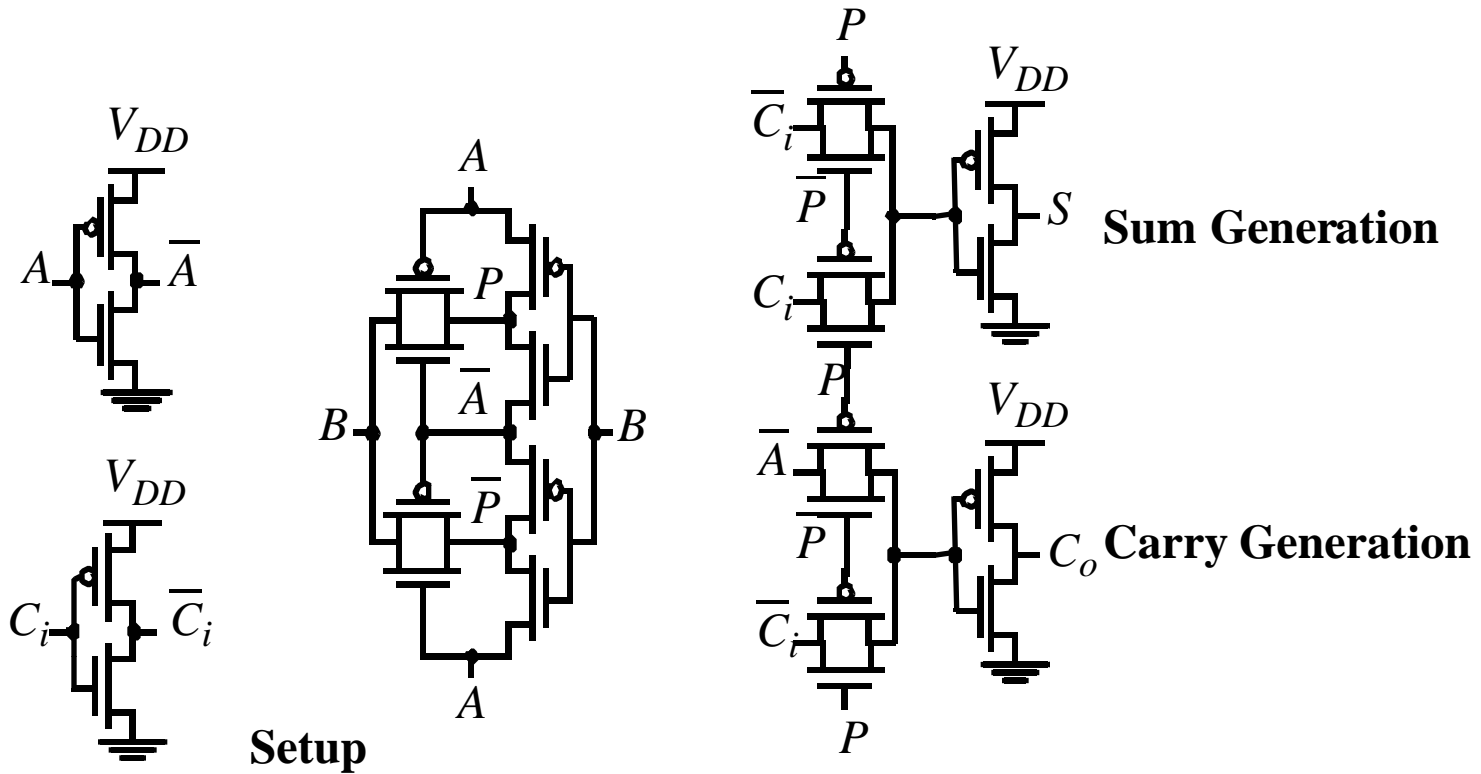

Similar delays for sum and carry