
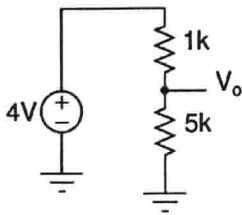


EE 311 Fundamentals Exam

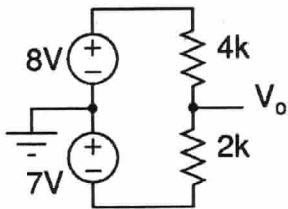


1. What is the voltage V_o ?

$V_o = \underline{\hspace{2cm}}$




2. What is V_o ?

$V_o = \underline{\hspace{2cm}}$

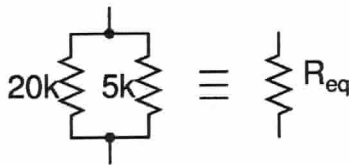


3. What is the equivalent resistance R_{eq} ?

$R_{eq} = \underline{\hspace{2cm}}$

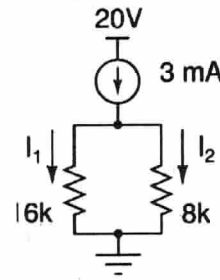

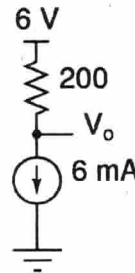
4. What are the currents I_1 and I_2 ?

$I_1 = \underline{\hspace{1cm}} \quad I_2 = \underline{\hspace{1cm}}$




5. What is V_o ?

$V_o = \underline{\hspace{2cm}}$

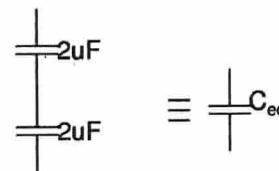


6. What is the equivalent capacitance, C_{eq} ?

$C_{eq} = \underline{\hspace{2cm}}$

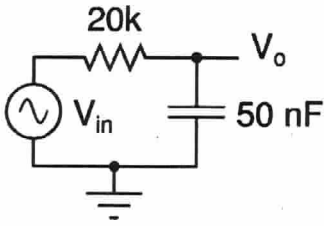


7. At what frequency, f_{3dB} , is the magnitude of V_o equal to $0.707 V_{in}$?

$f_{3dB} = \underline{\hspace{2cm}}$

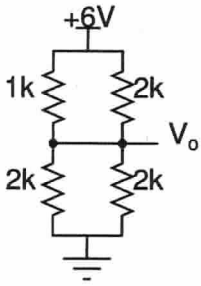


8. What is the voltage V_o ?

$V_o = \underline{\hspace{2cm}}$

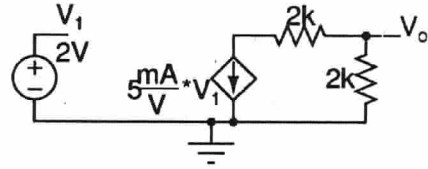

9. What is the output voltage, V_o ?

$V_o = \underline{\hspace{2cm}}$

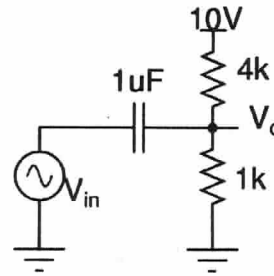

10. A) What is the voltage V_o when the frequency of V_{in} is zero?

$V_o = \underline{\hspace{2cm}}$

b) Is the circuit: (Circle one)

a low pass filter

a high pass filter

a band pass filter

none of the above?