



1. For the circuit shown, determine  $I_E$  and  $V_B$  for  $\beta = 59$  and  $|V_{BE}| = 0.6V$ .

$I_E = \underline{\hspace{2cm}} (7)$

$V_B = \underline{\hspace{2cm}} (3)$