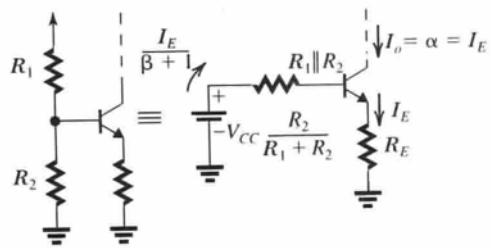


6.138




$$V_{CC} \cdot \frac{R_2}{R_1 + R_2} = \frac{I_E}{\beta + 1} (R_1 \parallel R_2) + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE}}{R_E + \frac{(R_1 \parallel R_2)}{\beta + 1}}$$

Thus,

$$I_O = \alpha I_E = \frac{\alpha \cdot \left[\frac{V_{CC} R_2}{R_1 + R_2} - V_{BE} \right]}{R_E + \frac{(R_1 \parallel R_2)}{\beta + 1}}$$

6.142

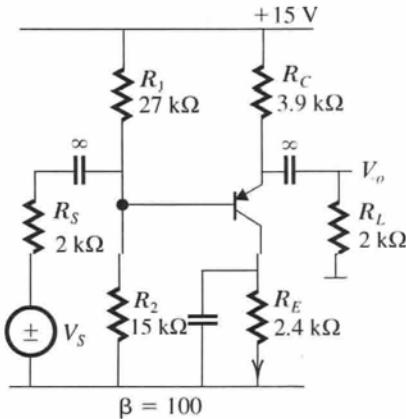

$$R_1 \parallel R_2 = 9.64 \text{ k}\Omega$$

$$V_{BB} = \frac{15 \times R_2}{R_1 + R_2} = 5.36 \text{ V}$$

$$I_E = \frac{V_{BB} - 0.7}{2.4 + \frac{9.64}{101}} = 1.87 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.99 I_E}{V_T} = 74 \text{ V/V}$$

$$r_o = \frac{V_A}{I_C} = 54 \text{ k}\Omega$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{74} = 1.35 \text{ k}\Omega$$

$$R_C \parallel R_L = \frac{3.9 \times 2}{5.9} = 1.32 \text{ k}\Omega \ll r_o$$

Thus we can neglect r_o

$$I_c = 0.99 \times I = 1.68 \text{ mA}$$

$$R_{in} = (R_1 \parallel R_2) | r_\pi = 1.18 \text{ k}\Omega$$

$$R_O = r_o \parallel R_C \approx 1.32 \text{ k}\Omega$$

$$\frac{v_o}{v_i} = -\frac{R_{in}}{R_{in} + R_s} \times g_m (r_o \parallel R_C \parallel R_L)$$

$$R_S = -\frac{1.18}{3.18} \times 74 \times 1.29 \\ = -35.4 \text{ V/V}$$

