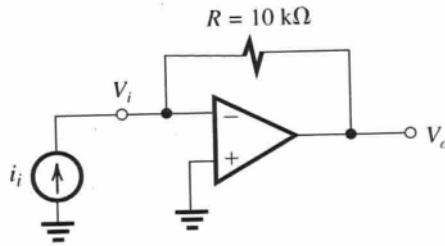


Ex: 2.5



From Table 1.1 we have:

$$R_m = \left. \frac{V_o}{i_i} \right|_{i_o = 0}, \text{ i.e., output is open circuit}$$

The negative input terminal of the op amp, i.e.,  $V_i$  is a virtual ground, thus  $V_i = 0$


$$V_o = V_i - R i_i = 0 - R i_i = -R i_i$$

$$\begin{aligned} R_m &= \left. \frac{V_o}{i_i} \right|_{i_o = 0} = -\frac{R i_i}{i_i} = -R \Rightarrow R_m = -R \\ &= -10 \text{ k}\Omega \end{aligned}$$

$$R_i = \frac{V_i}{i_i} \text{ and } V_i \text{ is a virtual ground } (V_i = 0),$$

$$\text{thus } R_i = \frac{0}{i_i} = 0 \Rightarrow R_i = 0 \Omega$$

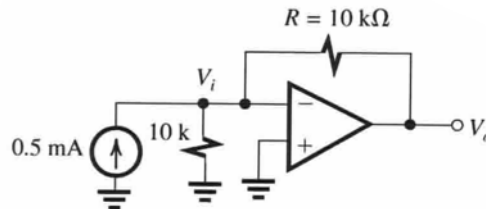Since we are assuming that the op amp in this transresistance amplifier is ideal, the op amp has zero output resistance and therefore the output resistance of this transresistance amplifier is also zero. That is  $R_o = 0 \Omega$ .



Connecting the signal source shown in Figure E2.5 to the input of this amplifier we have:

$V_i$  is a virtual ground that is  $V_i = 0$ , thus the current flowing through the  $10 \text{ k}\Omega$  resistor connected between  $V_i$  and ground is zero. Therefore

$$\begin{aligned} V_o &= V_i - R \times 0.5 \text{ mA} = 0 - 10 \text{ K} \times 0.5 \text{ mA} \\ &= -5 \text{ V} \end{aligned}$$

**2.8**

Circuit	$v_o/v_i$ (V/V)	$R_{in}$ (k $\Omega$ )
a	$\frac{-100}{10} = -10$	10
b	-10	10
c	-10	10
d	-10	10

virtual ground no current in 10 k $\Omega$


**2.16**

$$\frac{v_o}{v_i} = \frac{10 \text{ k}}{1 \text{ k}} = -10 \text{ V/V}$$

$$\begin{aligned} v_o &= -10 v_i \\ &= -10 \times (0.5) \\ &= -5 \text{ V/V} \end{aligned}$$

In the figure
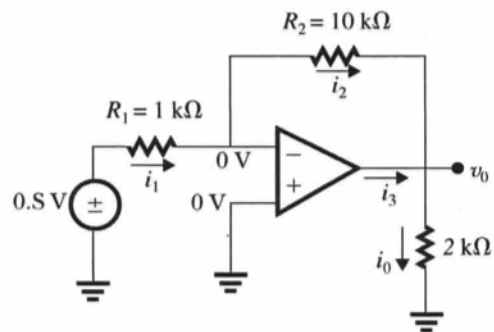
$$i_o = \frac{v_o}{2 \text{ k}\Omega} = \frac{-5}{2 \text{ k}\Omega} = -2.5 \text{ mA}$$



$$\begin{aligned} i_1 = i_2 &= \frac{0 - (v_o)}{10 \text{ k}\Omega} = \frac{0 - (-5)}{10 \text{ k}\Omega} \\ &= +0.5 \text{ mA} \end{aligned}$$

$$\begin{aligned} i_3 = i_o - i_2 &= -2.5 - 0.5 \\ &= -3 \text{ mA} \end{aligned}$$

This additional current is supplied by the op amp.