

**2.49**

$$v_+ = v_f \frac{R_4}{R_3 + R_4} = v$$

$$\frac{v}{R_1} = \frac{v_o - v_-}{R_2} \Rightarrow v_o = v_- \left( 1 + \frac{R_2}{R_1} \right)$$

From the two above equations:

$$\frac{v_o}{v_f} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) = \frac{1 + R_2/R_1}{1 + R_3/R_4}$$

**2.50**

Refer to Fig. 2.50. Setting  $v_2 = 0$ , we obtain the output component due to  $v_1$  as:

$$v_{o1} = -20 v$$

Setting  $v_1 = 0$ , we obtain the output component due to  $v_2$  as:

$$v_{o2} = v_2 \left( 1 + \frac{20R}{R} \right) \left( \frac{20R}{20R + R} \right) = 20 v_2$$

The total output voltage is:

$$v_o = v_{o1} + v_{o2} = 20 (v_2 - v_1)$$

For  $v_1 = 10 \sin 2\pi \times 60t - 0.1 \sin (2\pi \times 1000 t)$

$$v_2 = 10 \sin 2\pi \times 60t + 0.1 \sin (2\pi \times 1000 t)$$

$$v_o = 4 \sin (2\pi \times 1000 t)$$


**2.62**

Refer to fig P2.62:


Considering that  $v_- = v_+$ :

$$v_1 + \frac{v_O - v_1}{2} = \frac{v_2}{2} \Rightarrow v_O = v_2 - v_1$$
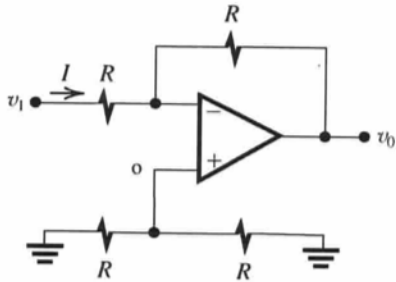
$$v_1 \text{ only: } R_I = \frac{v_1}{I} = R$$



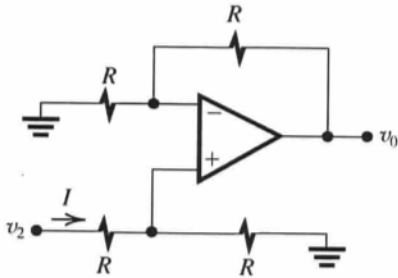
$$v_2 \text{ only: } R_I = \frac{v_2}{I} = 2R$$



$v_S$  between 2 terminals:

$$R_I = \frac{v}{I} = 2R$$

$$v_+ = v_- = 0$$

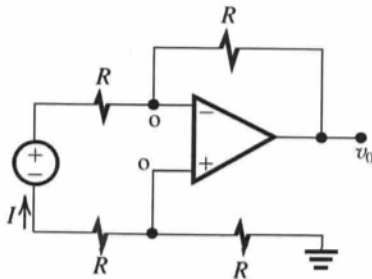

$v_3$  connected to both  $v_1$  &  $v_2$ :

$$R_I = \frac{v}{I} = R$$

$$v_+ = v_- = \frac{v_i}{2}$$

