

2.108

Eq. 2.25:

$$A = \frac{A_O}{1 + jw/w_b} \Rightarrow |A| = \frac{|A_O|}{\sqrt{1 + \left(\frac{f}{f_b}\right)^2}}$$

$$A_O = 80 \text{ dB}, A = 40 \text{ dB} @ f = 100 \text{ kHz}$$

$$20 \log \sqrt{1 + \left(\frac{f}{f_b}\right)^2} = 20 \log \frac{|A_O|}{|A|} = 20 \log A_O - 20 \log A$$

$$= 86 - 40 = 46 \text{ dB}$$

$$1 + \left(\frac{100 \text{ kHz}}{f_b}\right)^2 = (199.5)^2 \Rightarrow f_b = 0.501 \text{ kHz}$$

$$f_b = 501 \text{ Hz}$$

$$f_t = A_O f_b = 1.995 \times 10^4 \times 501$$

$$\overbrace{\quad\quad\quad}^{86 \text{ dB}}$$

$$= 9.998 \text{ MHz} \simeq 10 \text{ MHz}$$

2.110

we have:

$$A_o(\text{dB}) = 20 \text{ dB} + A(\text{dB})$$

$$20 \text{ dB} = 20 \log 10 \Rightarrow A_o = 10 \text{ A}$$

$$\text{a) } A_o = 10 \times 3 \times 10^5 = 3 \times 10^6 \text{ Hz V/V}$$

$$A = \frac{A_o}{1 + jf/f_b} \Rightarrow \left| 1 + j\frac{f}{f_b} \right| = \frac{A_o}{A} = 10 \Rightarrow$$

$$\frac{6 \times 10^2}{f_b} = \sqrt{99}$$

$$\Rightarrow f_b = 60.3 \text{ Hz}$$

$$f_t = A_o f_b = 3 \times 10^6 \times 60.3 = 180.9 \text{ MHz}$$

b)

$$A = 50 \times 10^5 \times 10 \text{ V/V} \Rightarrow A_o = 10 \times 50 \times 10^5$$

$$= 50 \times 10^6 \text{ V/V}$$

$$\left| 1 + j\frac{f}{f_b} \right| = \frac{A_o}{A} = 10 \Rightarrow \frac{10 \text{ Hz}}{f_b} = \sqrt{99} \Rightarrow f_b = 1 \text{ Hz}$$

$$f_t = A_o f_b = 50 \text{ MHz}$$

$$\text{c) } A = 1500 \text{ V/V} \Rightarrow A_o = 1500 \text{ V/V}$$

$$\left| 1 + j\frac{f}{f_b} \right| = 10 \Rightarrow \frac{0.1 \times 10^9}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ kHz}$$

$$f_t = 15000 \times 10 \text{ K} = 150 \text{ MHz}$$

$$\text{d) } A_o = 10 \times 100 = 1000 \text{ V/V}$$

$$\left| 1 + j\frac{f}{f_b} \right| = 10 \Rightarrow \frac{0.1 \times 10^9}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ MHz}$$


$$f_t = 1000 \times 10 \text{ MHz} = 10 \text{ GHz}$$

$$\text{e) } A = 25 \text{ V/mV} \times 10 = 25 \times 10^4 \text{ V/V}$$

$$\left| 1 + j\frac{f}{f_b} \right| = 10 \Rightarrow \frac{2.5 \text{ kHz}}{f_b} = \sqrt{99} \Rightarrow f_b = 2.51 \text{ kHz}$$

$$f_t = A_o f_b = 25 \times 10^4 \times 2.51 \times 10^3 = 627.5 \text{ MHz}$$

2.86

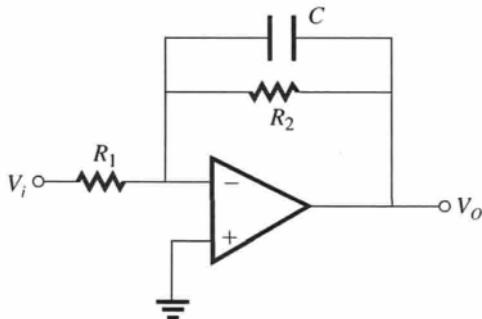

Let $Z_2 = R_2 \parallel \frac{1}{sC}$ and $Z_1 = R_1$

$$\begin{aligned}\frac{v_o}{v_i} &= -\frac{Z_2}{Z_1} = -\frac{Y_1}{Y_2} = -\frac{1/R_1}{\frac{1}{R_2} + sC} \\ &= -\frac{(R_2/R_1)}{1+sCR_2}\end{aligned}$$

This function is of a STC, low pass circuit having


a dc gain of $-\frac{R_2}{R_1}$ and 3-dB frequency

$$\omega_0 = \frac{1}{CR_2}$$

$$R_{in} = R_1 = 10 \text{ k}\Omega$$

$$\text{dc gain} = 20 \text{ dB} = 10$$
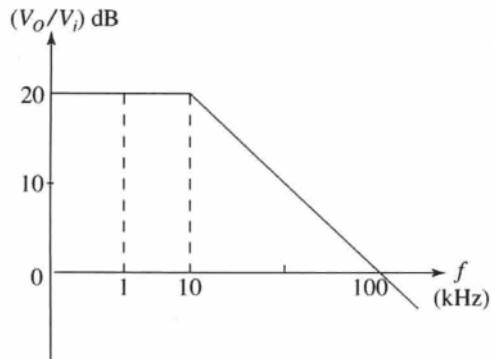
$$\therefore 10 = \frac{R_2}{R_1} \Rightarrow R_2 = 10 R_1 = 100 \text{ k}\Omega$$



3dB frequency at 10 kHz

$$\therefore \omega_0 = 2\pi \times 10 \times 10^3 = \frac{1}{CR_2}$$

$$C = \frac{1}{2\pi \times 10 \times 10^3 \times 100 \text{ K}} = 0.5 \text{ nF}$$

Unity gain frequency at 100 kHz