

2.114

$$\text{Gain} = 1 + \frac{R_2}{R_1} = 96 \text{ V/V}$$

$$f_{3\text{dB}} = 8 \text{ kHz}$$

$$f_t = 96 \times 8 = 768 \text{ kHz}$$

$$\text{for } f_{3\text{dB}} = 24 \text{ kHz}$$

$$\text{Gain} = \frac{768}{24} = 32 \text{ V/V}$$

2.117

a) Assume two identical stages, each with a gain

$$\text{function: } G = \frac{G_o}{1 + j\frac{w}{w_1}} = \frac{G_o}{1 + jf/f_1}$$

$$G = \frac{G_o}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$

$$\text{overall gain of the cascade is } \frac{G_o^2}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$

The gain will drop by 3db when:

$$1 + \left(\frac{f_{3\text{db}}}{f_1}\right)^2 = \sqrt{2}, \text{ Note } 3\text{db} = 20\log \sqrt{2}$$

$$f_{3\text{db}} = f_1 \sqrt{\sqrt{2} - 1}$$

$$\text{b) } 40 \text{ db} = 20 \log G_o \Rightarrow G_o = 100 = 1 + \frac{R_2}{R_1}$$

$$f_{3\text{db}} = \frac{f_t}{1 + \frac{R_2}{R_1}} = \frac{1 \text{ MHz}}{100} = 10 \text{ kHz}$$

c) Each stage should have 20db gain or

$$1 + \frac{R_2}{R_1} = 10 \text{ and therefore a 3db frequency of:}$$

$$f_1 = \frac{10^6}{10} = 10^5 \text{ Hz.}$$

$$\text{The overall } f_{3\text{db}} = 10^5 \sqrt{\sqrt{2} - 1} = 64.35 \text{ kHz}$$

which is 6 time greater than the bandwidth achieved using single op amp.

(case b above)