

Ex: 2.29

For the input voltage step of magnitude V the output waveform will still be given by the exponential waveform of equation(2.40)

If $w_t V \leq SR$

$$\text{That is } V \leq \frac{SR}{w_t} \Rightarrow V \leq \frac{SR}{2\pi f_t}$$

$V \leq 0.16 \text{ V}$, thus, the largest possible input voltage step is 0.16 V .

From Appendix F we know that the 10% to 90% rise time of the output waveform of the form of

$$\text{equation (2.40) is } t_r \simeq 2.2 \frac{1}{w_t}$$

Thus, $t_r \simeq 0.35 \mu\text{s}$

If an input step of amplitude 1.6 V (10 times as large compared to the previous case) is applied, the the output is slew-rate limited and is linearly rising with a slope equal to the slew-rate, as shown in the following figure.

2.123



Op Amp slew rate = $10 \text{ V}/\mu\text{s}$

For the input pulse to rise 5V_i , it will take

$$\frac{5}{10} = 0.5 \mu\text{s}$$

\therefore The minimum pulse width = $W = 0.5 \mu\text{s}$

The output will be a triangular with $10 \text{ V}/\mu\text{s}$ slew rate

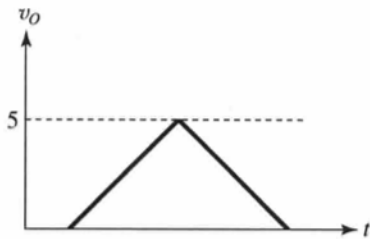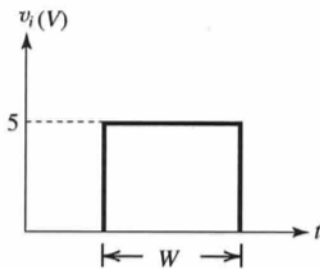**2.126**

$$v_o = 10 \sin \omega t \Rightarrow \frac{dv_o}{dt} = 10\omega \cos \omega t \Rightarrow \left. \frac{dv_o}{dt} \right|_{\max} = 10\omega$$

The highest frequency at which this output is possible is that for which:

$$\begin{aligned} \left. \frac{dv_o}{dt} \right|_{\max} &= \text{SR} \Rightarrow 10\omega_{\max} = 60 \times 10^6 \Rightarrow \omega_{\max} \\ &= 6 \times 10^5 \\ \Rightarrow f_{\max} &= 45.5 \text{ kHz} \end{aligned}$$