
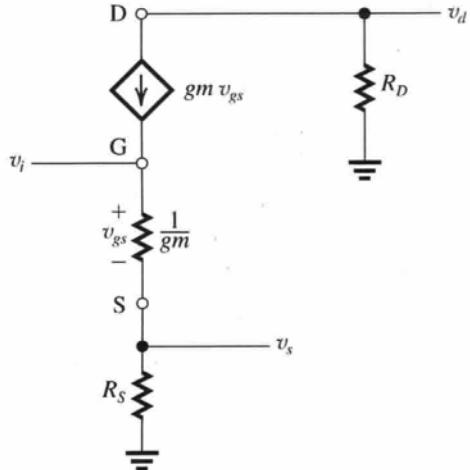


5.76

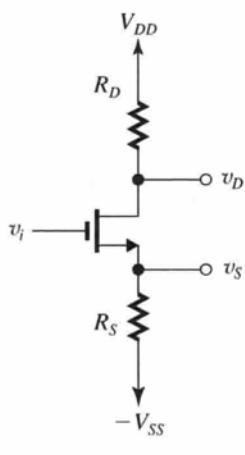

$$v_i = (g_m v_{gs}) \left( \frac{1}{g_m} + R_S \right)$$


$$v_d = -g_m v_{gs} R_D$$

$$v_s = +g_m v_{gs} R_S$$

$$\therefore \frac{v_s}{v_i} = \frac{R_S}{\frac{1}{g_m} + R_S} = \frac{+g_m R_S}{1 + g_m R_S}$$

$$\frac{v_d}{v_i} = \frac{-R_D}{\frac{1}{g_m} + R_S} = \frac{-g_m R_D}{1 + g_m R_S}$$

5.77

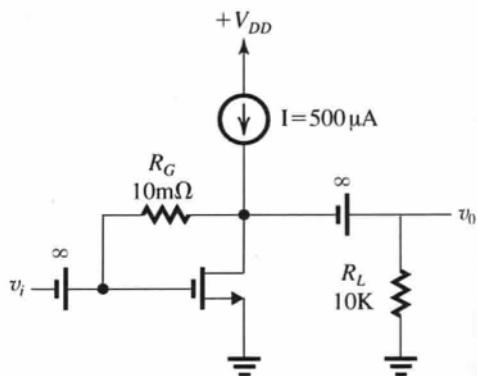

$$V_t = 0.5V.$$

$$V_A = 50 V.$$

$$\text{Given } V_{DS} = V_{GS} = 1 V.$$

$$V_{0V} = 0.5V., g_m = \frac{2I_D}{V_{0V}} = 2 \text{ mS}$$

**Ex: 5.31**

CD (source follower)

$$R_{\text{out}} = 200 \Omega = \frac{1}{g_m} \Rightarrow g_m = 5 \text{ mA/V}$$

$$g_m = k_n' \frac{W}{L} V_{OV} = (0.4 \text{ mA/V}^2)$$

$$\left(\frac{W}{L}\right)(0.25 \text{ V}) \Rightarrow \frac{W}{L} = 50$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} V_{OV}^2 = 0.625 \text{ mA}$$

$$G_V = \frac{g_m R_L}{1 + g_m R_L}$$

for  $K < R_L < 10 \text{ K}$ 

$$0.83 < G_V < 0.98$$

**Ex: 5.27**

$$I_D = 0.25 \text{ mA}, V_{ov} = 0.25 \text{ V},$$

$$V_A = 50 \text{ V}$$

$$r_o = \frac{V_A}{I_D} = 200 \text{ k}\Omega$$

$$g_m = \frac{2I_D}{V_{ov}} = 2 \text{ mS}$$

$$R_{in} = \infty$$

$$A_{vo} = -g_m(R_D \parallel r_o) \simeq -g_m R_D = -4$$

$$R_o = R_D \parallel r_o \simeq R_D \equiv 20 \text{ k}\Omega$$

$$A_v = G_V = -g_m(R_D \parallel r_o \parallel R_L) \simeq$$

$$-g_m(R_D \parallel R_L) = -20 \text{ V/V}$$

$$\text{for } \hat{v}_{gs} = (10\%) 2V_{ov} = 0.05 \text{ V.}$$

$$\hat{v}_o = (A_v \hat{v}_{gs}) = 1 \text{ V.}$$