

5.86 R_{in} = depends on biasing

$$\begin{aligned}A_{vo} &= -g_m(r_o \parallel R_D) \\ &= -0.4 \frac{\text{mA}}{\text{V}}(50 \text{ k}\Omega \parallel 6 \text{ k}\Omega) \\ &= -2.14 \text{ V/V}\end{aligned}$$

$$r_o = \frac{V_A}{I_D} = \frac{10 \text{ V}}{0.2 \text{ mA}} = 50 \text{ k}\Omega$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = 0.4 \text{ mA/V}$$

$$R_o = r_o \parallel R_D = 50 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 5.36 \text{ k}\Omega$$

WITH $R_L=10 \text{ k}\Omega$ and assuming losses due to source impedance are negligible

$$\begin{aligned}G_v = A_v &= -g_m(r_o \parallel R_D \parallel R_L) \\ &= -0.4 \frac{\text{mA}}{\text{V}}(5.36 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = -1.40 \text{ V/V}\end{aligned}$$

For a 0.2V peak output, the input must be

$$\frac{0.2 \text{ V}}{1.4} = 0.143 \text{ V peak}$$

$$5.92 \quad R_s = 1 \text{ k}\Omega$$

$$\frac{-g_m R'_L}{1 + g_m R_s} = -15$$

$$-g_m R'_L = -30$$

$$\therefore g_m = \frac{1}{R_s} = 1 \text{ ms}$$

$$\text{for } A_v = -10, \text{ let } R_s = \frac{2}{g_m} = 2 \text{ k}\Omega$$