

EE 311


EXAM 2 (100pts)

October 11, 2013

Name _____



ID _____

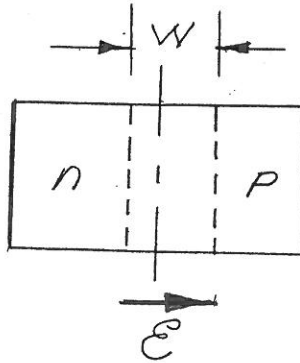- (8pts) 2. The pn junction shown has a depletion width, W , which extends unevenly into the n and p materials.



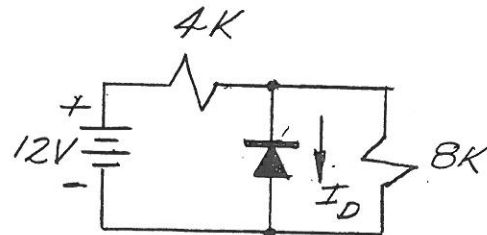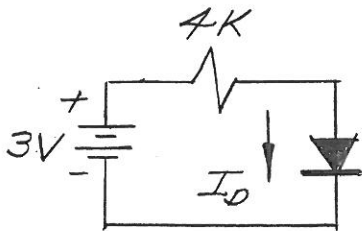- a) Which material is most heavily doped? (n or p) (3pts)
- b) Which net impurity concentration is largest? (N_D or N_A) (2pts)
- c) On the diagram above, indicate the direction of the built-in electric field, E . (3pts)

- (10pts) 3. The diode in the circuits below has a forward voltage drop of $0.6V$ and a breakdown voltage of $4V$. Estimate the current through the diode, I_D .



$$I_D = \underline{0.6 \text{ mA}}$$

(a)

(4pts)

$$I_D = \underline{1.5 \text{ mA}}$$

(b)

(6pts)

EE 311

EXAM 2 (100pts)

Name _____


October 11, 2013

ID _____

(20pts)


4. For the attenuator circuit shown, assume C_1 and C_2 to be very large (∞) coupling capacitors. Assume D_1 and D_2 are identical diodes.

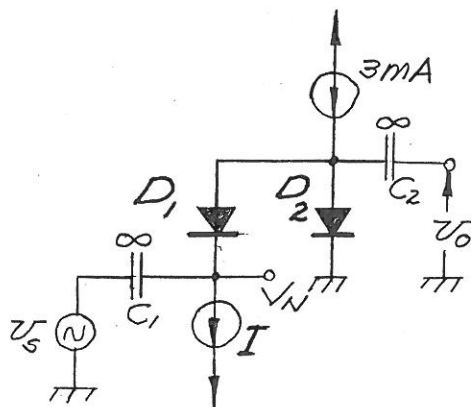a) Determine the value of the dc voltage, V_N when $I = 1mA$.



$V_N = \underline{17.3mV}$ (7pts)

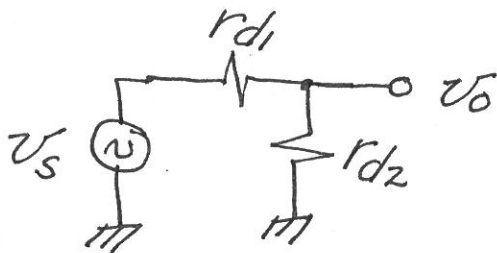b) Draw the small-signal equivalent circuit, replacing the diodes with their small signal resistive model, r_d . (6pts)



c) Determine the value of v_o/v_s when $I = 1mA$.

$v_o/v_s = \underline{1/3}$ (7pts)

EE 311

EXAM 2 (100pts)


October 11, 2013

Name _____

ID _____

(20pts)

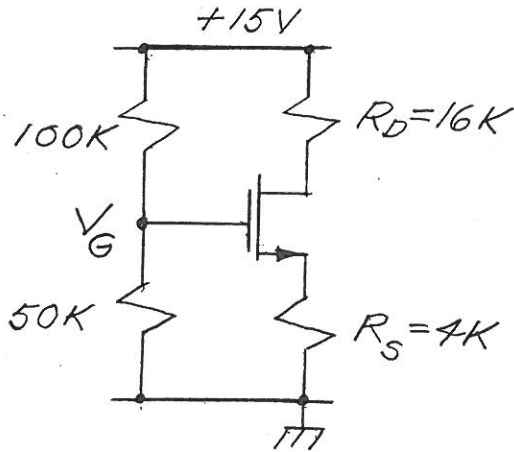5. For the circuit below let $k_n' \frac{W}{L} = 0.25 \text{mA/V}^2$, $V_t = 1\text{V}$ and $\lambda = 0$. Determine V_G , I_D , V_{GS} and V_{DS} .



$V_G = \underline{5\text{V}}$ (1pts)

$V_{GS} = \underline{3\text{V}}$ (3pts)

$I_D = \underline{0.5\text{mA}}$ (4pts)

$V_{DS} = \underline{5\text{V}}$ (4pts)

EE 311


EXAM 2 (100pts)

October 11, 2013

Name _____

ID _____

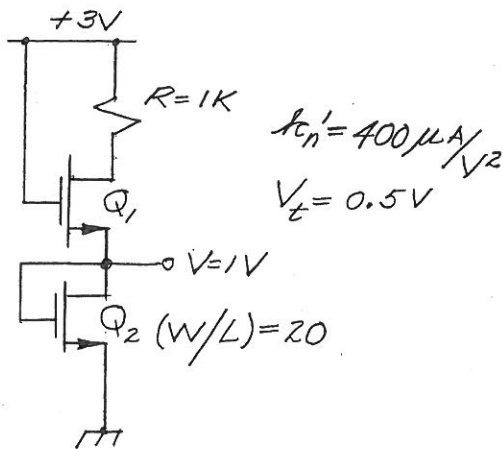(20pts) 6. a) For the circuit shown, determine the value of the drain current, I_D , for $V = 1V$.



$I_D = \underline{1mA}$ (4pts)

b) Determine V_{GS1} and V_{DS1} for transistor Q_1 .

$V_{GS1} = \underline{2V}$ (2pts)

$V_{DS1} = \underline{1.0V}$ (3pts)

c) Does Q_1 operate in the {saturation, triode} region? (3pts)

d) Determine the required aspect ratio, $(W/L)_1$, for transistor Q_1 .

$(W/L)_1 = \underline{2.5}$ (8pts)