
EE434

ASIC & Digital Systems

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Dae Hyun Kim
daehyun@eecs.wsu.edu

Lecture 2


Introduction to CMOS Gates

Ref: Textbook chapter 2

*Some of the slides are adopted from Digital
Integrated Circuits by Jan M Rabaey*


Signals

 - $0 = V_{SS} = \text{Ground} = \text{GND} = \text{Low} = 0\text{V}$
- $1 = V_{DD} = \text{Power} = \text{PWR} = \text{High} = 5\text{V}, 3.3\text{V}, 1.5\text{V}, 1.2\text{V}, 1.0\text{V}$




Switches


- What is a switch?

 


Electrically open

 

Electrically short

 

Electrically open

 


Electrically short

Switches

- Function


$$F = \bar{A} \text{ (inverter)}$$

 

		A	
		0	1
1	0	1	0
	1	0	1

- Two issues

1.

 


		A	
		0	1
1	0	1	0
	1	0	1

 2. Electrical modeling of the operation

Static CMOS Circuit



- At every point in time (except during the switching transients), each gate output is connected to either V_{DD} or V_{SS} via a low-resistive path.
- The outputs of the gates assume at all times the value of the Boolean function implemented by the circuit (ignoring the transient effects during switching periods).





Switches

- Two types of switches

Normally open


 
 


Normally closed

  

Switches

- Function
 $F = \bar{A}$ (inverter)

   


Switches

- Function

$$F = \overline{A \cdot B}$$

V_{DD}

 

V_{SS}


F

		A	
		0	1
B	0	1	1
	1	1	0

Switches

- Function

$$F = \overline{A \cdot B}$$

 


		A	
		0	1
B	0	1	1
	1	1	0

Example


- $F = \overline{A + B}$ (NOR2)
- $F = \overline{A + B + C}$ (NOR3)

Transistors as Switches





- NMOS and PMOS

 

NMOS Transistor

 


PMOS Transistor

    


Transistors as Switches

- NMOS and PMOS

Normally open
(NMOS)

 


Normally closed
(PMOS)

 

CMOS Gates

- Function

$$F = \bar{A}$$

 


		A	
		0	1
0	1	1	0
1	0	1	0

CMOS Gates

- Function

$$F = \overline{A \cdot B}$$

 


		A	
		0	1
B	0	1	1
	1	1	0

CMOS Gates

- Function

$$F = A \cdot B$$

V_{DD}

 


V_{SS}

F

		A	
		0	1
B	0	0	0
	1	0	1

CMOS Gates

- Function
 $F = A \cdot B$

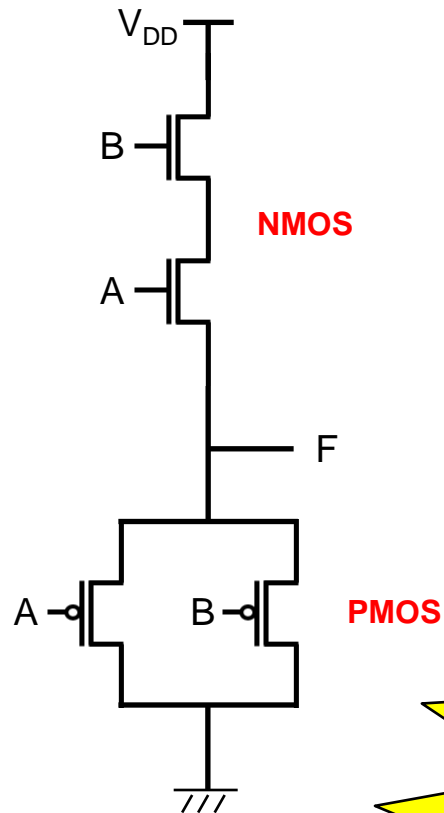


		A	
		0	1
B	0	0	0
	1	0	1

This is not a good design.


Why?

Electrical Modeling

- Ideal switch



 


- Real switch


 


Electrical Modeling

- Ideal switch

   







- Real switch

  

Charge



Transistors as Switches

- NMOS and PMOS

     
 


Threshold Drops

Pull-up network

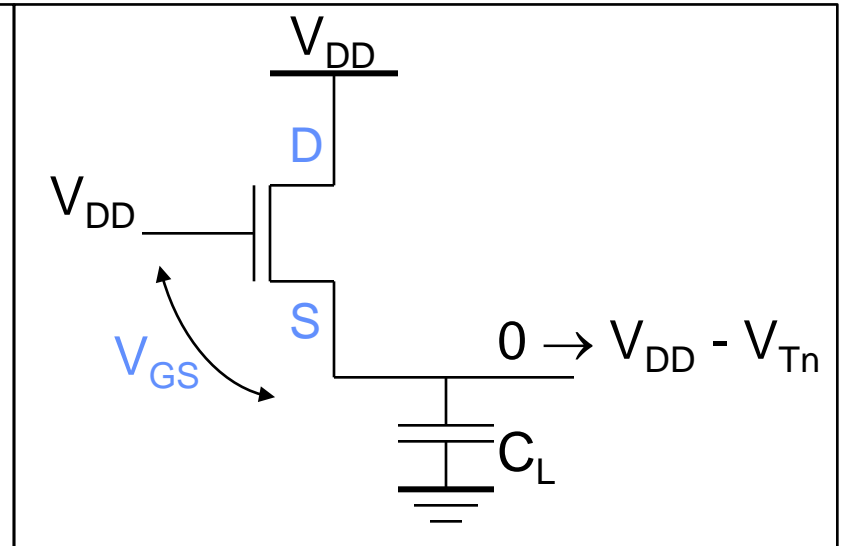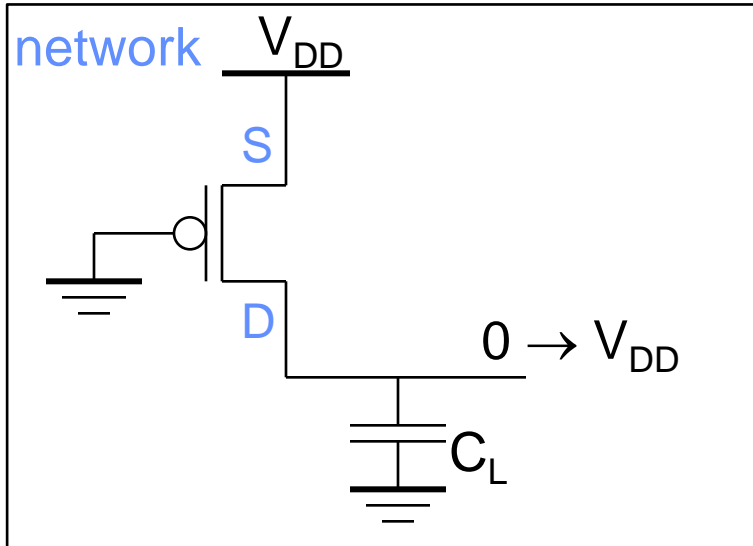


Pull-down network

 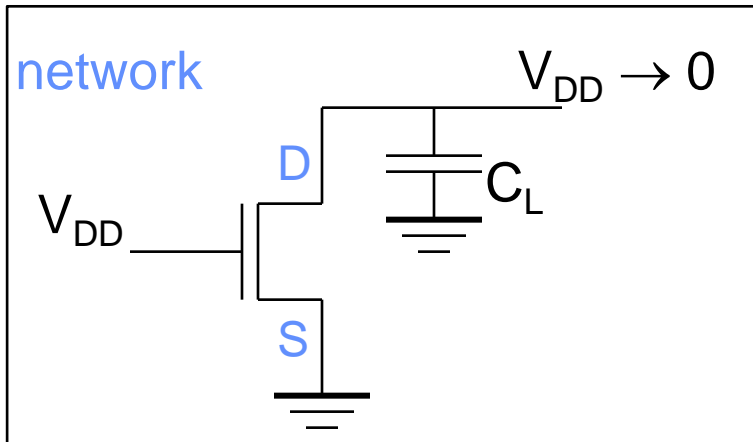

CMOS Gates

- Function

$$F = \overline{A \cdot B}$$

 


		A	
		0	1
B	0	1	1
	1	1	0

CMOS Gates

- Function

$$F = A \cdot B$$

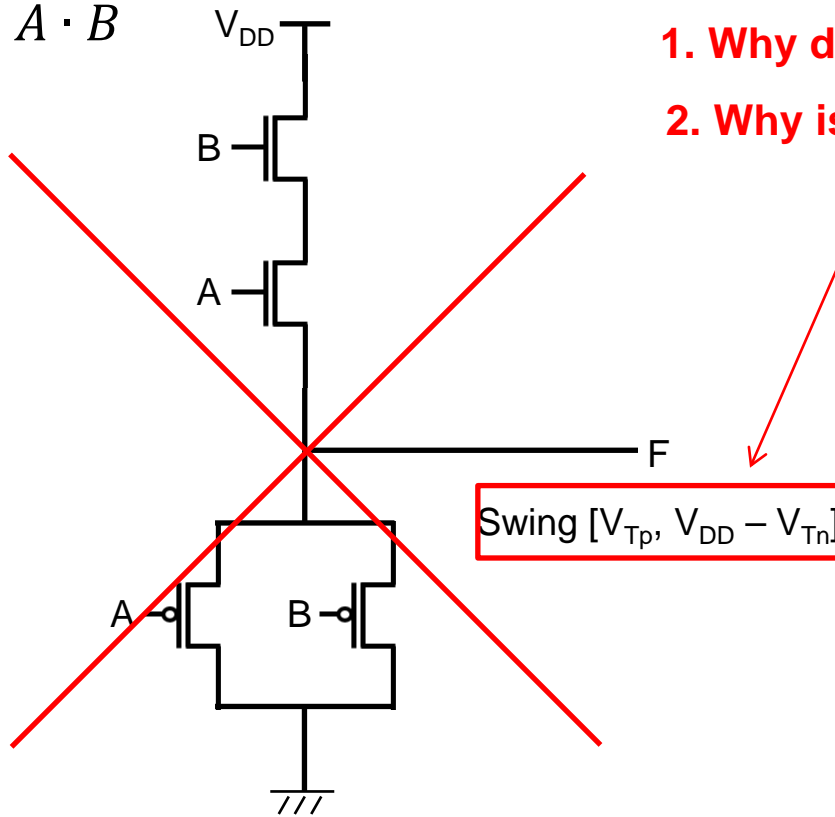


Threshold drop!

1. Why does this happen?
2. Why is this a problem?


		A	
		0	1
B	0	0	0
	1	0	1

The MOS Transistor

 

Structural Details

 
- Channel length L
 - Typical values of L today vary from 130nm to 22 nm
 - The dimension will continue to scale according to Moore's law
- Perpendicular to the plane of the figure is the channel width W
 - Much larger than the minimum length
- Gate oxide thickness t_{ox}
 - Around 25 Å




Operational Mechanism

- NMOS
 - N+ source and N+ drain regions separated by p-type material
 - The body or substrate, is a single-crystal silicon wafer
 - Suppose, source, drain and body are all tied to ground and a positive voltage applied to the gate
 - A positive gate voltage will tend to draw electrons from the substrate into the channel region
 - A conducting path is created between drain and source
 - Current will flow from drain to source in presence of a voltage difference between the source and the drain
 - The gate voltage needed to initiate formation of a conducting channel is termed as the threshold voltage V_t

Threshold Voltage: Concept

 


Transistor in Linear

 


MOS transistor and its bias conditions

Transistor in Saturation

 

Drain Current (NMOS)

 - Cut-off ($V_{gsn} - V_{tn} < 0$)
 - $I_{dsn} = 0$
- Linear region ($V_{gsn} - V_{tn} > 0$ and $V_{dsn} < V_{gsn} - V_{tn}$)
 - $I_{dsn} = \beta_n \left[(V_{gsn} - V_{tn})V_{dsn} - \frac{1}{2}V_{dsn}^2 \right]$
- Saturation region ($V_{gsn} - V_{tn} > 0$ and $V_{dsn} \geq V_{gsn} - V_{tn}$)
 - $I_{dsn} = \frac{1}{2}\beta_n(V_{gsn} - V_{tn})^2$



$$\beta_n = \mu_n c_{OX} \frac{W_n}{L_n} = \mu_n \frac{\epsilon_{OX}}{t_{OX}} \cdot \frac{W_n}{L_n}$$

Drain Current (PMOS)

- Cut-off ($|V_{gsp}| - |V_{tp}| < 0$)


- $I_{sdp} = 0$

- Linear region ($|V_{gsp}| - |V_{tp}| > 0$ and $|V_{dsp}| < |V_{gsp}| - |V_{tp}|$)

- $I_{sdp} = \beta_p \left[(|V_{gsp}| - |V_{tp}|) |V_{dsp}| - \frac{1}{2} |V_{dsp}|^2 \right]$

- Saturation region ($|V_{gsp}| - |V_{tp}| > 0$ and $|V_{dsp}| > |V_{gsp}| - |V_{tp}|$)

- $I_{sdp} = \frac{1}{2} \beta_p (|V_{gsp}| - |V_{tp}|)^2$

 


$$\beta_p = \mu_p c_{OX} \frac{W_p}{L_p} = \mu_p \frac{\epsilon_{OX}}{t_{OX}} \cdot \frac{W_p}{L_p}$$

CMOS Gates

- Function

$$F = \overline{A \cdot B}$$

 


		A	
		0	1
B	0	1	1
	1	1	0

CMOS Gates

- Function

$$F = A \cdot B$$

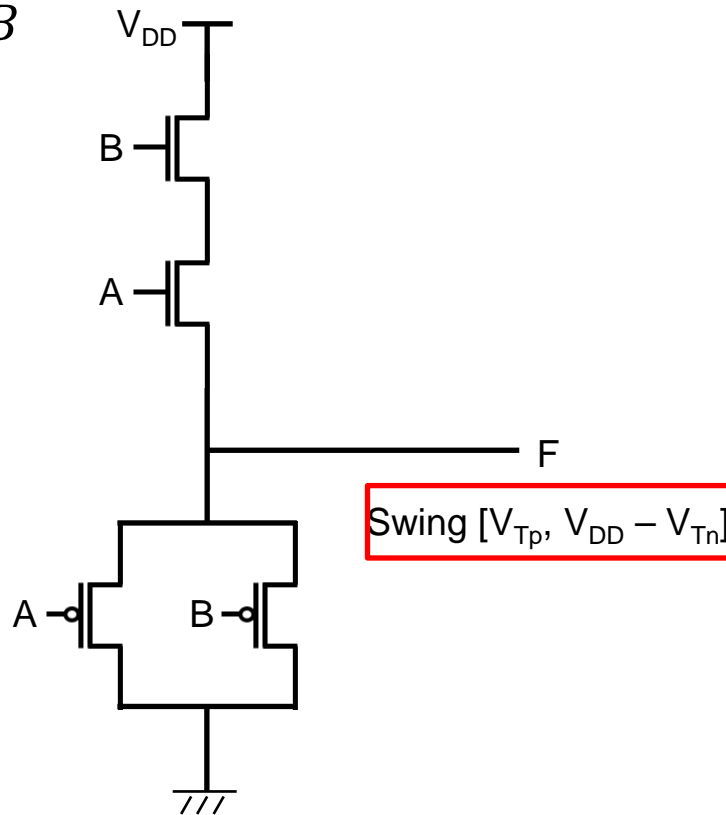


		A	
		0	1
B	0	0	0
	1	0	1

CMOS Gates

- Function

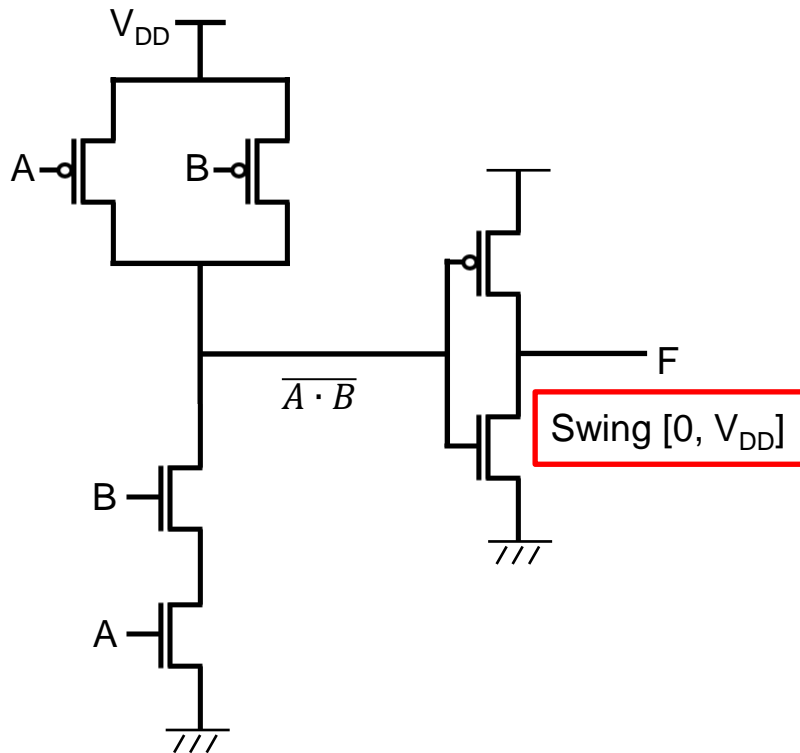
$$F = A \cdot B = \overline{\overline{A \cdot B}}$$



		A	
		0	1
B	0	0	0
	1	0	1

How to Design CMOS Gates

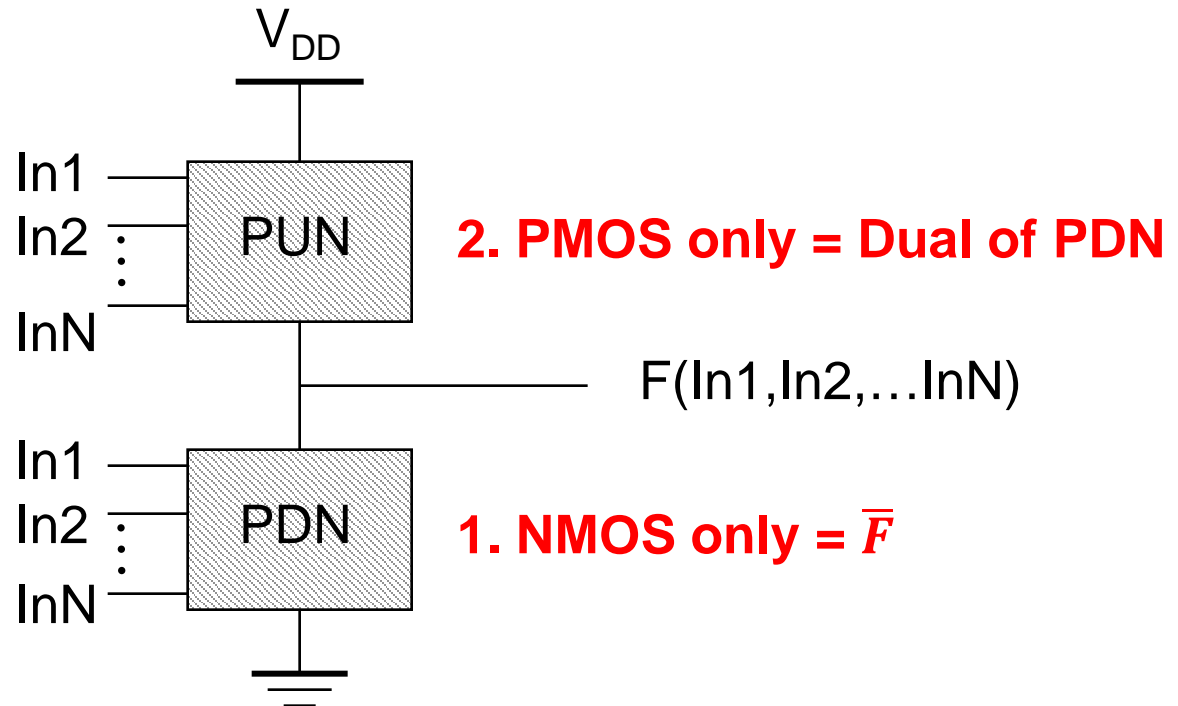- The function of the PUN is to provide a connection between the output and V_{DD} anytime the output of the logic gate is meant to be 1
- Similarly the role of the PDN is to connect the output to GND when the output is meant to be 0



Pull-up network (PUN) and Pull-down network (PDN) are **dual** logic networks.


Dual Logic

- Dual of $f(X_1, X_2, \dots, X_n, 0, 1, \text{AND}, \text{OR})$
 $= f(X_1, X_2, \dots, X_n, \mathbf{1}, \mathbf{0}, \mathbf{OR}, \mathbf{AND})$
- $(A \cdot B)^D = A + B$
- $(A + B)^D = A \cdot B$
- $(1 \cdot A)^D = 0 + A = A$
- $(1 + A)^D = 0 \cdot A = 0$
- $(0 \cdot A)^D = 1 + A = 1$
- $(0 + A)^D = 1 \cdot A = A$

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

PDN: $G = A B \Rightarrow$ Conduction to GND


PUN: $F = \overline{A + B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 


Complex CMOS Gate

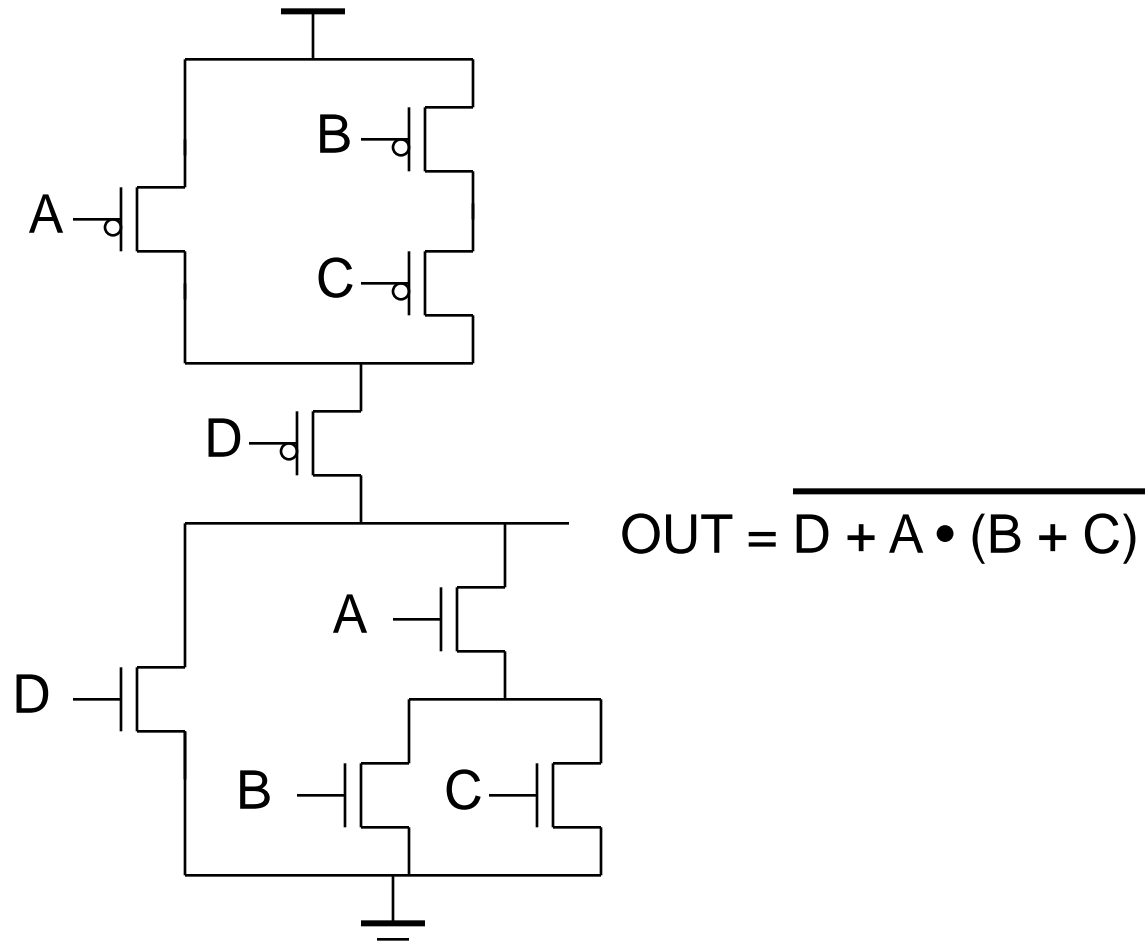


Constructing a Complex Gate

 

(a) pull-down network

 

 (b) Deriving the pull-up network hierarchically by identifying sub-nets



(c) complete gate

Conversion From a Boolean Equation to a Schematic

- For given F

1. F

2. $F = \bar{\bar{F}} = \boxed{\bar{F}} \rightarrow \text{NOT} \rightarrow F$

- $F = \overline{A \cdot B}$
- $F = A \cdot B$
- $F = A \cdot \bar{B}$


Example

- $F = \overline{A \cdot B \cdot C}$ (NAND3)
- $F = A + B + C$ (OR3)
- $F = \overline{A \cdot B + C}$ (AOI21)
- $F = A \oplus B$ (XOR2)
- $F = \overline{A \oplus B}$ (XNOR2)
- $S = A \oplus B \oplus C$ (Sum)
- $CO = (A \oplus B) \cdot C + (A \cdot B)$ (Carry-out)


DC Characteristics of CMOS Gates

- Need to consider
 - ON resistance
 - Parasitic capacitance


Dynamic Behavior of MOS Transistor

 

The Gate Capacitance

 

Top view

 


Cross section

$$C_{gate} = \frac{\epsilon_{ox}}{t_{ox}} WL$$



MOS Capacitance

 - The source and drain regions and the substrate form pn junctions that give rise to two additional capacitances
- The capacitances C_{sb} and C_{db} are n+p source/drain junction capacitance for NMOS devices



MOS Capacitance

$$C_g = C_{gb} + C_{gs} + C_{gd}$$

  

Cut-off

$$C_{gs} = C_{gd} = 0$$

$$C_{gb} = \frac{C_o C_{dep}}{C_o + C_{dep}}$$

$$C_o = \frac{\epsilon_{SiO2} \epsilon_o}{t_{ox}} WL$$

$$C_{dep} = \frac{\epsilon_{Si} \epsilon_o}{d} WL$$

Linear

$$C_{gb} = 0$$

$$C_{gs} = C_{gd} = \frac{1}{2} \cdot \frac{\epsilon_{SiO2} \epsilon_o}{t_{ox}} WL$$

Saturation

$$C_{gb} = 0$$

$$C_{gd} = 0$$

$$C_{gs} = \frac{2}{3} \cdot \frac{\epsilon_{SiO2} \epsilon_o}{t_{ox}} WL$$


MOS Resistance

- Average V/I at two voltages:
 - maximum output voltage
 - middle of linear region
- Voltage is V_{ds} , current is given I_d at that drain voltage. Step input means that $V_{gs} = V_{DD}$ always.

Saturation: conductance = $g_m = \beta(V_{gs} - V_t)$

Linear: conductance = $g_m = \beta V_{ds}$

MOS Resistance Approximation

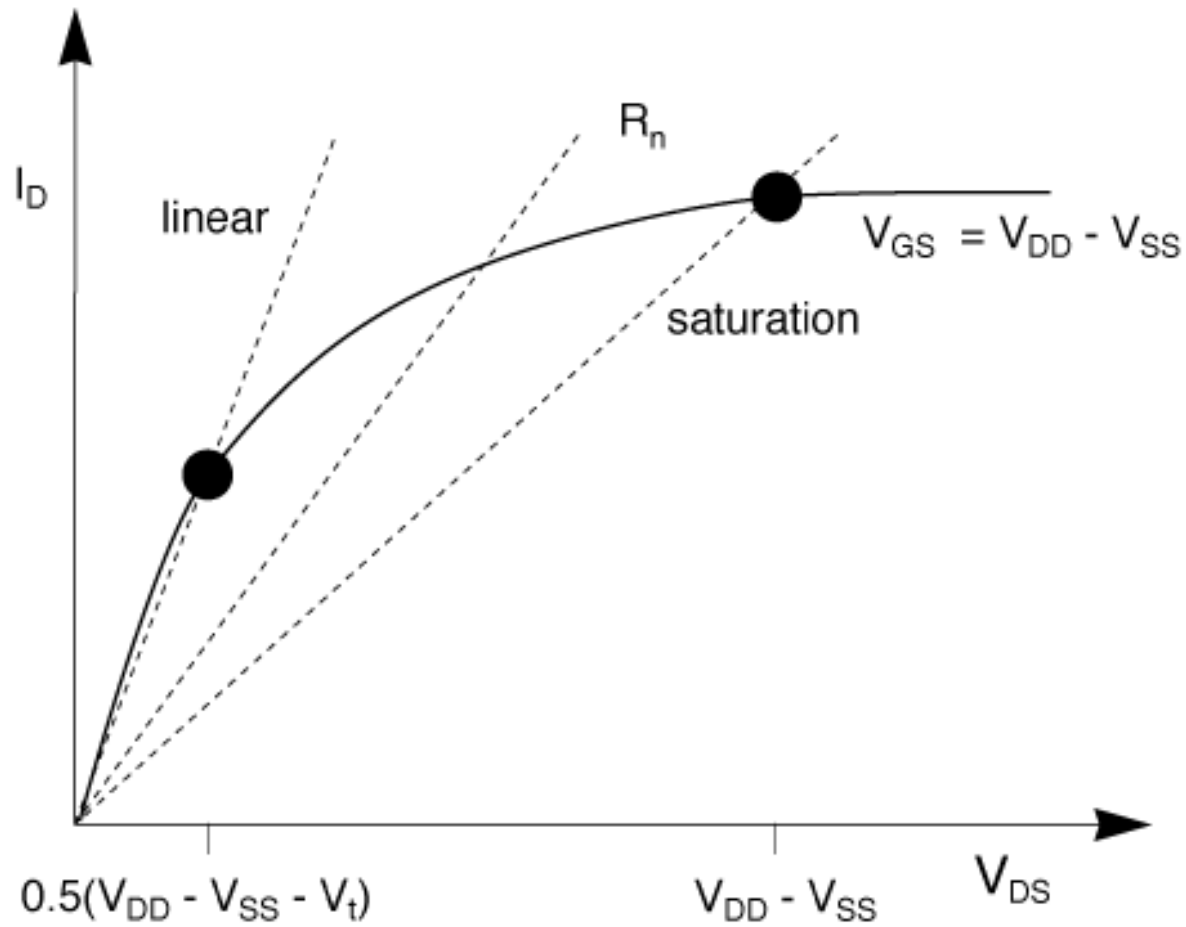

Example

- $F = \overline{A1 \cdot A2 \cdot A3 \cdot A4 \cdot A5 \cdot A6 \cdot A7 \cdot A8}$ (NAND8)