
EE434

ASIC & Digital Systems

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Dae Hyun Kim
daehyun@eecs.wsu.edu

Lecture 3

More on CMOS Gates

Ref: Textbook chapter 2



*Some of the slides are adopted from Digital Integrated Circuits
by Jan M Rabaey*

CMOS Inverter – DC Characteristics

- Why do we study the DC characteristics of a CMOS inverter?
 - Analyze a CMOS inverter by hand calculation
 - Understand how the transistors operate in a CMOS inverter
 - Understand the influence of β_n and β_p
 - Understand Noise Margin



CMOS Inverter – DC Characteristics

- Region A) $0 \leq V_{in} \leq V_{tn}$
- Region B) $V_{tn} \leq V_{in} < \frac{V_{DD}}{2}$
- Region C) $V_{in} = \frac{V_{DD}}{2}$
- Region D) $\frac{V_{DD}}{2} < V_{in} \leq V_{DD} - |V_{tp}|$
- Region E) $V_{DD} - |V_{tp}| < V_{in}$

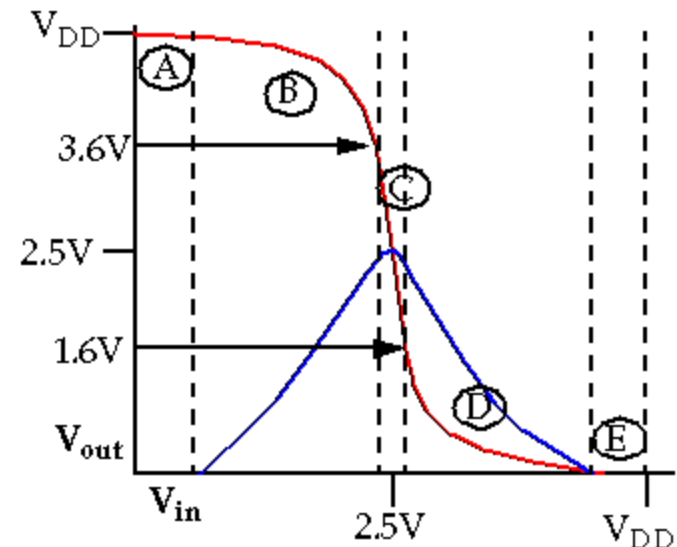 



CMOS Inverter – DC Characteristics

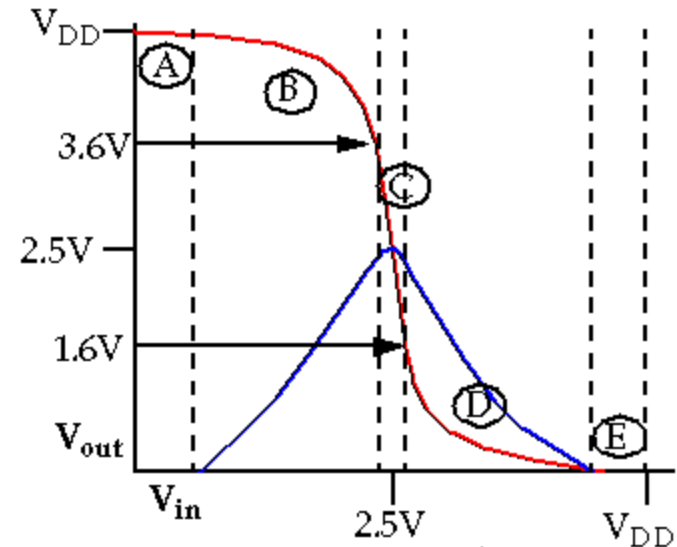 - Region A) $0 \leq V_{in} \leq V_{tn}$
 - NMOS: Cut-off
 - PMOS: Linear



CMOS Inverter – DC Characteristics

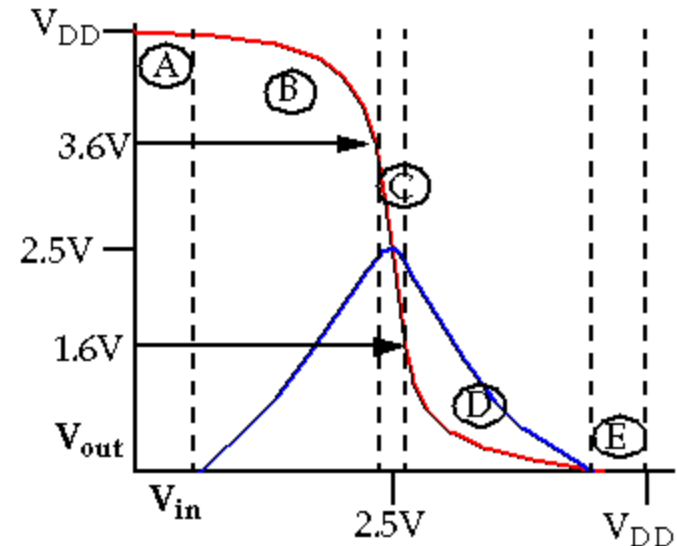
 
- Region B) $V_{tn} \leq V_{in} < \frac{V_{DD}}{2}$
 - NMOS: Saturated
 - PMOS: Linear



$$V_{out} = (V_{in} - V_{tp}) + \sqrt{(V_{in} - V_{tp})^2 - 2 \left(V_{in} - \frac{V_{DD}}{2} - V_{tp} \right) V_{DD} - \frac{\beta_n}{\beta_p} (V_{in} - V_{tn})^2}$$

CMOS Inverter – DC Characteristics

 
 
- Region C) $V_{in} = \frac{V_{DD}}{2}$
 - NMOS: Saturated
 - PMOS: Saturated



$$V_{in} - V_{tn} < V_{out} < V_{in} - V_{tp}$$

CMOS Inverter – DC Characteristics



- Region D) $\frac{V_{DD}}{2} < V_{in} \leq V_{DD} - |V_{tp}|$
 - NMOS: Linear
 - PMOS: Saturated

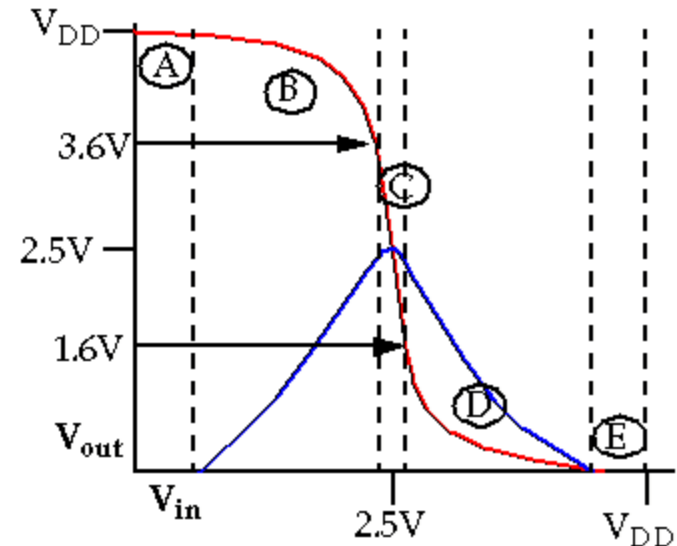 

$$V_{out} = (V_{in} - V_{tn}) - \sqrt{(V_{in} - V_{tn})^2 - \frac{\beta_p}{\beta_n} (V_{in} - V_{DD} - V_{tp})^2}$$


CMOS Inverter – DC Characteristics

- Region E) $V_{DD} - |V_{tp}| < V_{in}$
 - NMOS: Linear
 - PMOS: Cut-off

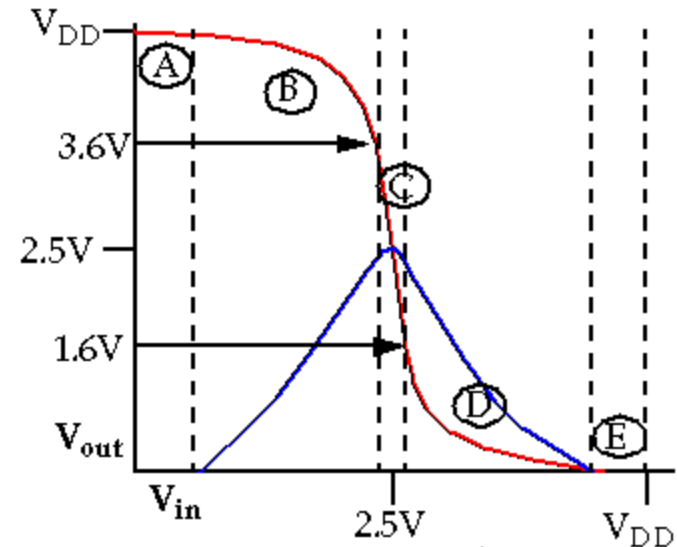 

CMOS Inverter – DC Characteristics

- β_n and β_p

 


$$\text{Region B) } V_{out} = (V_{in} - V_{tp}) + \sqrt{(V_{in} - V_{tp})^2 - 2 \left(V_{in} - \frac{V_{DD}}{2} - V_{tp} \right) V_{DD} - \frac{\beta_n}{\beta_p} (V_{in} - V_{tn})^2}$$




$$\text{Region D) } V_{out} = (V_{in} - V_{tn}) - \sqrt{(V_{in} - V_{tn})^2 - \frac{\beta_p}{\beta_n} (V_{in} - V_{DD} - V_{tp})^2}$$

CMOS Inverter – DC Characteristics

- Intuitive analysis

 

Noise Margin

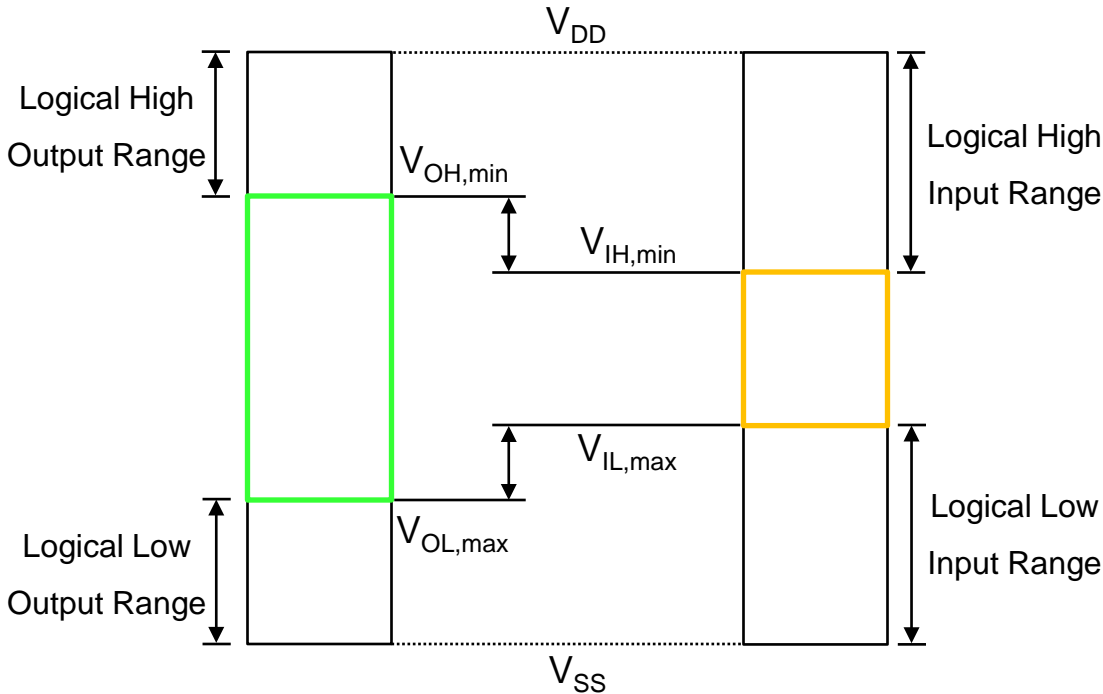  

- $V_{IH,min}$: minimum high input voltage
- $V_{IL,max}$: maximum low input voltage
- $V_{OH,min}$: minimum high output voltage
- $V_{OL,max}$: maximum low output voltage

Low noise margin = $NM_L = |V_{IL,max} - V_{OL,max}|$

High noise margin = $NM_H = |V_{OH,min} - V_{IH,min}|$


Noise Margin

- How to increase the noise margin



$$\text{Low noise margin} = \text{NM}_L = |V_{IL,\text{max}} - V_{OL,\text{max}}|$$



$$\text{High noise margin} = \text{NM}_H = |V_{OH,\text{min}} - V_{IH,\text{min}}|$$

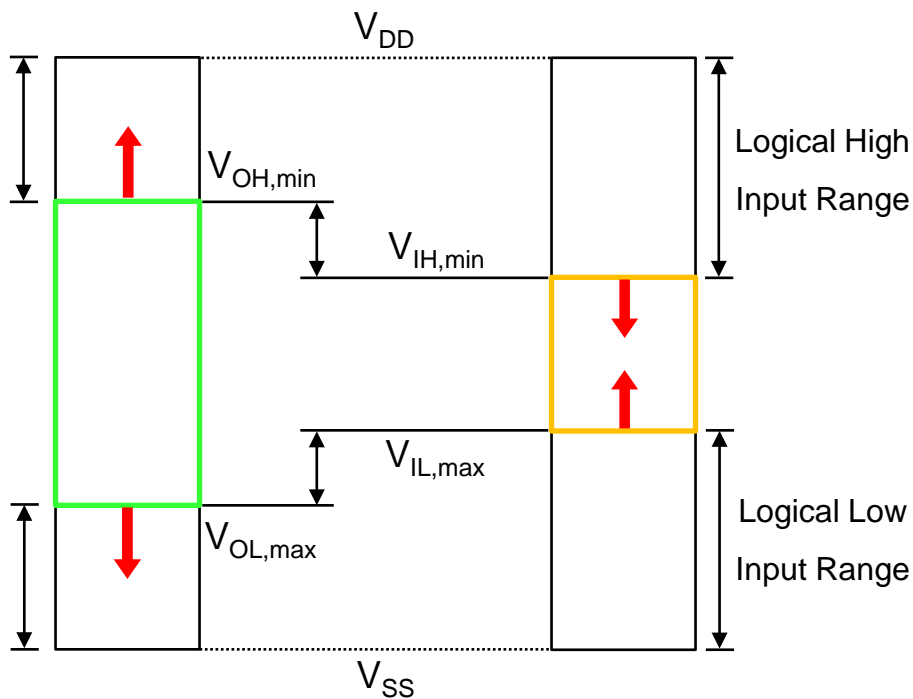

- $V_{IH,\text{min}}$: minimum high input voltage
- $V_{IL,\text{max}}$: maximum low input voltage
- $V_{OH,\text{min}}$: minimum high output voltage
- $V_{OL,\text{max}}$: maximum low output voltage

CMOS Inverter – Switching Characteristics

- Fall time & Rise time

  

CMOS Inverter – Switching Characteristics

- Fall time calculation
 - Natural response

$$V_{out}(t) = V_{DD}e^{-\frac{t}{R_n C_{out}}} = V_{DD}e^{-\frac{t}{\tau_n}}$$
$$t = \tau_n \ln\left(\frac{V_{DD}}{V_{out}(t)}\right)$$

- τ_n : NMOS time constant

- Fall time

$$t_f = t_{0.1V_{DD}} - t_{0.9V_{DD}} = \tau_n \ln\left(\frac{V_{DD}}{0.1V_{DD}}\right) - \tau_n \ln\left(\frac{V_{DD}}{0.9V_{DD}}\right) = \tau_n \ln(9) \approx 2.2\tau_n$$

CMOS Inverter – Switching Characteristics

- Rise time calculation
 - Step response

$$V_{out}(t) = V_{DD} \left(1 - e^{-\frac{t}{R_p C_{out}}}\right) = V_{DD} \left(1 - e^{-\frac{t}{\tau_p}}\right)$$
$$t = \tau_p \ln \left(\frac{V_{DD}}{V_{DD} - V_{out}(t)} \right)$$

- τ_p : PMOS time constant

- Rise time

$$t_r = t_{0.9V_{DD}} - t_{0.1V_{DD}} = \tau_p \ln \left(\frac{V_{DD}}{0.1V_{DD}} \right) - \tau_p \ln \left(\frac{V_{DD}}{0.9V_{DD}} \right) = \tau_p \ln(9) \approx 2.2\tau_p$$

CMOS Inverter – Switching Characteristics

- Maximum signal frequency

$$f_{max} = \frac{1}{t_r + t_f} = \frac{1}{2.2(\tau_p + \tau_n)}$$

- Example

- $R_p = 500\Omega$
- $R_n = 500\Omega$
- $C_{out} = 20\text{fF}$

- $\tau_p = 10\text{ps}$
- $\tau_n = 10\text{ps}$
- $f_{max} = 23\text{GHz}$

CMOS Inverter – Switching Characteristics

- Speed vs. area trade-off

- $\beta_n = \mu_n C_{ox} \frac{W_n}{L_n}$

- $\beta_p = \mu_p C_{ox} \frac{W_p}{L_p}$

- $R_n = \frac{1}{\beta_n (V_{DD} - V_{tn})}$


- $R_p = \frac{1}{\beta_p (V_{DD} - |V_{tp}|)}$

- $\tau_n = R_n C_{out}$

- $\tau_p = R_p C_{out}$

Transistor Sizing

 
- Achieve perfectly-balanced switching characteristics in the worst case.
- Satisfy target constraints ($\tau = RC$).
- Assumption: $\mu_n = 2 \cdot \mu_p$



$$\begin{aligned} \tau_n &= RC \\ \tau_p &= 2RC \end{aligned}$$

Transistor Sizing

 
- Achieve perfectly-balanced switching characteristics in the worst case.
- Satisfy target constraints ($\tau = RC$).
- Assumption: $\mu_n = 2 \cdot \mu_p$




$$\begin{aligned} \tau_n &= RC \\ \tau_p &= RC \end{aligned}$$

Transistor Sizing

- NAND2

 

 
$$\begin{aligned}\tau_n &= 2RC \\ \tau_p &= 2RC\end{aligned}$$




$$\begin{aligned}\tau_n &= RC \\ \tau_p &= RC\end{aligned}$$

Transistor Sizing

- NOR2

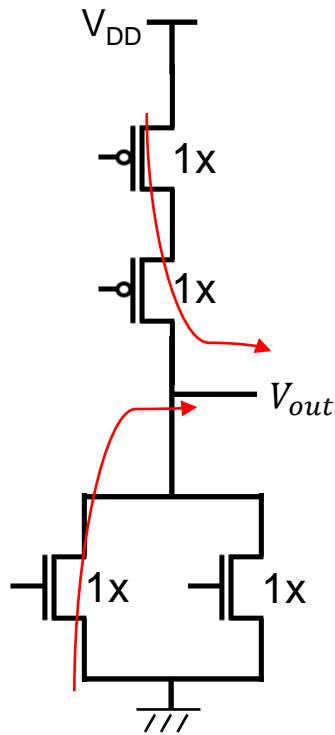

 
$$\begin{aligned}\tau_n &= RC \\ \tau_p &= 4RC\end{aligned}$$




$$\begin{aligned}\tau_n &= RC \\ \tau_p &= RC\end{aligned}$$

Transistor Sizing

- $F = \overline{A + B \cdot C}$

 



$$\tau_n = 2RC$$
$$\tau_p = 4RC$$

 

$$\tau_n = RC$$
$$\tau_p = RC$$

Transistor Sizing

- Examples (target: $\tau = RC$)

  


CMOS NAND/NOR – DC Characteristics


- CMOS NAND
- CMOS NOR

CMOS NAND/NOR – DC Characteristics

- CMOS NAND

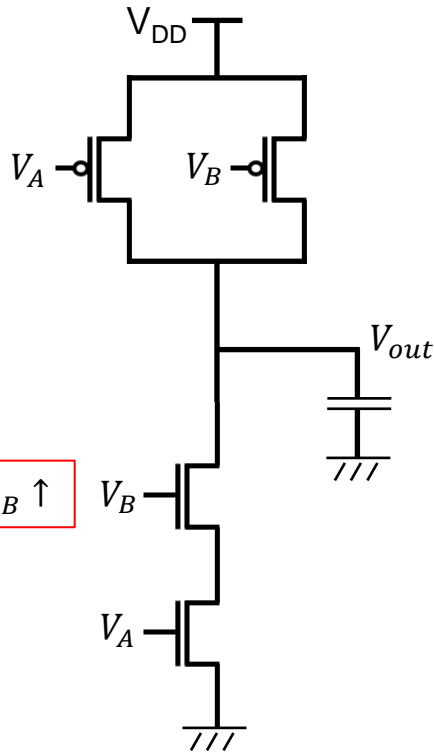


	V_A	V_B
(i)	$0 \rightarrow V_{DD}$	$0 \rightarrow V_{DD}$
(ii)	V_{DD}	$0 \rightarrow V_{DD}$
(iii)	$0 \rightarrow V_{DD}$	V_{DD}

 


$$V_{tn} = V_{tn,0} + \gamma(\sqrt{|V_{SB} + 2\phi_F|} - \sqrt{2\phi_F})$$

CMOS NAND/NOR – DC Characteristics

- CMOS NOR

 

	V_A	V_B
(i)	$0 \rightarrow V_{DD}$	$0 \rightarrow V_{DD}$
(ii)	0	$0 \rightarrow V_{DD}$
(iii)	$0 \rightarrow V_{DD}$	0

 


Elmore Delay

- Before we study the switching characteristics of the NAND and NOR gates, we need to know how to compute (approximate) delay of an RC tree.
- Elmore Delay
 - A very simple delay computation method.

Elmore Delay


- For two-pin nets

 

$$\begin{aligned} \tau = & R_{OUT} * (C_1 + \dots + C_5 + C_{LOAD}) \\ & + R_1 * (C_1 + \dots + C_5 + C_{LOAD}) \\ & + R_2 * (C_2 + \dots + C_5 + C_{LOAD}) \\ & + R_3 * (C_3 + \dots + C_5 + C_{LOAD}) \\ & \quad + R_4 * (C_4 + C_5 + C_{LOAD}) \\ & \quad \quad + R_5 * (C_5 + C_{LOAD}) \end{aligned}$$

Elmore Delay


- For multi-pin nets

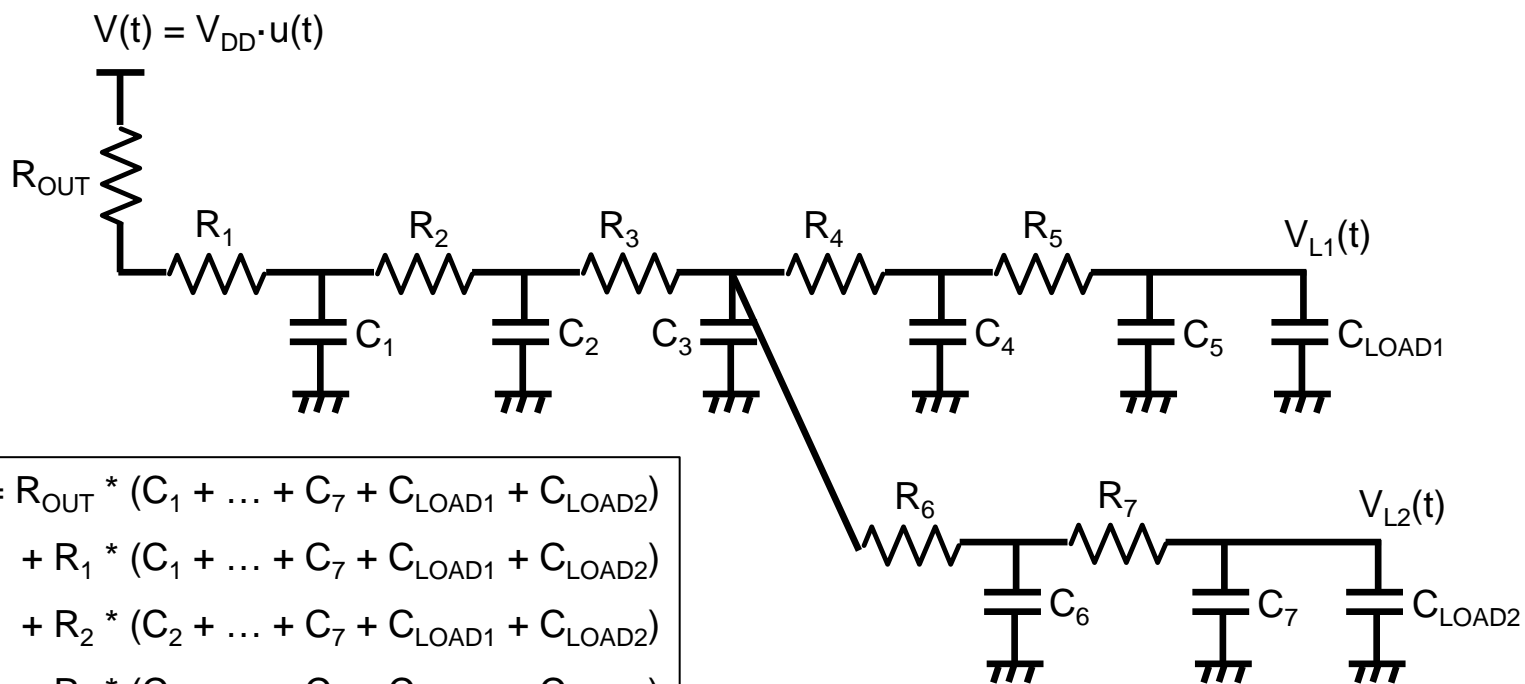

$$\begin{aligned} \tau_1 = & R_{OUT} * (C_1 + \dots + C_7 + C_{LOAD1} + C_{LOAD2}) \\ & + R_1 * (C_1 + \dots + C_7 + C_{LOAD1} + C_{LOAD2}) \\ & + R_2 * (C_2 + \dots + C_7 + C_{LOAD1} + C_{LOAD2}) \\ & + R_3 * (C_3 + \dots + C_7 + C_{LOAD1} + C_{LOAD2}) \\ & \quad + R_4 * (C_4 + C_5 + C_{LOAD1}) \\ & \quad + R_5 * (C_5 + C_{LOAD1}) \end{aligned}$$

CMOS NAND/NOR – Switching Characteristics

- CMOS NAND

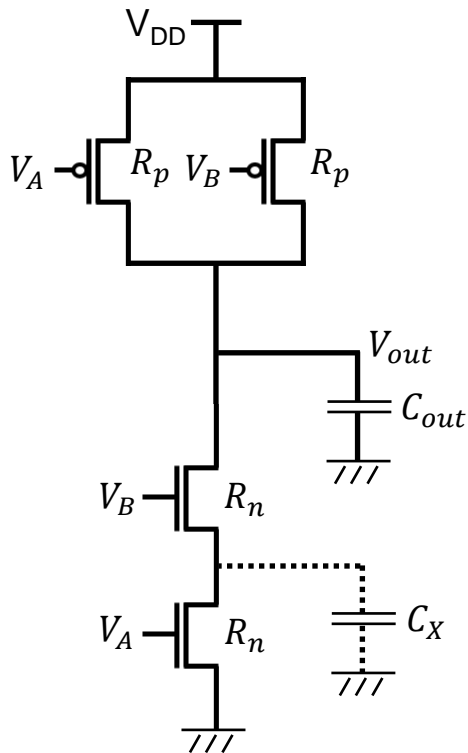

Worst-case rise time: $t_r \approx 2.2\tau_p = 2.2(R_p(C_{out} + C_X))$


Best-case rise time: $t_r \approx 2.2\tau_p = 2.2\left(\frac{R_p}{2}\right)C_{out}$

Worst-case fall time: $t_f \approx 2.2\tau_n = 2.2[(2R_n)C_{out} + R_nC_X]$

Best-case fall time: $t_f \approx 2.2\tau_n = 2.2(2R_n)C_{out}$

CMOS NAND/NOR – Switching Characteristics

- CMOS NOR

 

Worst-case rise time: $t_r \approx 2.2\tau_p = 2.2[R_p(C_X + C_{out}) + R_p C_{out}]$


Best-case rise time: $t_r \approx 2.2\tau_p = 2.2(2R_p)C_{out}$

Worst-case fall time: $t_f \approx 2.2\tau_n = 2.2[R_n C_{out} + (R_n + R_p)C_X]$

Best-case fall time: $t_f \approx 2.2\tau_n = 2.2\left(\frac{R_n}{2}\right)C_{out}$

CMOS Inverter – Power Dissipation

 - $P = V_{DD}I_{DD}$
 - = $P_{DC} + P_{dyn}$
 - $P_{DC} = V_{DD}I_{DDQ}$
 - I_{DDQ} : Quiescent leakage current
 - $P_{dyn} = \alpha \cdot f \cdot C_{out}V_{DD}^2$





More CMOS Gates

- Combinational logic
- Transmission gates
- Multiplexors
- Tristate gates
- Sequential gates
 - Latches
 - Flip Flops

Transmission Gate

- Transmission gate

  


		A	
		0	1
S	0	Z	Z
	1	0 ($V_{SS} + \delta$)	1 ($V_{DD} - \delta$)

Multiplexor



- Multiplexor $F = \bar{S} \cdot P_0 + S \cdot P_1$
 
$$F = \bar{\bar{\bar{\bar{\bar{S}}}} \cdot P_0 + S \cdot P_1 = (\bar{S} \cdot \bar{P_0} + S \cdot \bar{P_1} + \bar{P_0} \cdot \bar{P_1})$$




	S	F
0	P_0	
1	P_1	

4 transistors vs. 12 (or 10) transistors

 
 


Tristate gate

- Tristate inverter

 


	Out
EN = 0	Z
EN = 1	\bar{in}

  


Static CMOS Sequential Gates

- D-latch

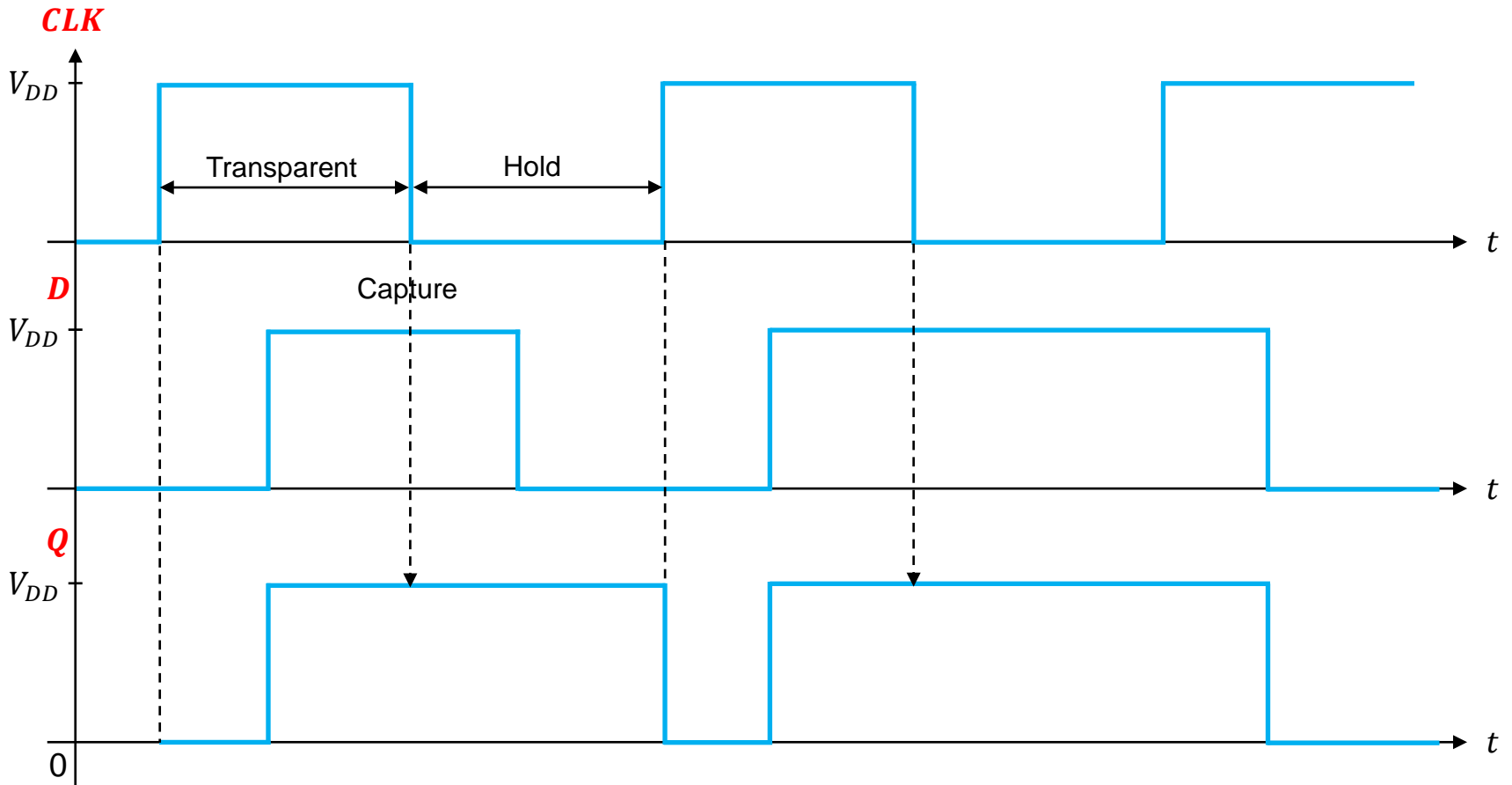


Static CMOS Sequential Gates

- D-latch

 


Static CMOS Sequential Gates

- Positive Edge-Triggered D Flip-Flop

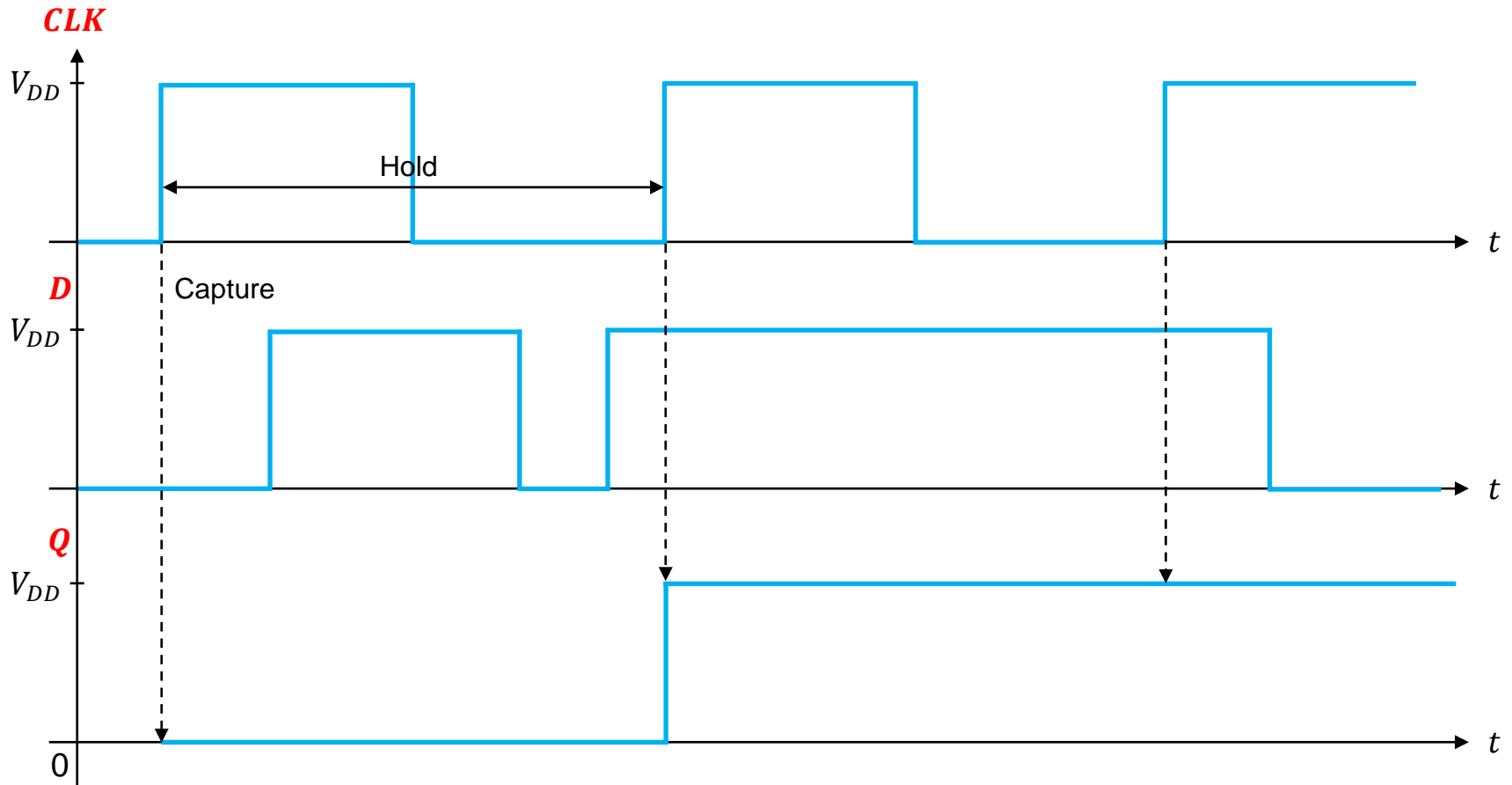

Static CMOS Sequential Gates


- Positive Edge-Triggered D Flip-Flop

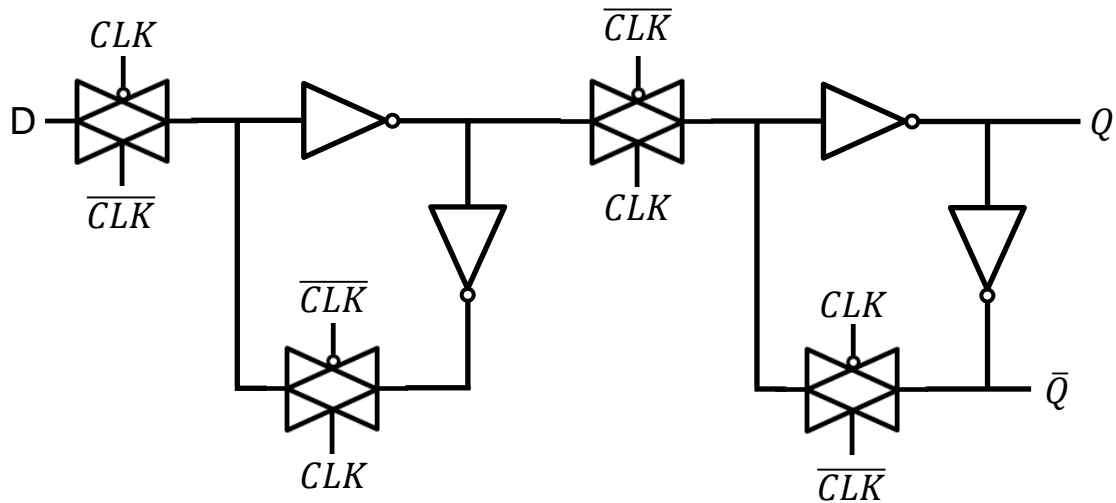

Static CMOS Sequential Gates

- Positive Edge-Triggered D Flip-Flop


$CLK = 0$

 

Static CMOS Sequential Gates


- Positive Edge-Triggered D Flip-Flop

CLK = 1

 


Static CMOS Sequential Gates

 - Positive Edge-Triggered D Flip-Flop with ??



Static CMOS Sequential Gates

- Why not?

 

CMOS Properties

- Full rail-to-rail swing; **high noise margins**
- Logic levels not dependent upon the relative device sizes; **ratio less**
- Always a path to Vdd or Gnd in steady state; **low output impedance**
- Extremely **high input resistance**; nearly zero steady-state input current
- No direct path between power and ground; **no static power dissipation**
- Propagation delay function of load capacitance and resistance of transistors
- N fan-in gates need 2N transistors