
EE434

ASIC & Digital Systems

Partha Pande
School of EECS
Washington State University
pande@eecs.wsu.edu

Spring 2015
Dae Hyun Kim
daehyun@eecs.wsu.edu

Lecture 4

More on CMOS Gates

Ref: Textbook chapter 2

*Some of the slides are adopted from Digital Integrated Circuits
by Jan M Rabaey*

CMOS Properties


- Full rail-to-rail swing; **high noise margins**
- Logic levels not dependent upon the relative device sizes; **ratio less**
- Always a path to Vdd or Gnd in steady state; **low output impedance**
- Extremely **high input resistance**; nearly zero steady-state input current
- No direct path between power and ground; **no static power dissipation**
- Propagation delay function of load capacitance and resistance of transistors
- N fan-in gates need 2N transistors

Special CMOS Design Styles

- Ratioed Logic (Pseudo-nMOS)
- Dynamic CMOS
- Domino Logic
- Multiple-Output Domino Logic
- Dual-Rail Logic
- Pass Transistor Logic
- Transmissions Gate Logic


Ratioed Logic

 - Pseudo NMOS
 - Smaller area and load, but static power dissipation
 - Follow board notes



Pseudo-nMOS



 
- More accurate computation
 - PMOS: Saturation
 - NMOS: Linear



$$\frac{\beta_n}{2} [2(V_{DD} - V_{tn})V_{OL} - V_{OL}^2] = \frac{\beta_p}{2} (V_{DD} - |V_{tp}|)^2$$

$$V_{OL} = (V_{DD} - V_{tn}) - \sqrt{(V_{DD} - V_{tn})^2 - \frac{\beta_p}{\beta_n} (V_{DD} - |V_{tp}|)^2}$$

Pseudo-nMOS

  
 


$$V_{out} = 0.1V_{DD} = V_{DD} \cdot \frac{R_n}{R_p + R_n}$$
$$R_p = 9R_n$$

Dynamic CMOS

- In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires on $n + 2$ ($n+1$ N-type + 1 P-type) transistors

Dynamic CMOS

  


Two phase operation

Precharge (CLK = 0)

Evaluate (CLK = 1)


Dynamic CMOS

- Operation

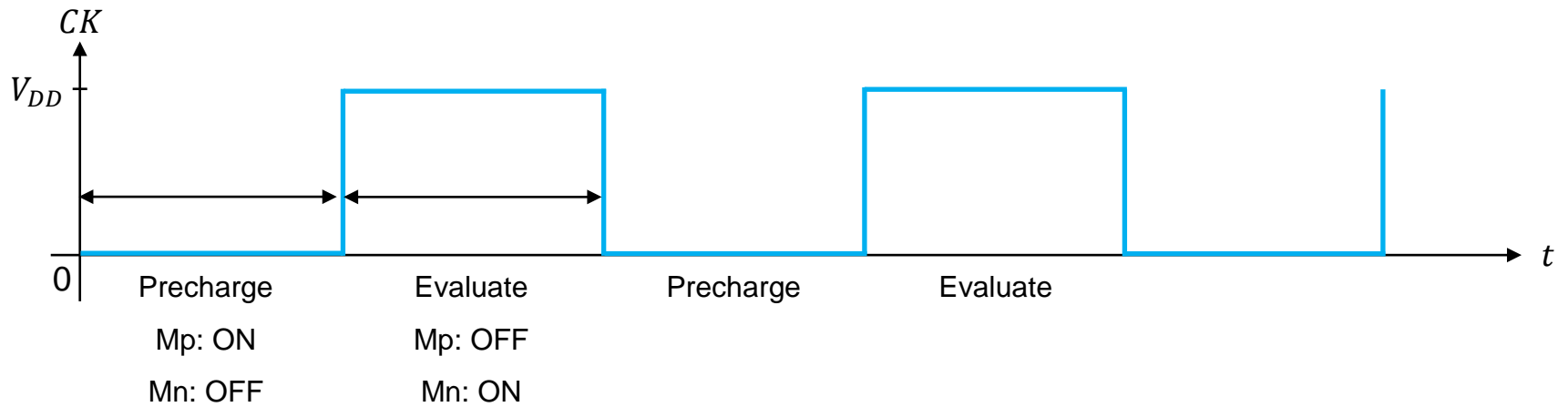


Dynamic CMOS

- $F = \overline{A \cdot B \cdot C}$

 


Dynamic CMOS

- Precharge

 

Dynamic CMOS

- Evaluation

 

Properties of Dynamic CMOS


- Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static CMOS gates)
- Full swing outputs
- Non-ratioed - sizing of the devices does not affect the logic levels
- Faster switching speeds
 - reduced load capacitance due to lower input capacitance (C_{in})
 - reduced load capacitance due to smaller output loading (C_{out})

Properties of Dynamic CMOS

- Overall power dissipation usually **higher** than static CMOS
 - no static current path ever exists between V_{DD} and GND
 - no glitching
 - **higher transition probabilities**
 - **extra load on Clk**
- Needs a precharge/evaluate clock


Dynamic CMOS

- Charge sharing

 

Dynamic CMOS

- Charge sharing

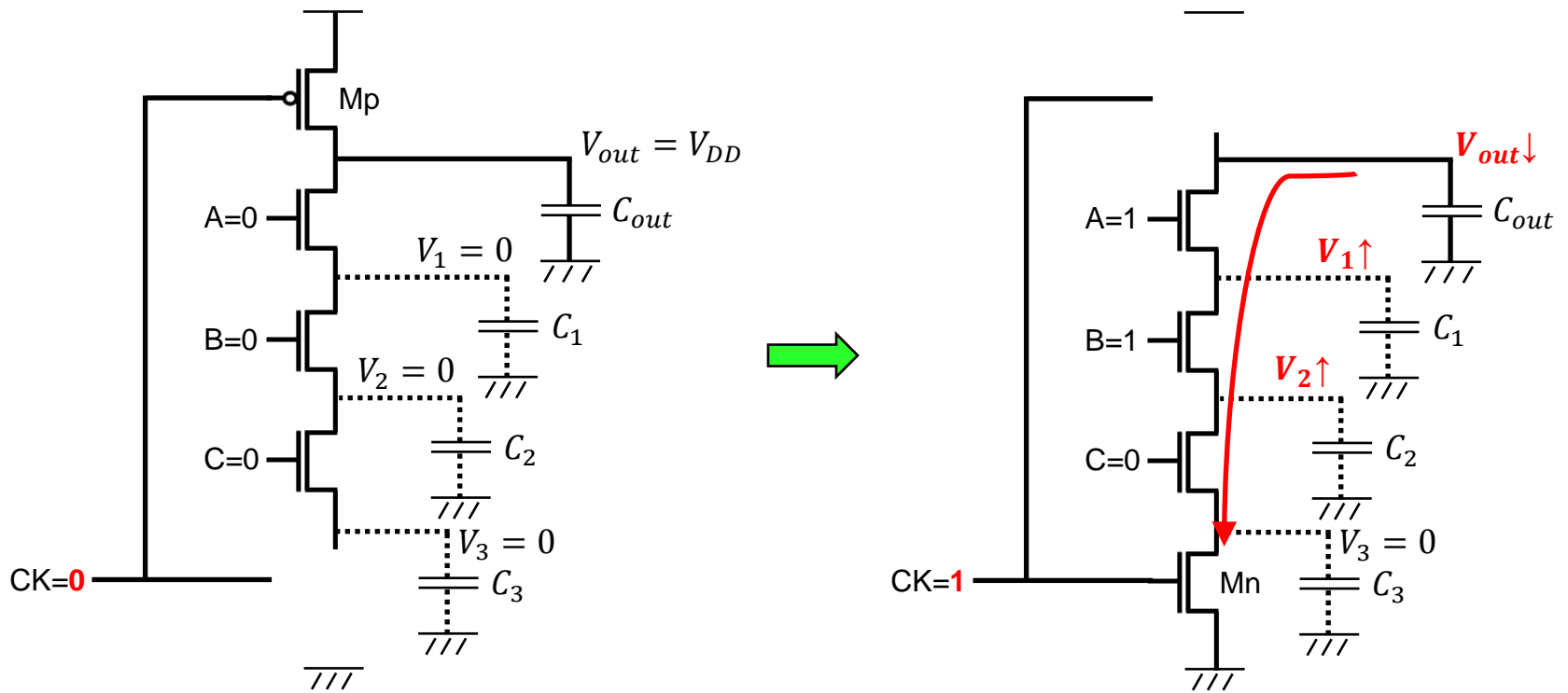


Dynamic CMOS

- Charge sharing

- $V_{out} = V_1 = V_2$


- $Q = C_{out}V_{DD} = C_{out}V_f + C_1V_f + C_2V_f = (C_{out} + C_1 + C_2)V_f$

 - $V_f = \left(\frac{C_{out}}{C_{out} + C_1 + C_2}\right)V_{DD}$




Dynamic CMOS

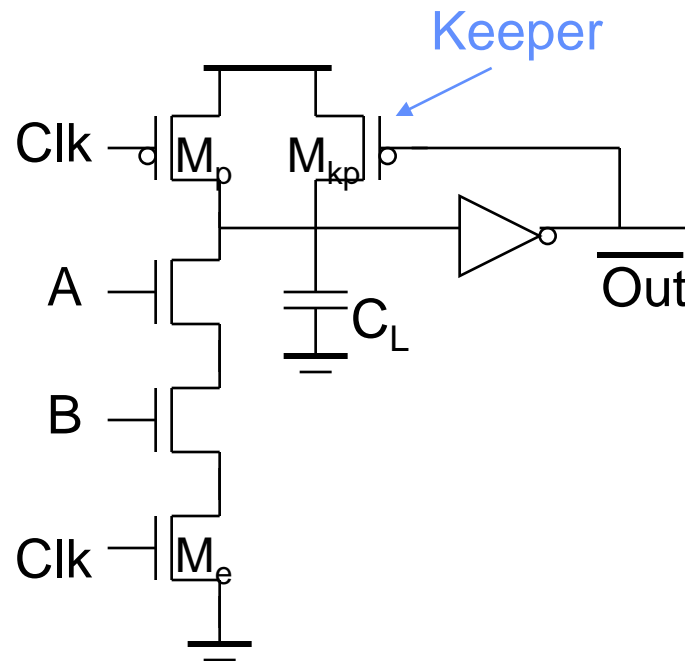- How to solve the charge sharing problem
 - Constraint: $C_{out} \gg C_1 + C_2$
 - Keeper




Dynamic CMOS

 - How to solve the charge sharing problem




Precharge internal nodes using a clock-driven transistor
(at the cost of increased area and power)

Domino Logic

 





Domino Logic

 

Domino Logic

- Example

- $Sum = a \oplus b \oplus c$

    


Properties of Domino Logic

- Only non-inverting logic can be implemented
- Very high speed
 - static inverter can be skewed, only L-H transition
 - Input capacitance reduced


Multiple-Output Domino Logic (MODL)

- $f_1 = G$
- $f_2 = F \cdot G$

 


Dual-Rail Logic Network

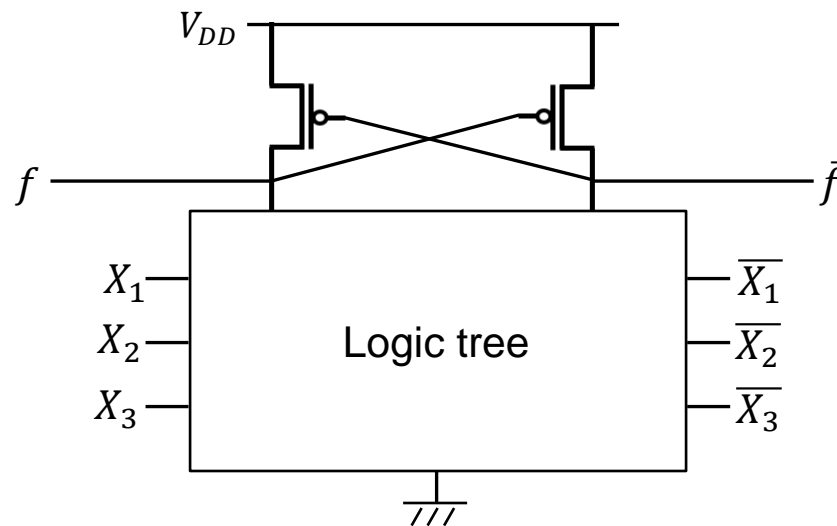- Differential Cascode Voltage Switch Logic (DCVSL)





Pass Transistor Logic

 

- **N transistors**
- **No static consumption**



Pass Transistor Logic

- Example

  


Issues with Pass Transistor Logic

  - Threshold drop
- Capacitive feed through
- Charge sharing
- Follow board notes




Pass Transistor Logic

- Capacitive Feedthrough

 

Transmission Gate Logic

 

- The control signal S turns the transfer gates on and off depending on its value.
- When $s=1$, the upper transfer gate is on and that allows A to follow to the output

- Implement the Multiplexer with static CMOS and compare with this

Transmission Gate Logic

