

---

# **EE434**

## **ASIC & Digital Systems**

Partha Pande  
School of EECS  
Washington State University  
pande@eecs.wsu.edu


Spring 2015  
Dae Hyun Kim  
daehyun@eecs.wsu.edu

---

# Lecture 5

## Layout

# Semiconductor Layers

 

Real Objects
Well (n, p)
Active (n+, p+)
Poly (gate)
Contact
Metal (m1, m2, ...)
Via (v12, v23, ...)


Virtual Objects
Cell boundary
Labels
Pins

# Layout

- INV\_X1

PMOS

NMOS

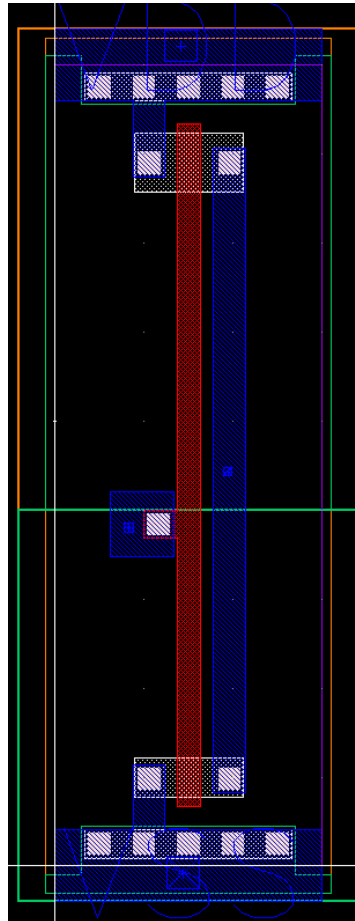

## Real Objects


Well (n, p)



Active (n+, p+)




Poly (gate)

 

Contact



Metal (m1, m2, ...)

 

Metal 1

Via (v12, v23, ...)

## Virtual Objects

Cell boundary




Labels

VDD, VSS

Pins


# Layout

- INV\_X1, INV\_X2, INV\_X4, INV\_X8

 


# Layout

- INV\_X8, INV\_X16, INV\_X32

 


# Layout

- NAND2\_X1

 


- NOR2\_X1

 



# Layout


- BUF\_X1, BUF\_X2, BUF\_X4

 




# Layout


- AND2\_X1

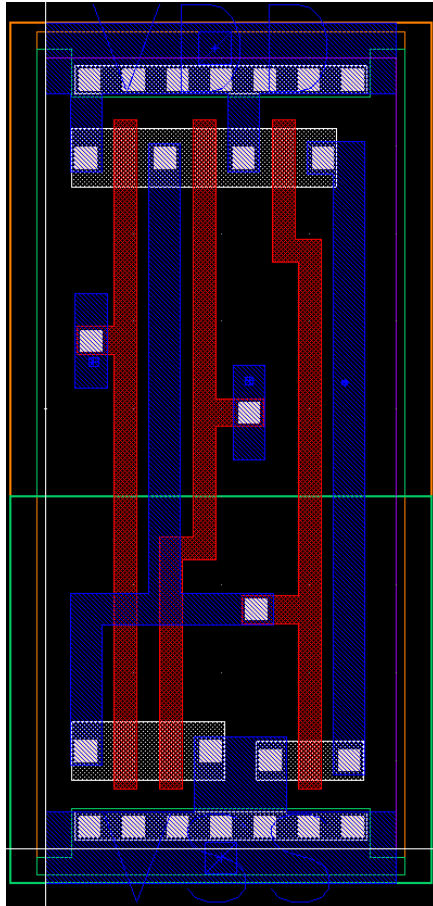

- AND3\_X1

 


- AND4\_X1

 


# Layout

- XOR2\_X1

 


- XNOR2\_X1

 


# Layout

- MUX2\_X1

 

# Layout


- FA\_X1

 



# Layout

- DFF\_X1

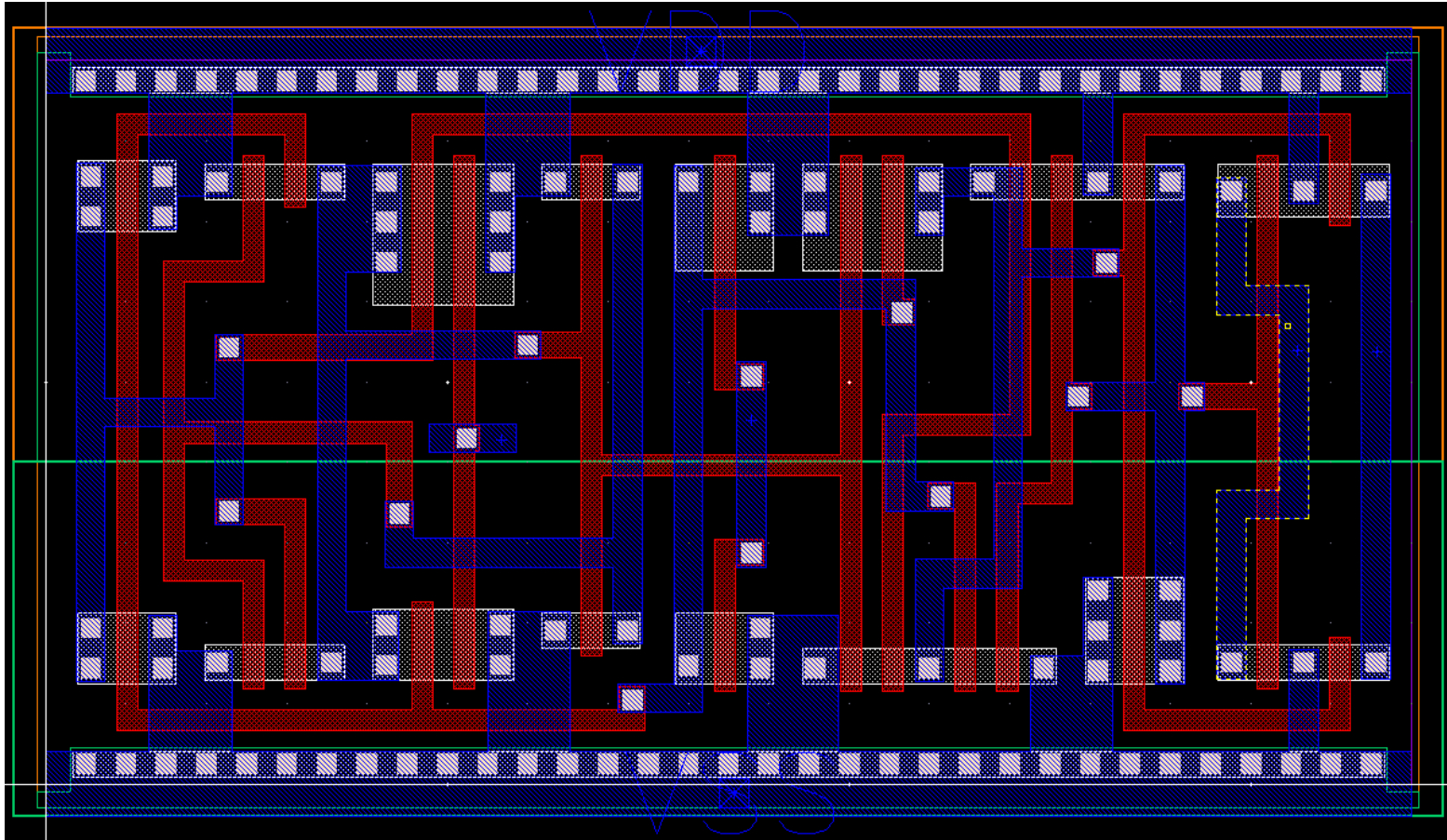

# Layout Generation

---

1. Draw a layout
  - Output: gdsii
2. Design rule check (DRC)
3. Layout vs. Schematic (LVS)
  1. Layout -> netlist 1
  2. Schematic -> netlist 2
  3. netlist 1 == netlist 2
4. Parasitic RC extraction (xRC)
  - Output: A SPICE netlist with parasitic RC
5. Simulation & Characterization