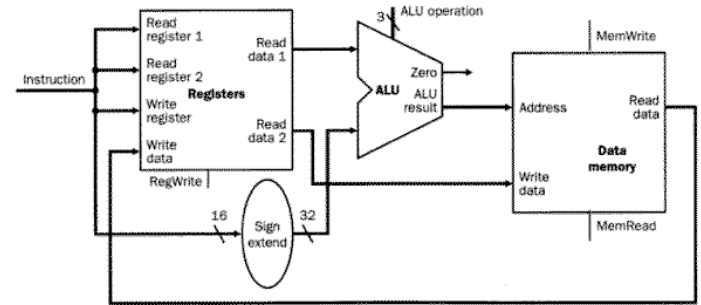
 

EE434
ASIC & Digital Systems

VHDL

Spring 2016
Dae Hyun Kim
daehyun@eecs.wsu.edu

Terminologies

- Entity
 - Basic building block
- Architecture (belongs to an entity)
 - Description of an entity
 - Behavioral
 - Structural



```
ARCHITECTURE mux2arch OF mux2 IS
  SIGNAL sel : INTEGER;
BEGIN
  sel <= 0 WHEN s = '0'
    ELSE 1;
  z <= a AFTER 0.2 NS WHEN sel = 0
    ELSE b AFTER 0.2 NS;
END mux2arch;
```


```
ARCHITECTURE mux2arch OF mux2 IS
BEGIN
  u1 : myAND2 PORT MAP (...);
  u2 : myAND2 PORT MAP (...);
  u3 : myINV PORT MAP (...);
  ...
END mux2arch;
```

Terminologies


- Package
 - Libraries
- Driver
 - A source on a signal
- Bus
 - A group of signals
- Attribute
 - Properties of an object
- Generic
 - Parameter
- Process
 - A basic unit of execution

Terminologies


- Instance

 

Definition

 

Instance (name: u1)

 

Instance (name: u2)

- Instantiation
 - Create an instance

VHDL Coding

- For each functional module
 - Create an entity (myModule).
 - Create an architecture (myModule_arch).
- Create a testbench entity to test it.
 - Create an entity (myModule_tb).
 - Create an architecture (myModule_tb_arch).
 - Define test input and output signals.
 - Instantiate the functional module.
 - Connect the test input and output signals to the ports (pins) of the target module.
 - Set the input signals to a specific vector and observe the output values.

Entity

- Format


```
ENTITY entity_name IS  
  PORT ( port_list );  
END entity_name;
```

- Example

```
ENTITY vmux2 IS  
  PORT ( a, b : IN BIT;  
        s : IN BIT;  
        z : OUT BIT );  
END vmux2;
```

↑
keyword

vmux2
(2:1 MUX)

 

Example

- Create an entity for a four-input NAND gate.
- Create an entity for a full adder.
- Create an entity for a D-F/F.

Example

- Create an entity for a four-input NAND gate.

```
ENTITY vnand4 IS
  PORT ( a, b, c, d : IN BIT;
         zn : OUT BIT );
END vnand4;
```

- Create an entity for a full adder.

```
ENTITY vfa IS
  PORT ( a, b, ci : IN BIT;
         s, co : OUT BIT );
END vfa;
```

- Create an entity for a D-F/F.

```
ENTITY vdff IS
  PORT ( D, CK : IN BIT;
         Q, QN : OUT BIT );
END vdff;
```


Architecture

- Details of an entity
- Format

```
ARCHITECTURE architecture_name OF entity_name IS
BEGIN
END architecture_name;
```

- Example (behavioral description)

```
ARCHITECTURE vnand4_arch OF vnand4 IS
BEGIN
    zn <= NOT (a AND b AND c AND d);
END vnand4_arch;
```

“<=“ is a signal assignment.

Example

- Create an architecture for a three-input OR gate.
 - Entity name: vor2
 - Inputs: a, b, c
 - Output: z
 - Use “OR”.

Example

- Create an architecture for a three-input OR gate.
 - Entity name: vor2
 - Inputs: a, b, c
 - Output: z
 - Use “OR”.

```
ARCHITECTURE vor2_arch OF vor2 IS
BEGIN
  z <= a OR b OR c;
END vor2_arch;
```

Example

- Create an architecture for a two-input MUX.
 - Entity name: vmux2
 - Inputs: a, b, s (selection)
 - Output: z
 - Function
 - $z = a$ when s is 0.
 - $z = b$ when s is 1.

Example

- Create an architecture for a two-input MUX.
 - Entity name: vmux2
 - Inputs: a, b, s (selection)
 - Output: z
 - Function
 - $z = a$ when s is 0.
 - $z = b$ when s is 1.

```
ARCHITECTURE vmux2_arch OF vmux2 IS
BEGIN
  z <= (a AND (NOT s)) OR (b AND s);
END vmux2_arch;
```

Example

- Create an architecture for a full adder.
 - Entity name: vfa
 - Inputs: a, b, ci (carry-in)
 - Outputs: s (sum), co (carry-out)
 - Function
 - $s = a \oplus b \oplus ci$ (^ is XOR)
 - $co = a * b + b * ci + a * ci$
 - Use “XOR” for XOR.

Example

- Create an architecture for a full adder.
 - Entity name: vfa
 - Inputs: a, b, ci (carry-in)
 - Outputs: s (sum), co (carry-out)
 - Function
 - $s = a \oplus b \oplus ci$ (^ is XOR)
 - $co = a \cdot b + b \cdot ci + a \cdot ci$
 - Use “XOR” for XOR.

```
ARCHITECTURE vfa_arch OF vfa IS
BEGIN
  s <= a XOR b XOR ci;
  co <= (a AND b) OR (b AND ci) OR (a AND ci);
END vfa_arch;
```

Architecture

- How does it work?

```
ARCHITECTURE vnand4_arch OF vnand4 IS
BEGIN
  zn <= NOT (a AND b AND c AND d);
END vnand4_arch;
```

- Execution of a statement is triggered by events.
- An event on a signal
 - A change in the value of the signal
 - The signal is *sensitive* to the change.

Architecture

- How does it work?

```
ARCHITECTURE vnand4_arch OF vnand4 IS
BEGIN
  zn <= NOT (a AND b AND c AND d);
END vnand4_arch;
```

- If any of the input signals (a, b, c, d) changes, the above statement will be executed.

Architecture

- How does it work?

```
ARCHITECTURE vfa_arch OF vfa IS
BEGIN
  s <= a XOR b XOR ci;
  co <= (a AND b) OR (b AND ci) OR (a AND ci);
END vfa_arch;
```

- The order of the statements is not important.
- All the statements in an architecture are executed in parallel.

Signal

- Signal
 - Local net
- Format

```
ARCHITECTURE architecture_name OF entity_name IS
    SIGNAL signal_name : signal_type;
BEGIN
END architecture_name;
```

- Example

```
ARCHITECTURE vnand4_arch OF vnand4 IS
    SIGNAL n1, n2 : BIT;
BEGIN
    n1 <= a AND b;
    n2 <= c AND d;
    zn <= NOT (n1 AND n2);
END vnand4_arch;
```

Architecture

- Example (structural description) – Netlist

```
ARCHITECTURE vnand4_arch OF vnand4 IS
  COMPONENT vnand2
    PORT ( a, b : IN BIT; zn : OUT BIT );
  END COMPONENT;
  COMPONENT vor2
    PORT ( a, b : IN BIT; z : OUT BIT );
  END COMPONENT;
  SIGNAL n1, n2 : BIT;
BEGIN
  u1 : vnand2 PORT MAP (a, b, n1);
  u2 : vnand2 PORT MAP (c, d, n2);
  u3 : vor2 PORT MAP (a => n1, b => n2, z => zn);
END vnand4_arch;
```

Testing

- Entity

```
ENTITY FA_X1 IS
  PORT ( a, b, ci : IN BIT; s, co : OUT BIT );
END FA_X1;
```

- Architecture

```
ARCHITECTURE FA_X1_arch OF FA_X1 IS
BEGIN
  s <= a XOR b XOR ci;
  co <= (a AND b) OR (b AND ci) OR (a AND ci);
END FA_X1_arch;
```

Testing

- Test entity

```
ENTITY FA_X1_tb IS
END FA_X1_tb;
```

- Test architecture

```
ARCHITECTURE FA_X1_tb_arch OF FA_X1_tb IS
  COMPONENT FA_X1 PORT ( a, b, ci : IN BIT; s, co : OUT BIT );
  END COMPONENT;
  SIGNAL in1, in2, in3, out1, out2 : BIT;
BEGIN
  u1 : FA_X1 PORT MAP ( a => in1, b => in2, ci => in3, s => out1, co => out2 );
  in1 <= '1';
  in2 <= '0';
  in3 <= '1';
END FA_X1_tb_arch;
```

Testing

The screenshot displays two windows from a testing tool. The 'Objects' window on the left shows a table of variables and their values. The 'Wave' window on the right shows a table of messages and their values, with a corresponding waveform visualization on the right side.

Name	Value	Kind
in1	1	Signal
in2	0	Signal
in3	1	Signal
out1	0	Signal
out2	1	Signal

Messages	Kind
:fa_x1_tb;in1	1
:fa_x1_tb;in2	0
:fa_x1_tb;in3	1
:fa_x1_tb;out1	0
:fa_x1_tb;out2	1

Architecture

- Sequential

```
ARCHITECTURE vnand4_arch OF vnand4 IS
BEGIN
  PROCESS (a, b, c, d)
    VARIABLE v1 : INTEGER;
  BEGIN
    IF (a = '0') THEN v1 := 1;
    ELSIF (b = '0') THEN v1 := 1;
    ELSIF (c = '0') THEN v1 := 1;
    ELSIF (d = '0') THEN v1 := 1;
    ELSE v1 := 0;
    END IF;
    CASE v1 IS
      WHEN 1 =>
        zn <= '1';
      WHEN OTHERS =>
        zn <= '0';
    END CASE;
  END PROCESS;
END vnand4_arch;
```