

Homework Assignment 2 (Due Feb. 1st at the beginning of the class)

* Submission policy: Please zip your source code and waveform screenshots into a single file and send it to daehyun@eecs.wsu.edu. The file name should be *firstname_lastname.zip* (or .tar.gz or .tar ...)

(1) [VHDL, 10 points] Design a positive-edge-triggered D-FF with synchronous reset and set. Use the following spec:

- Input ports: D, R, S, Clk
- Output port: Q
- Function:
 - $Q = 0$ if reset = 1 (regardless of D and set) when Clk \uparrow .
 - $Q = 1$ if reset = 0 and set = 1 (regardless of D) when Clk \uparrow .
 - $Q = D$ if reset = 0 and set = 0 when Clk \uparrow .
- Create your own test input vectors to test all the following 16 combinations:
 - reset=0, set=0, D=0, Clk \uparrow (when Q=0)
 - reset=0, set=0, D=0, Clk \uparrow (when Q=1)
 - reset=0, set=0, D=1, Clk \uparrow (when Q=0)
 - reset=0, set=0, D=1, Clk \uparrow (when Q=1)
 - ...
- [Submit] Source code + test waveform (inputs + outputs)

* Source code (PDF with synchronous RS)

```
LIBRARY IEEE;
```

```
USE IEEE.std_logic_1164.all;
```

```
ENTITY vPdff_SRS IS
```

```
    PORT ( D, R, S, Clk : IN std_logic;
```

```
          Q : OUT std_logic );
```

```
END vPdff_SRS;
```

```
ARCHITECTURE vPdff_SRS_arch OF vPdff_SRS IS
```

```
BEGIN
```

```
    PROCESS (Clk)
```

```

BEGIN
  IF rising_edge(Clk) THEN
    IF (R = '1') THEN
      Q <= '0';
    ELSIF (S = '1') THEN
      Q <= '1';
    ELSE
      Q <= D;
    END IF;
  END IF;
END PROCESS;
END vPDFF_SRS_arch;

```

*** Source code (testbench)**

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.all;

```

```

ENTITY vPDFF_SRS_tb IS
END vPDFF_SRS_tb;

```

```

ARCHITECTURE vPDFF_SRS_tb_arch OF vPDFF_SRS_tb IS
  COMPONENT vPDFF_SRS PORT ( D, R, S, Clk : IN std_logic; Q : OUT std_logic ); END
  COMPONENT;

```

```

  SIGNAL g_in : std_logic_vector (3 downto 0);
  SIGNAL g_out : std_logic;
BEGIN
  u1 : vPDFF_SRS PORT MAP (g_in(1), g_in(3), g_in(2), g_in(0), g_out);

```

```

PROCESS
BEGIN
  g_in <= "0000"; -- R/S/D/Clk
  WAIT FOR 0.1 ns;
  g_in <= "0001"; -- Q = 0
  WAIT FOR 0.1 ns;
  g_in <= "0000";
  WAIT FOR 0.1 ns;

```

```
g_in <= "0001"; -- case 0: RSDQ=0000. Q: 0->0
WAIT FOR 0.1 ns;
g_in <= "0010"; -- this input transition is safe
WAIT FOR 0.1 ns;
g_in <= "0011"; -- case 2: RSDQ=0010. Q: 0->1
WAIT FOR 0.1 ns;
g_in <= "0000";
WAIT FOR 0.1 ns;
g_in <= "0001"; -- case 1: RSDQ=0001. Q: 1->0
WAIT FOR 0.1 ns;
g_in <= "0100";
WAIT FOR 0.1 ns;
g_in <= "0101"; -- case 4: RSDQ=0100. Q: 0->1
WAIT FOR 0.1 ns;
g_in <= "0010";
WAIT FOR 0.1 ns;
g_in <= "0011"; -- case 3: RSDQ=0011. Q: 1->1
WAIT FOR 0.1 ns;
g_in <= "0100";
WAIT FOR 0.1 ns;
g_in <= "0101"; -- case 5: RSDQ=0101. Q: 1->1
WAIT FOR 0.1 ns;
g_in <= "1000";
WAIT FOR 0.1 ns;
g_in <= "1001"; -- case 9: RSDQ=1001. Q: 1->0
WAIT FOR 0.1 ns;
g_in <= "0110";
WAIT FOR 0.1 ns;
g_in <= "0111"; -- case 6: RSDQ=0110. Q: 0->1
WAIT FOR 0.1 ns;
g_in <= "0110";
WAIT FOR 0.1 ns;
g_in <= "0111"; -- case 7: RSDQ=0111. Q: 1->1
WAIT FOR 0.1 ns;
g_in <= "1000";
WAIT FOR 0.1 ns;
g_in <= "1001"; -- Q: 0
```

```
WAIT FOR 0.1 ns;
g_in <= "1000";
WAIT FOR 0.1 ns;
g_in <= "1001"; -- case 8: RSDQ=1000. Q: 0->0
WAIT FOR 0.1 ns;
g_in <= "1010";
WAIT FOR 0.1 ns;
g_in <= "1011"; -- case 10: RSDQ=1010. Q: 0->0
WAIT FOR 0.1 ns;
g_in <= "0100";
WAIT FOR 0.1 ns;
g_in <= "0101"; -- Q = 1
WAIT FOR 0.1 ns;
g_in <= "1010";
WAIT FOR 0.1 ns;
g_in <= "1011"; -- case 11: RSDQ=1011. Q: 1->0
WAIT FOR 0.1 ns;
g_in <= "1100";
WAIT FOR 0.1 ns;
g_in <= "1101"; -- case 12: RSDQ=1100. Q: 0->0
WAIT FOR 0.1 ns;
g_in <= "0100";
WAIT FOR 0.1 ns;
g_in <= "0101"; -- Q = 1
WAIT FOR 0.1 ns;
g_in <= "1100";
WAIT FOR 0.1 ns;
g_in <= "1101"; -- case 13: RSDQ=1101. Q: 1->0
WAIT FOR 0.1 ns;
g_in <= "1110";
WAIT FOR 0.1 ns;
g_in <= "1111"; -- case 14: RSDQ=1110. Q: 0->0
WAIT FOR 0.1 ns;
g_in <= "0100";
WAIT FOR 0.1 ns;
g_in <= "0101"; -- Q = 1
WAIT FOR 0.1 ns;
```

```

g_in <= "1110";
WAIT FOR 0.1 ns;
g_in <= "1111"; -- case 15: RSDQ=1111. Q: 1->0
WAIT FOR 100 ns;
END PROCESS;
END vPDFF_SRS_tb_arch;

```

* **Waveform**



(2) [VHDL, 10 points] Design a positive-edge-triggered D-FF with asynchronous reset and set. Use the following spec:

- Input ports: D, R, S, Clk
- Output ports: Q
- Function:
 - $Q = 0$ if reset = 1 (regardless of D, set, and Clk).
 - $Q = 1$ if reset = 0 and set is 1 (regardless of D and Clk).
 - $Q = D$ if reset = 0 and set is 0 when Clk \uparrow .
 - Test your design using the same input vectors you created above.
- **[Submit]** Source code + test waveform (inputs + outputs)

* **Source code (PDFF with asynchronous RS)**

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.all;

ENTITY vPDFF_ARS IS
  PORT ( D, R, S, Clk : IN std_logic;
        Q : OUT std_logic );
END vPDFF_ARS;

ARCHITECTURE vPDFF_ARS_arch OF vPDFF_ARS IS
BEGIN
  PROCESS (R, S, Clk)

```

```

BEGIN
  IF (R = '1') THEN
    Q <= '0';
  ELSIF (S = '1') THEN
    Q <= '1';
  ELSIF rising_edge(Clk) THEN
    Q <= D;
  END IF;
END PROCESS;
END vPDFF_ARS_arch;

```

*** Source code (testbench)**

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.all;

```

```

ENTITY vPDFF_ARS_tb IS
END vPDFF_ARS_tb;

```

```

ARCHITECTURE vPDFF_ARS_tb_arch OF vPDFF_ARS_tb IS
  COMPONENT vPDFF_ARS PORT ( D, R, S, Clk : IN std_logic; Q : OUT std_logic ); END
  COMPONENT;

```

```

  SIGNAL g_D, g_R, g_S, g_Clk : std_logic;
  SIGNAL g_out : std_logic;

```

```

BEGIN
  u1 : vPDFF_ARS PORT MAP (g_D, g_R, g_S, g_Clk, g_out);

```

```

PROCESS

```

```

  BEGIN

```

```

    g_D <= '0';

```

```

    g_R <= '1';

```

```

    g_S <= '0';

```

```

    g_Clk <= '0';

```

```

    WAIT FOR 0.1 ns;

```

```

  FOR i1 IN 0 TO 1 LOOP

```

```

    IF (i1 = 0) THEN

```

```
    g_R <= '0';
ELSE
    g_R <= '1';
END IF;

FOR i2 IN 0 TO 1 LOOP
    IF (i2 = 0) THEN
        g_S <= '0';
    ELSE
        g_S <= '1';
    END IF;

    FOR i3 IN 0 TO 1 LOOP
        IF (i3 = 0) THEN
            g_D <= '0';
        ELSE
            g_D <= '1';
        END IF;

        FOR i4 IN 0 TO 1 LOOP
            IF (i4 = 0) THEN
                g_Clk <= '0';
            ELSE
                g_Clk <= '1';
            END IF;

            WAIT FOR 0.1 ns;
        END LOOP;
    END LOOP;
END LOOP;

    WAIT FOR 100 ns;
END PROCESS;
END vPDFF_ARS_tb_arch;
```

*** Waveform**

