 


Homework Assignment 4 (Due Feb. 22nd at the beginning of the class)


- (1) [Static CMOS Gates, 5 points] Draw a transistor-level schematic for the following function. Use (6 NMOS and 6 PMOS transistors) or (5 NMOS and 5 PMOS transistors).

$$F = A \cdot B + C \cdot D$$

- (2) [Static CMOS Gates, 5 points] A pull-down network of a Boolean function is shown below. Draw its pull-up network to complete the function.



 - (3) [Static CMOS Gates, 5 points] A pull-up network of a Boolean function is shown below. Draw its pull-down network to complete the function.



- (4) [Static CMOS Gates, 5 points] Draw a transistor-level schematic for the following function. Try to minimize # transistors. Inverted inputs are not provided.

$$F = \overline{\overline{A} + \overline{B} + \overline{C}}$$