 


Homework Assignment 4 (Due Feb. 22nd at the beginning of the class)


- (1) [Static CMOS Gates, 5 points] Draw a transistor-level schematic for the following function. Use (6 NMOS and 6 PMOS transistors) or (5 NMOS and 5 PMOS transistors).


$$F = A \cdot B + C \cdot D$$





(or $F = \overline{\overline{A \cdot B} + \overline{C \cdot D}} = \overline{\overline{A \cdot B} \cdot \overline{C \cdot D}}$, so you can use three two-input NAND gates (6 NMOS + 6 PMOS transistors))

 - (2) [Static CMOS Gates, 5 points] A pull-down network of a Boolean function is shown below. Draw its pull-up network to complete the function.



 

  (3) [Static CMOS Gates, 5 points] A pull-up network of a Boolean function is shown below. Draw its pull-down network to complete the function.



(4) [Static CMOS Gates, 5 points] Draw a transistor-level schematic for the following function. Try to minimize # transistors. Inverted inputs are not provided.

$$F = \overline{\overline{A + B + C}}$$

$$F = A \cdot B \cdot C$$

