

Homework Assignment 5 (Due Feb. 26th at the beginning of the class)

* Submission policy: Please zip your source code and waveform screenshots into a single file and send it to daehyun@eecs.wsu.edu. The file name should be *firstname_lastname.zip* (or .tar.gz or .tar ...)


(1) [Switching Characteristics of a CMOS Inverter, 10 points] First, go to “Labs” and see “tut-hspice.pdf”. It shows how to use HSPICE. Once you are done with it, download the following file into your working directory.

- <http://eecs.wsu.edu/~ee434/Homework/hw05.zip>
- Unzip it.
 - `> unzip hw05.zip`
- You will see the following files.
 - 45nm_PTM_HP_v2.1.pm (HSPICE transistor models)
 - inv-ac.sp (an HSPICE netlist for the simulation of switching characteristics of an inverter)
 - inv-dc.sp (an HSPICE netlist for the simulation of DC characteristics of an inverter)
- The size of the 1X inverter is $(W_n, W_p) = (45\text{nm}, 70\text{nm})$. The rise/fall time of the 1X inverter is 216ps as shown in the tutorial.
- Upsize the inverter to 2X, i.e., $(W_n, W_p) = (45\text{nm} * 2, 70\text{nm} * 2) = (90\text{nm}, 140\text{nm})$. Measure the rise and fall times again.
- **[Submit]** Fill the following table.

Inverter size	Rise time (ps)	Fall time (ps)
1X		
2X		
3X		
4X		
8X		
16X		
32X		

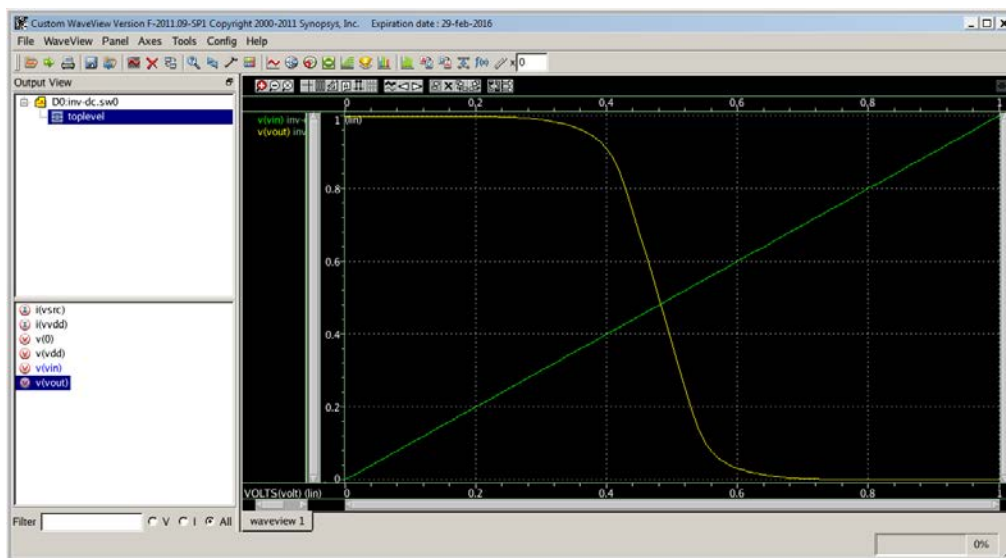(2) [DC Characteristics of a CMOS Inverter, 20 points] Open “inv-dc.sp” in a text editor and see the contents of the file. We use “.DC” for DC simulation.

- Run HSPICE for the DC simulation.
 - > hspice inv-dc.sp
- Open the DC simulation result.
 - wv inv-dc.sw0
- Double-click v(vin) and v(vout) to visualize the DC characteristics of the inverter.
- Drag and drop one of the graphs into the other one as follows:



- Measure V_{IL} , V_{IH} , V_{OL} , V_{OH} (use “Difference” in the measurement tool).
- In my window, $V_{IL} = 375mV$, $V_{IH} = 580mV$, $V_{OL} = 45mV$, and $V_{OH} = 950mV$.
- $NM_L = 375mV - 45mV = 330mV$, $NM_H = 950mV - 580mV = 370mV$.
- **[Submit]** Use ($W_n = 90nm$, $W_p = 70nm$) and run DC sweep analysis again. Compute and submit NM_L and NM_H .
- **[Submit]** Use ($W_n = 45nm$, $W_p = 140nm$) and run DC sweep analysis again. Compute and submit NM_L and NM_H .
- **[Submit]** Use ($W_n = 90nm$, $W_p = 140nm$) and run DC sweep analysis again. Compute and submit NM_L and NM_H .