
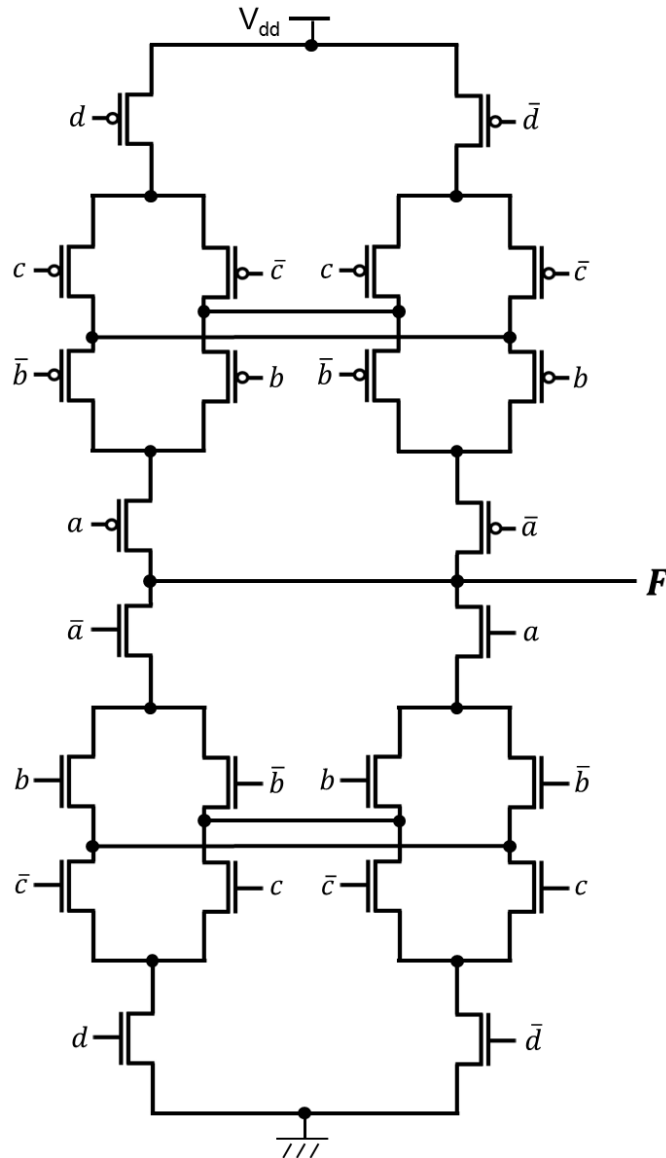


## Homework Assignment 6 (Due Mar. 4th at the beginning of the class)

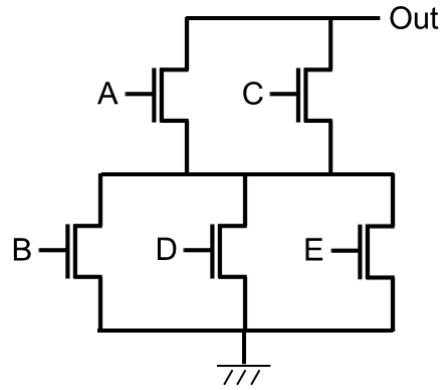
- (1) [Transistor Sizing, 5 points]  $\mu_n = 2\mu_p$ .  $R$  is the resistance of a 1X NMOS transistors. The target time constant is  $RC$  where  $C$  is the load capacitance. Size the transistors in the following figure to satisfy the target time constant (try not to over-optimize them).



- (2) [Transistor Sizing, 5 points]  $R$  is the resistance of a 1X NMOS transistors. The target time constant is  $RC$  where  $C$  is the load capacitance. Size the transistors in the following pull-down network to satisfy the time constant. However, **minimize** the total width of the transistors.



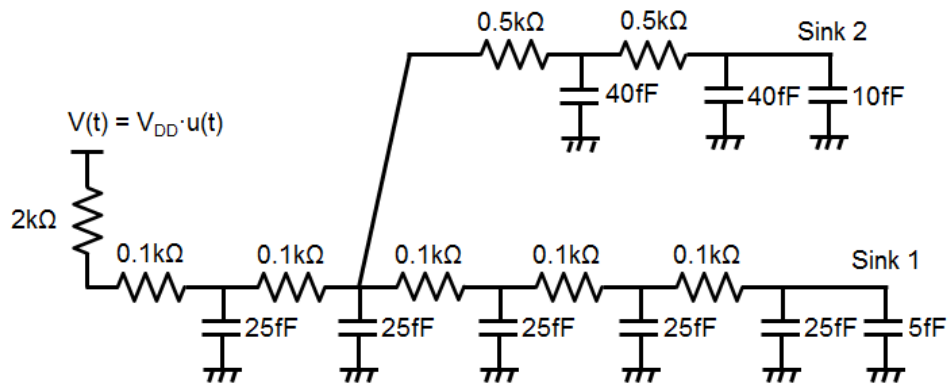- (3) [Elmore Delay, 5 points] Compute Elmore delay at Sink 1 and Sink 2 in the following figure.



- (4) **[Switching Characteristics, 5 points]** Compute the rise time at the output node in the following figure.  $C_1$  and  $C_2$  are parasitic capacitances at the internal nodes. The input switches from  $(A, B, C, D, E, F) = (1, 0, 0, 0, 0, 0)$  to  $(0, 0, 0, 1, 0, 1)$ . Use  $R_X$  (where  $X=A, B, C, D, E, F$ ) for the resistance of transistor  $X$ .

