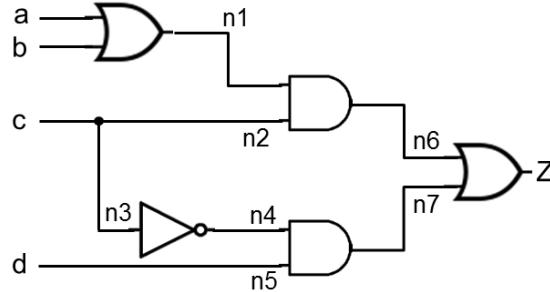


## Homework Assignment 9

**(Due Apr. 25<sup>th</sup> at the beginning of the class)**

1. [Testing, 20 points] Find all input vectors that can detect the following stuck-fault errors.



$$Z = (a + b)c + \bar{c}d$$

- a s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{bc + \bar{c}d\} = 1 \Rightarrow abcd = 101 *$
- a s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{c + \bar{c}d\} = 1 \Rightarrow abcd = 001 *$
- b s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{ac + \bar{c}d\} = 1 \Rightarrow abcd = 011 *$
- b s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{c + \bar{c}d\} = 1 \Rightarrow abcd = 001 *$
- c s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{d\} = 1 \Rightarrow abcd = 1010, 0110, 1110, 0011$
- c s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{a + b\} = 1 \Rightarrow abcd = 0001, 0100, 1000, 1100$
- d s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c\} = 1 \Rightarrow abcd = ** 01$
- d s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c + \bar{c}\} = 1 \Rightarrow abcd = ** 00$
- n1 s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{\bar{c}d\} = 1 \Rightarrow abcd = 101 *, 011 *, 111 *$
- n1 s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{c + \bar{c}d\} = 1 \Rightarrow abcd = 001 *$
- n2 s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{\bar{c}d\} = 1 \Rightarrow abcd = 101 *, 011, *, 111 *$
- n2 s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b) + \bar{c}d\} = 1 \Rightarrow abcd = 100 *, 010 *, 110 *$
- n3 s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c + d\} = 1 \Rightarrow abcd = 0011$
- n3 s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c\} = 1 \Rightarrow abcd = ** 01$
- n4 s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c\} = 1 \Rightarrow abcd = ** 01$
- n4 s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c + d\} = 1 \Rightarrow abcd = 0011$
- n5 s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c\} = 1 \Rightarrow abcd = ** 01$
- n5 s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c + \bar{c}\} = 1 \Rightarrow abcd = ** 00$
- n6 s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{\bar{c}d\} = 1 \Rightarrow abcd = 101 *, 011 *, 111 *$
- n6 s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{1\} = 1 \Rightarrow abcd = ** 00, 001 *$
- n7 s-a-0:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{(a + b)c\} = 1 \Rightarrow abcd = ** 01$
- n7 s-a-1:  $Z \oplus Z_f = \{(a + b)c + \bar{c}d\} \oplus \{1\} = 1 \Rightarrow abcd = ** 00, 001 *$

- Z s-a-0:  $Z \oplus Z_f = \{(a+b)c + \bar{c}d\} \oplus \{0\} = 1 \Rightarrow abcd =** 01, 101 *, 011 *, 111 *$
- Z s-a-1:  $Z \oplus Z_f = \{(a+b)c + \bar{c}d\} \oplus \{1\} = 1 \Rightarrow abcd =** 00, 001 *$