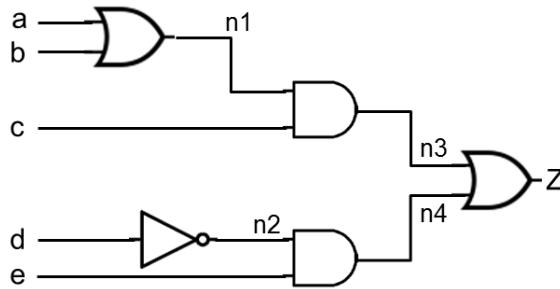


## Homework Assignment 10

**(Due Apr. 29<sup>th</sup> at the beginning of the class)**

1. [Testing, 20 points] Apply the ATPG algorithm to find an input vector that can detect a stuck-at-1 fault at n2 in the following figure.



1.  $a = b = c = d = e = X$
2. Justify (n2, 0)
  - a. Set n2=0 (i.e.,  $d = 1$ ).
  - b.  $d$  is a PI, so return.
3. Propagate (n2,  $\bar{D}$ )
  - a. Set n2= $\bar{D}$
  - b.  $k = n4$
  - c.  $c = 0$
  - d.  $i = 0$
  - e. Justify (e, 1)
    - i. Set  $e = 1$
    - ii.  $e$  is a PO, so return.
  - f. Propagate (n4,  $\bar{D} \oplus 0$ ) = Propagate (n4,  $\bar{D}$ )
    - i. Set n4= $\bar{D}$
    - ii.  $k = Z$
    - iii.  $c = 1$
    - iv.  $i = 0$
    - v. Justify (n3, 0)
      1. Set n3=0.
      2.  $c = 0$
      3.  $i = 0$
      4.  $inval=0$
      5.  $inval \neq 1$ , so Justify (n1, 0) or Justify (c, 0). I'll choose the latter.
      6. Justify (c, 0) sets c to 0 and returns.  $c = 0$ .
    - vi. Propagate (Z,  $\bar{D} \oplus 0$ ) = Propagate (Z,  $\bar{D}$ )
      1. Set Z =  $\bar{D}$

2.  $Z$  is a PO, so return.

Thus,  $(abcde) = (\text{XX011})$  detects the fault.

Notice that if we choose to run Justify ( $n1, 0$ ) instead of Justify ( $c, 0$ ),  $n1=0$ ,  $c=1$ ,  $i=0$ ,  $inval=0$ ,  $inval=\bar{c}$ , so we call Justify ( $a, 0$ ) and Justify ( $b, 0$ ), which set  $a$  and  $b$  to 0. In this case, we obtain  $(abcde) = (\text{00X11})$ .

If we solve it by  $Z \oplus Z_f$ , we obtain both.