
EE434
ASIC & Digital Systems


Lab1

Design of a Register File and an ALU for MIPS64

Dae Hyun Kim
daehyun@eecs.wsu.edu


Overview

- Register File (RF)

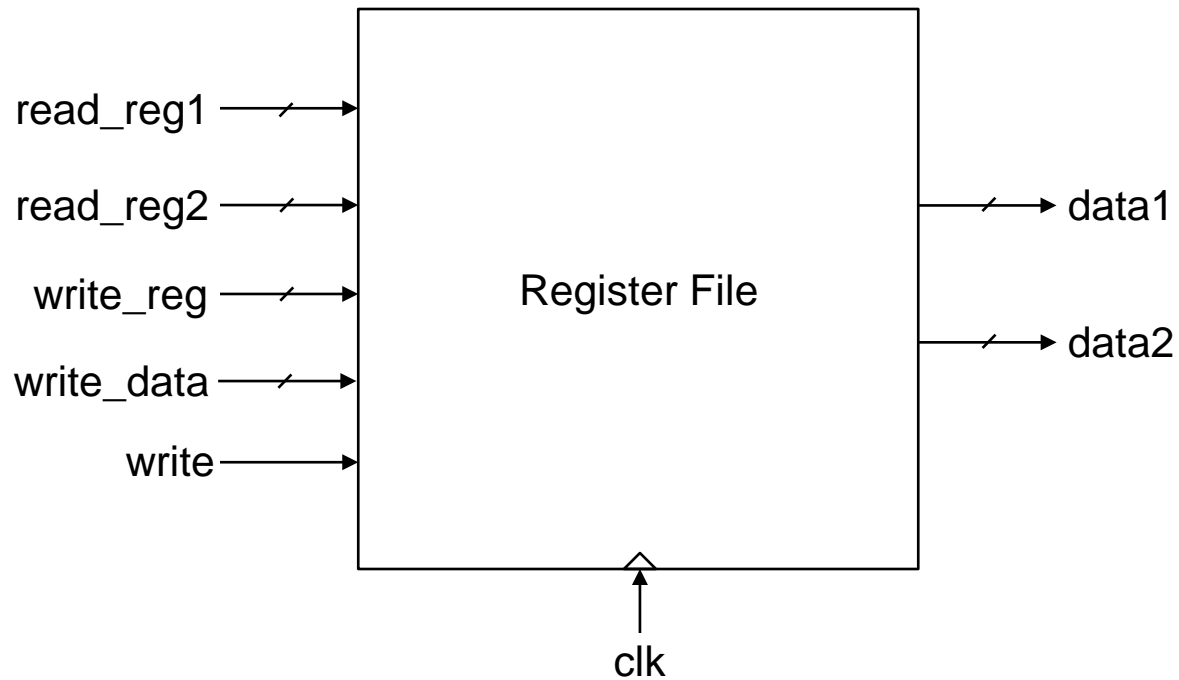


Overview

- Arithmetic Logic Unit (ALU)

 

Overview

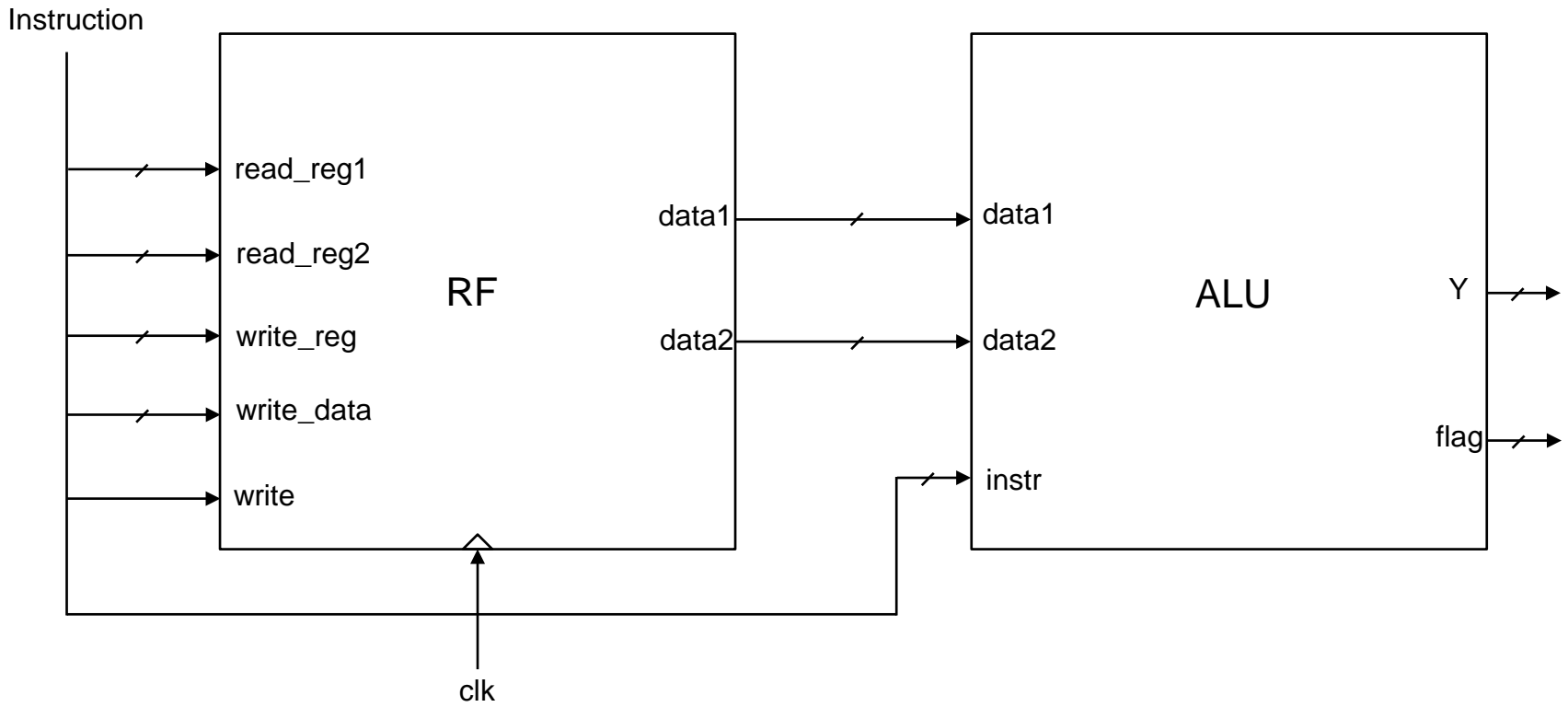

RF: Inputs and Outputs

- Input
 - Register id (0 ~ 31)
 - read_reg1: std_logic_vector [4:0]
 - read_reg2: std_logic_vector [4:0]
 - write_reg: std_logic_vector [4:0]
 - Data
 - write_data: std_logic_vector [63:0]
 - Control
 - write: std_logic
 - Clock
 - clk: std_logic
- Output
 - data1: std_logic_vector [63:0]
 - data2: std_logic_vector [63:0]

RF: Architecture

- It has 32 64-bit registers (r0 ~ r31).
- Each register is accessed by a 5-bit vector.

RF: Functionality

- When Clk ↑
 - If write = '0'
 - data1 <= mem[read_reg1]
 - data2 <= mem[read_reg2]
 - If write = '1'
 - mem[write_reg] <= write_data

ALU: Inputs and Outputs

- Input
 - Data
 - data1: std_logic_vector [63:0]
 - data2: std_logic_vector [63:0]
 - Control
 - instr: std_logic_vector [11:0]
- Output
 - Y: std_logic_vector [63:0]
 - flag: std_logic_vector [1:0]

ALU


- flag
 - flag[0] (zero flag)
 - 1 if the result is zero
 - 0 otherwise
 - flag[1] (branch flag)
 - 1 if “branch” should executed
 - 0 otherwise

ALU: Functionality


instr [11:6]	instr [5:0]	Function	Y	flag [1:0]
000000	100000	ADD	data1 + data2	flag[0]
000000	100010	SUB	data1 – data2	flag[0]
000000	100100	AND	data1 AND data2	flag[0]
000000	100101	OR	data1 OR data2	flag[0]
000000	000000	SLL	shift left (data1 << data2)	
000000	000010	SRL	shift right (data1 >> data2)	
000100	-----	BEQ	Branch on equal (data1 == data2)	flag[1]
000101	-----	BNE	Branch on not equal (data1 != data2)	flag[1]
000001	-----	BGEZ	Branch if data1 ≥ 0	flag[1]
000110	-----	BLEZ	Branch if data1 ≤ 0	flag[1]

ALU: Functionality

 
- Shift left (SLL) or shift right (SRL)
 - data2 = k



- SLL

 

- SRL

 

Example:

data2 = 000...0011 (3_{10})

data1 = 111...1111

SLL: Y = 111...11000

SRL: Y = 000111...111

Implement SLL and SRL!

Do not use "sll" and "srl"!

ALU: Functionality

- Branch
 - Set flag[1] to '1' if the branch condition is true.

Simulation

- Test input vectors will be given to you.
- Entity definition

```
ENTITY myMIPS IS
  PORT (
    read_reg1, read_reg2, write_reg : IN std_logic_vector (4 DOWNTO 0);
    write_data : IN std_logic_vector (63 DOWNTO 0);
    instr : IN std_logic_vector (11 DOWNTO 0);
    write, clk : IN std_logic;
    Y : OUT std_logic_vector (63 DOWNTO 0);
    flag : OUT std_logic_vector (1 DOWNTO 0)
  );
END myMIPS;
```

Submission

- Deadline
 - Feb. 28 (Sunday), 11:59:59pm.
- What to submit
 - Source code