

# Solution to HW 3

(3)

(1) Note that

$$f = x_2(x_1 x_4 + x_3 \bar{x}_4) + \bar{x}_2(\bar{x}_1 \bar{x}_3)$$

$$= x_2 \cdot g + \bar{x}_2 \cdot h$$

where  $g = x_1 x_4 + x_3 \bar{x}_4$

and  $h = \bar{x}_1 \bar{x}_3$

} both can be implemented using 3 input LUTs.

(2)

$$F = ABC\bar{C} + \bar{A}C\bar{D} + ABD + \bar{B}C\bar{D}$$

$$= AB(\bar{C} + D) + (\bar{A} + \bar{B})C\bar{D}$$

$$= AB \oplus C\bar{D}$$

$$F_1 = AB$$

$$F_2 = C\bar{D}$$

$$F = F_1 \oplus F_2$$

(3)


Hard Macro —

Specifies how logic elements are physically interconnected and placed

Soft Macro —


only logical interconnection specified

(4)

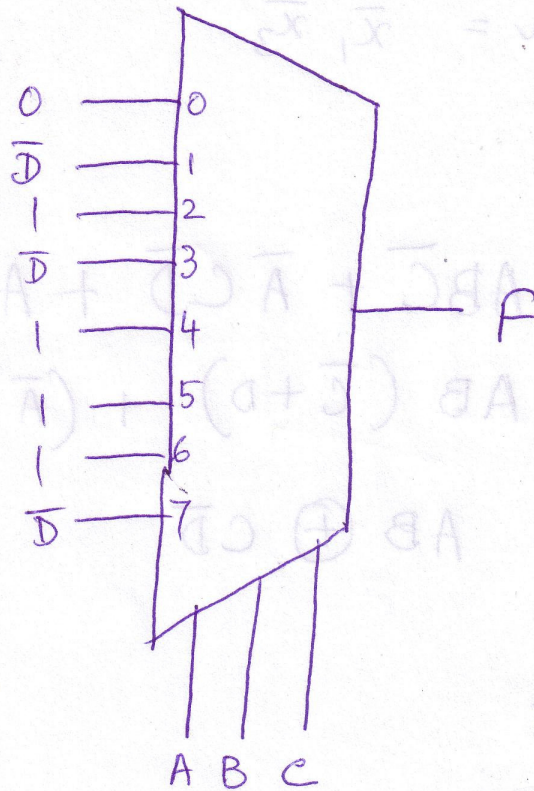


5

$$f = x_1 x_2 + x_3$$

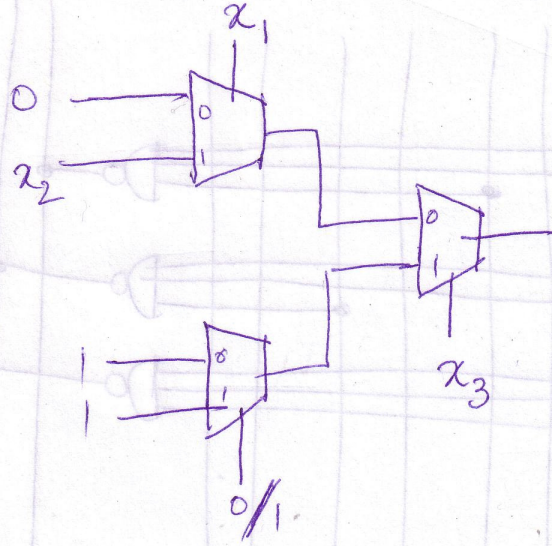
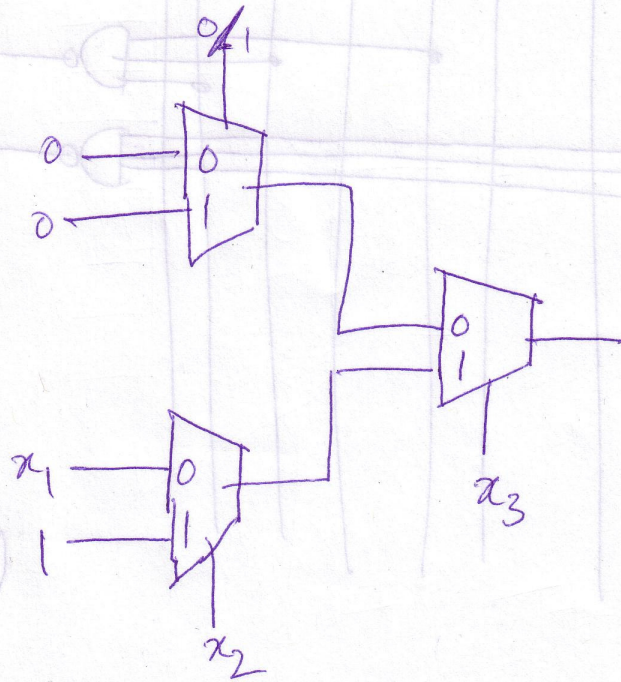
$$f = x_1 x_3 + x_2 x_3 = x_3 (x_1 + x_2)$$





(7)

