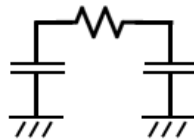


## Homework Assignment 6

(Due Mar. 30<sup>th</sup> at the beginning of the class)


1. [Wire Resistance and Capacitance, 20 points]

- [Submit] Compute the resistance of the following wire:
  - $\rho = 2.0 \cdot 10^{-8} \Omega \cdot m$
  - $\epsilon_{OX} = 2.0 \cdot 10^{-11} F/m$
  - width:  $0.14\mu m$
  - spacing between the wire and the ground plane:  $0.28\mu m$
  - length:  $100\mu m$
  - thickness:  $0.28\mu m$
  - spacing between two laterally-adjacent wires:  $0.14\mu m$
- [Submit] Compute the area capacitance of the above wire:
- [Submit] Compute the lateral capacitance of the above wire.
- [Submit] Compute the fringe capacitance of the above wire.
- [Submit] The above wire is driven by a buffer whose output resistance is  $1k\Omega$ . The other end of the wire is connected to a gate whose input capacitance is  $5fF$ . Compute Elmore delay at the load.  $C_{wire} = 2 * C_{area} + 2 * C_{lateral} + 4 * C_{fringe}$ . Use the PI model to model the above wire.




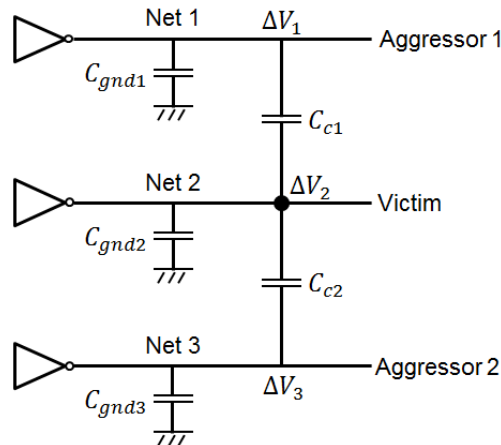2. [Coupling, 10 points]

- In real designs, a victim net is usually surrounded by multiple aggressors. The following models a victim net surrounded by two aggressors.



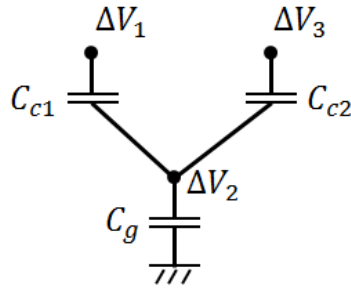
- To compute  $\Delta V_2$ , we can use the following model:




- **[Submit]** Represent  $\Delta V_2$  as a function of  $\Delta V_1$ ,  $\Delta V_3$ ,  $C_{c1}$ ,  $C_{c2}$ , and  $C_g$ .

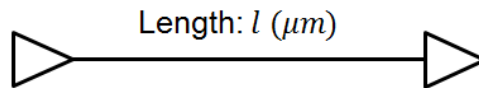3. **[Elmore Delay, 10 points]**

- We want to compute Elmore delay for the following net:



- This net is modeled as follows:

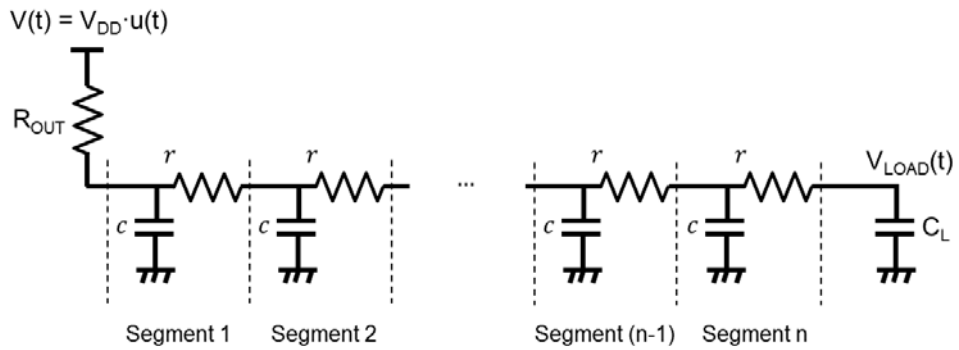

- $R_w$ : Total wire resistance
- $C_w$ : Total wire capacitance
- $r = \frac{R_w}{n}$ ,  $c = \frac{C_w}{n}$
- **[Submit]** Compute Elmore Delay at the load when  $n$  goes to infinity. Represent the delay as a function of  $R_{OUT}$ ,  $C_L$ ,  $R_w$ , and  $C_w$ .